 


ECE 448
Midterm Exam
Thursday, March 3, 2011

Problem 1 (20%)

Assuming state diagram given below, supplement timing waveforms given in the answer sheet with the correct values of signals **State**, **g1**, **g2**, **g3**, in the interval from 0 to 575 ns.




Problem 2


Introduction

The digital circuit shown in the diagrams below is called a Non-linear Feedback Shift Register (NFSR). The Feedback Function F of this circuit is given by the block diagram shown on the next page.

NFSR: Top-Level Circuit

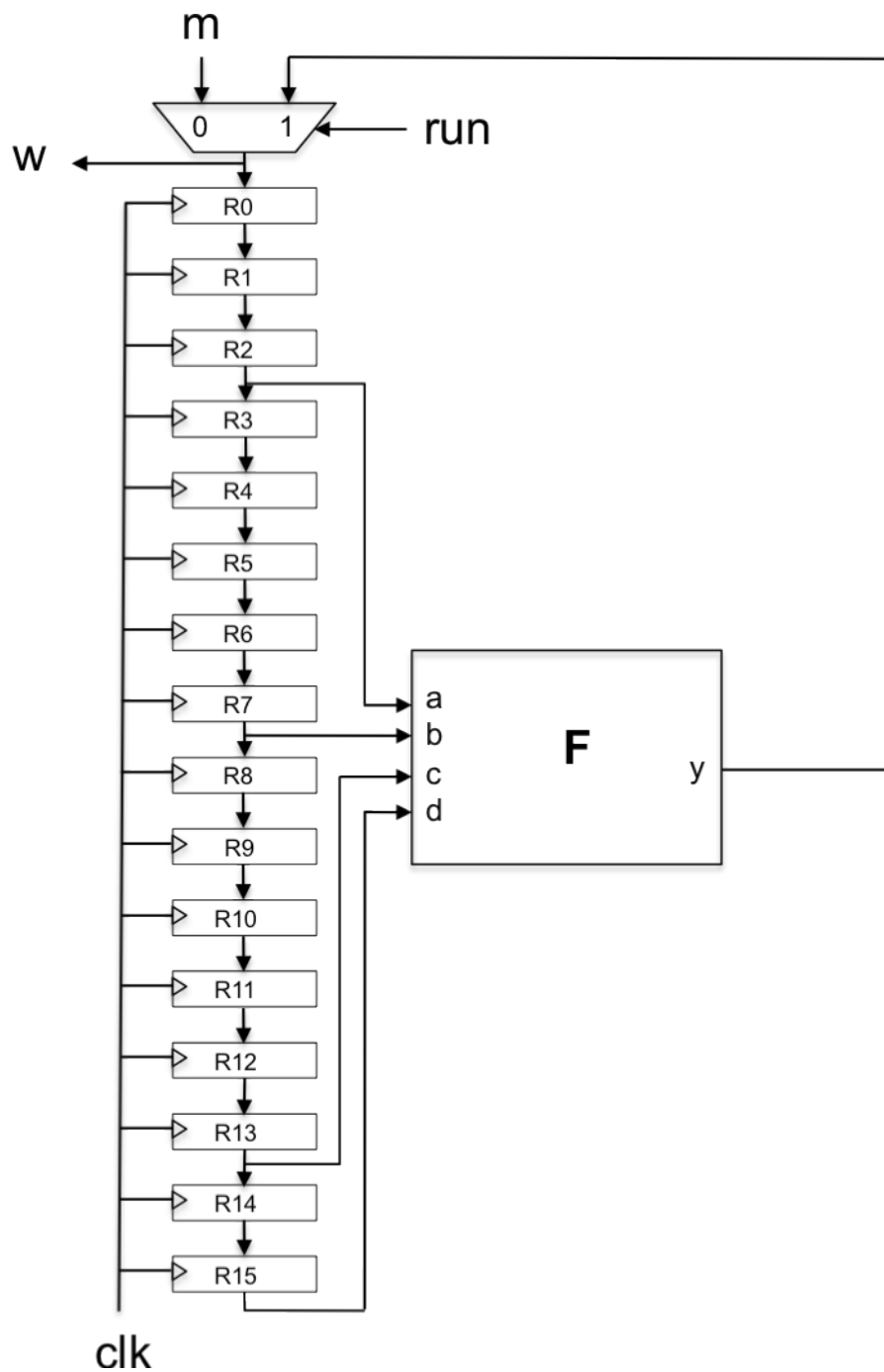

NFSR: Feedback Function F

 

The meaning of components in the above diagrams is given below:

R0-R15: 1-bit registers (D flip-flops),

$\lll k$: rotation by k positions to the left.

For the circuit described using the above block diagrams, perform the following tasks:

Task 1 (40% of points)

- Write entity declaration and architecture of the Top-Level Circuit using **mixed design** style, including: the **dataflow, behavioral, and structural** design styles
Hint: when choosing a design style for a given part of the block diagram, do it in such a way to minimize the total number of lines of VHDL code.
- Write entity declaration and architecture of the Feedback Function F, using **exclusively dataflow** design style.

Task 2 (20% of points)

Write a testbench that performs the following tasks:

1. It initializes NFSR with the hexadecimal value $P=0x00CE$ using only inputs shown in the top-level diagram. This initialization should work properly in the circuit after synthesis and implementation. After initialization, **R0** should contain the least significant bit of **P**, and **R15** should contain the most significant bit of **P**.
2. It collects values of the output **w**, during the first 16 clock cycles after the initialization, in the signal **Q** of the size of 16 bits. At the end of simulation, **Q(0)** should contain the first value of **w** after initialization, **Q(1)** the second value, ..., and **Q(15)** the 16th value after initialization.

Assume clock signal operating at the frequency of 100 MHz.

Task 3 (20% of points)

Based on your knowledge of the internal structure of Spartan 3E FPGAs, and assuming that NFSR is implemented using CLB slices only, perform the following tasks:

1. In the diagrams provided in the answer sheet, please circle any portion of logic that can be implemented using a **single**:
 - Multipurpose Look-up Table – MLUT,
 - Carry&Control Logic – C&C, or
 - Storage Element – SE.
2. Next to each circle write an abbreviation of an appropriate part of Logic Cell, i.e.,
 - MLUT,
 - C&C, or
 - SE.
3. For pieces of logic implemented using MLUTs, write also, after comma, the corresponding mode of operation,
 - ROM,
 - RAM, or
 - SR (shift register).

For example, you can write next to a circle:

SE
MLUT, ROM
MLUT, RAM
C&C.

4. How many logic cells (Logic Cell = $\frac{1}{2}$ of a CLB slice) are needed to implement the entire circuit?

Assume that multiple logic components can be implemented using a single MLUT, but only one part of each Logic Cell (MLUT or SE or C&C) is utilized within each Logic Cell.