


ECE 448

Midterm Exam

Solutions

March 4, 2013

Problem 1 - ASM chart

 


Dataflow VHDL code for the output function computing p, r, and y, as a function of the state S, and the inputs a and b:

```
p <= '1' when (S = S1) or (S = S3) else '0';
```

```
r <= '1' when ((S = S1) and (b = '0')) or ((S = S2) and (b = '1')) or ((S = S3) and (b = '1')) or  
((S = S4) and (b = '0')) else '0';
```

```
y <= '1' when (S = S4) and (b = '0') and (a = '1') else '0';
```

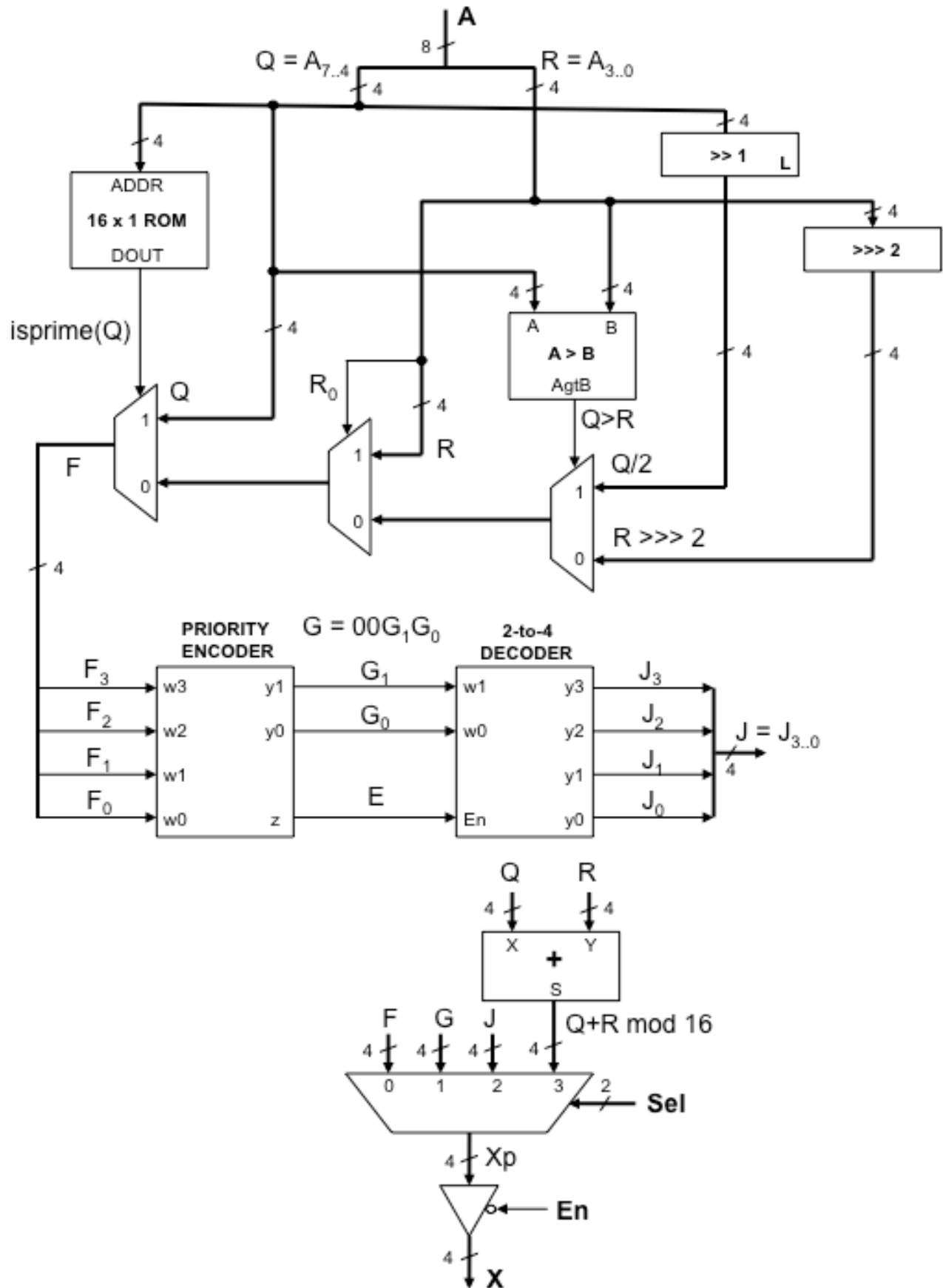Problem 2 – Block Diagram of Combinational Logic



16 x 1 ROM Memory Map

ADDR

0	0
1	0
2	1
3	1
4	0
5	1
6	0
7	1
8	0
9	0
A	0
B	1
C	0
D	1
E	0
F	0

Problem 3 – Mixed Code of Sequential Logic

```
library ieee;
use ieee.std_logic_1164.all;

entity misr is
  generic (C : std_logic_vector(7 downto 0) );
  port (
    -- inputs
    clk   : in    std_logic;
    rst   : in    std_logic;
    en    : in    std_logic;
    D     : in    std_logic_vector (7 downto 0);

    -- outputs
    Q_out: out   std_logic_vector (7 downto 0)
  );
end misr;
```

architecture mixed of misr is

```
-- intermediate signals
signal Q : std_logic_vector (7 downto 0);
signal Q0_replicated : std_logic_vector (7 downto 0);
signal d_ff_in : std_logic_vector (7 downto 0);
```

begin



```
Q0_replicated <= (others => Q(0));
d_ff_in <= D xor ('0' & Q(7 downto 1)) xor (C and Q0_replicated);
```

```
-- D flip flop operation
```

```
D_FF: process (rst, clk)
begin
  if (rst = '1') then
    Q <= (others => '0');
  elsif rising_edge(clk) then
    if(en = '1') then
      Q <= d_ff_in;
    end if;
  end if;
end process;
```

```
Q_out <= Q;
end mixed;
```

Problem 4 – FPGA Resources

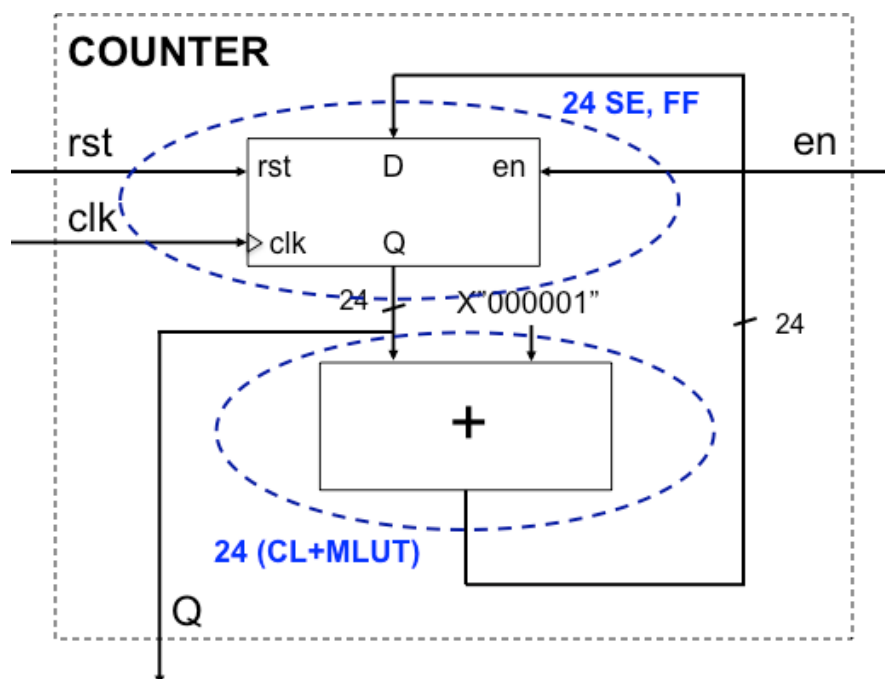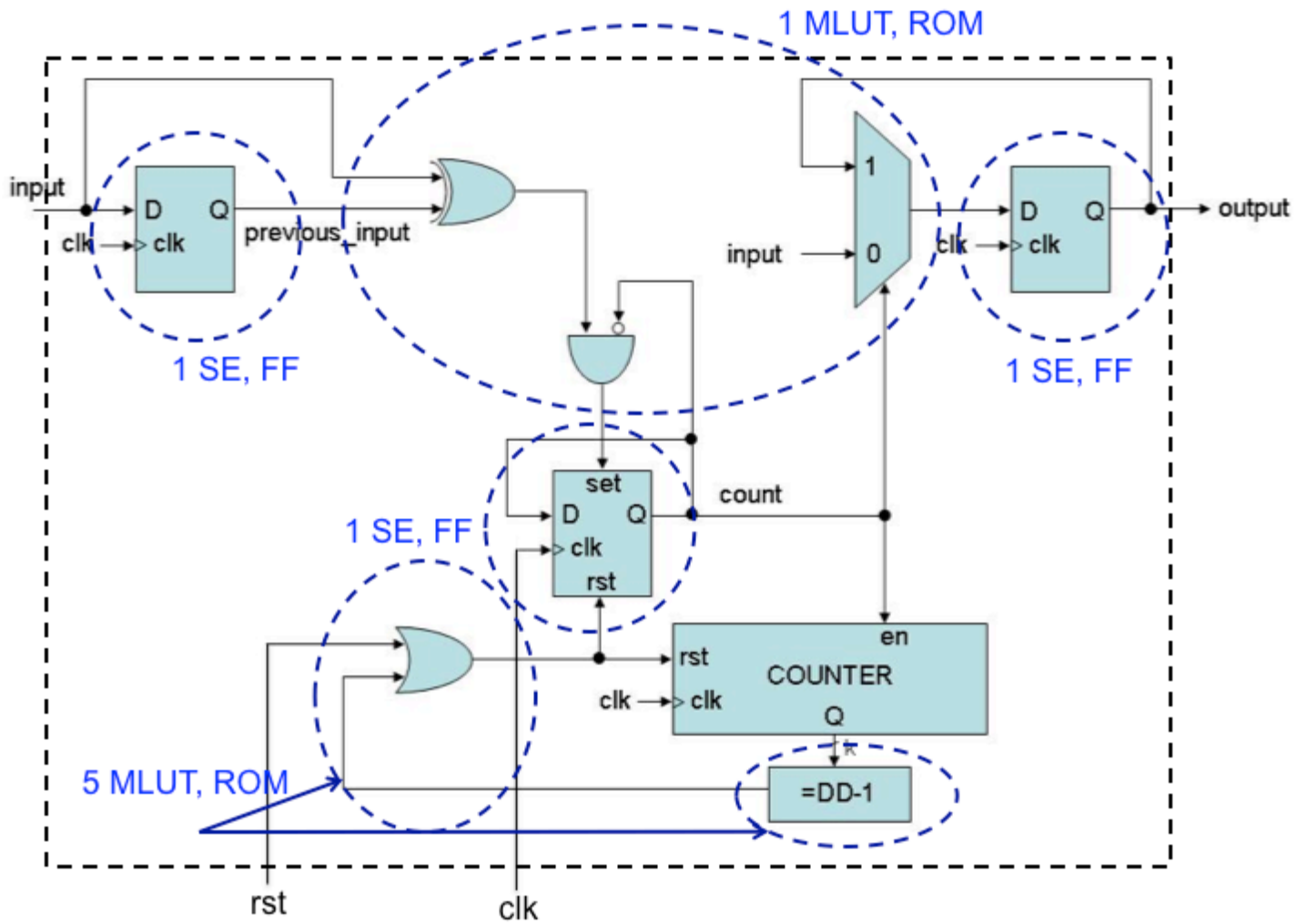

Problem 5 – Simple Testbench

```
library ieee;
use ieee.std_logic_1164.all;

entity debouncer_tb is
end debouncer_tb;

architecture behavioral of debouncer_tb is

    -- inputs
    signal clk : std_logic := '0';
    signal rst : std_logic;
    signal input: std_logic;

    -- outputs
    signal output : std_logic;

    -- constant definitions
    constant clk_period : time := 10 ns;
    constant rst_length : time := 50 ns;
    constant min_before_pulse : time := 100 ns;
    constant pulse_width : time := 500 ns;
    constant bounce_period : time := 40 ns;

begin

    debouncer_inst: entity work.debouncer
        generic map (
            K => 4,
            DD => 15)
        port map (
            clk => clk,
            rst => rst,
            input => input,
            output => output
        );

    clk <= not clk after clk_period/2;

    rst_process: process
    begin
        rst <= '1';
        wait for rst_length;
        rst <= '0';
        wait;
    end process;

end architecture;
```

```
input_process: process
```

```
begin
```

```
    input <= '0';  
    wait for min_before_pulse;  
    wait until falling_edge(clk);
```

```
    for i in 0 to 2 loop  
        input <= '1';  
        wait for bounce_period/2;  
        input <= '0';  
        wait for bounce_period/2;  
    end loop;
```

```
    input <= '1';  
    wait for pulse_width;
```

```
    for i in 0 to 2 loop  
        input <= '0';  
        wait for bounce_period/2;  
        input <= '1';  
        wait for bounce_period/2;  
    end loop;
```

```
    input <= '0';  
    wait;
```

```
end process;
```

```
end behavioral;
```