
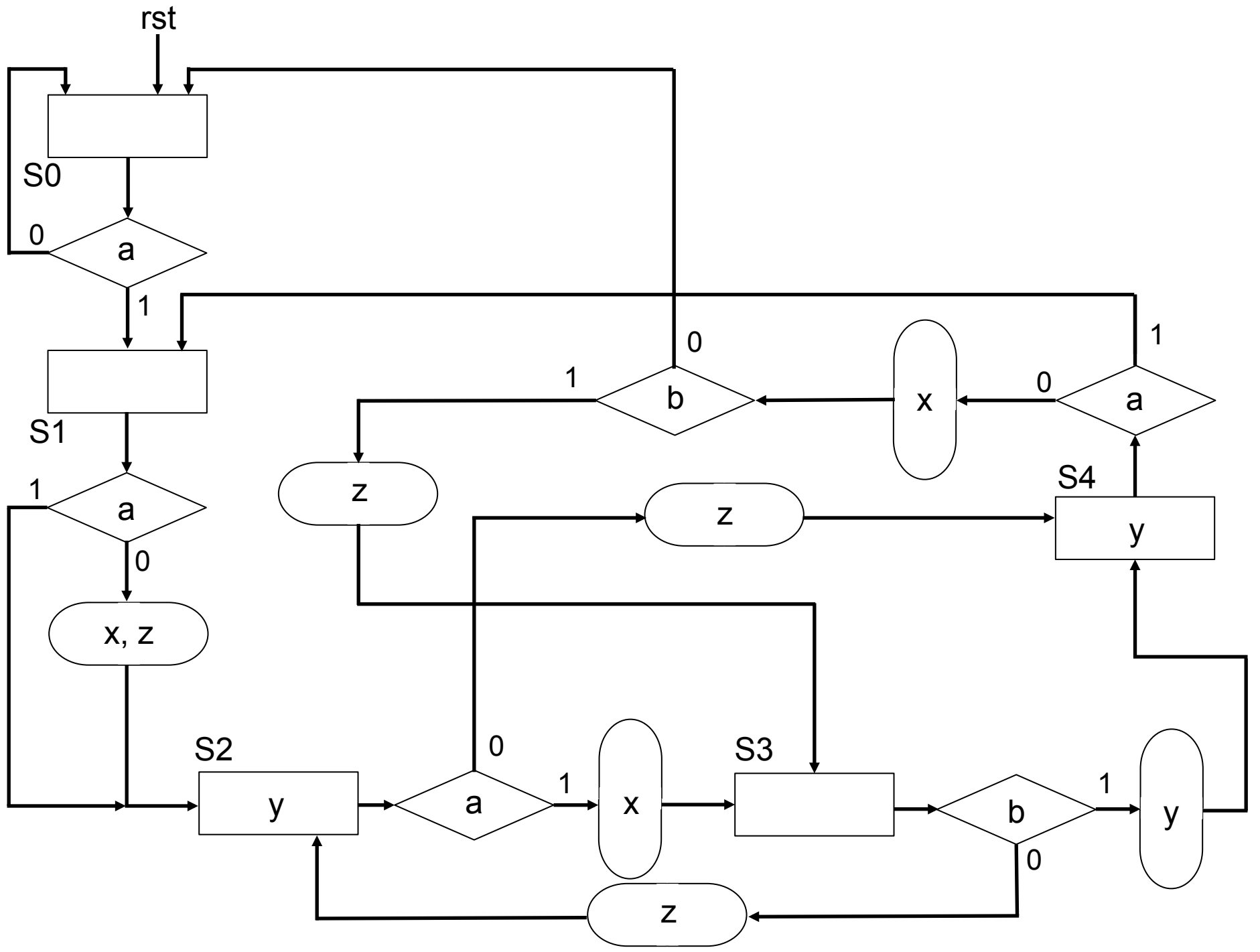



ECE 448
Midterm Exam
Solutions

Problem 1

FSM

 



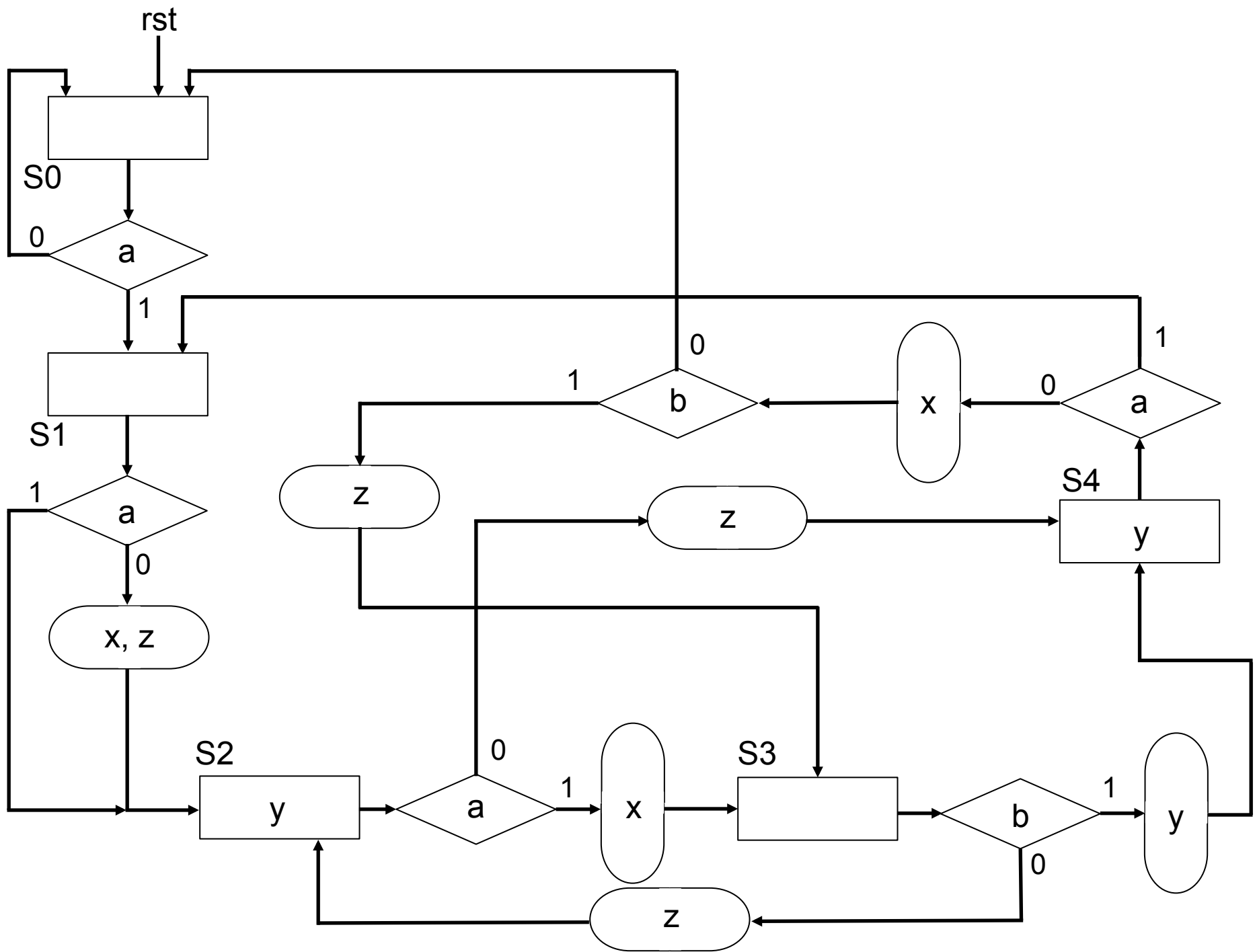

Dataflow representation of the output function


```
x <= '1' WHEN (State = S1 and a='0') OR (State = S2 and a='1') OR  
             (State = S4 and a='0') ELSE  
             '0';
```

```
y <= '1' WHEN (State = S2) OR (State = S3 and b='1') OR ( State = S4 ) ELSE  
             '0';
```

```
z <= '1' WHEN (State = S1 and a='0') OR (State = S2 and a='0') OR  
             (State = S3 and b='0') OR  
             (State = S4 and a='0' and b='1') ELSE  
             '0';
```


Problem 2
Block Diagrams
& Resource Utilization

 A. 3-to-8 decoder (with enable) built of 2-to-4 decoders (with enable) and a minimum number of logic gates




4 LUTs, ROM mode

 
- B. 5-bit priority encoder built of 2-to-1 multiplexers and a minimum number of logic gates (assume that the least significant bit of the input w has the highest priority, and the z output is equal to 1 when at least one input bit is equal to 1).



2 LUTs, ROM mode

 


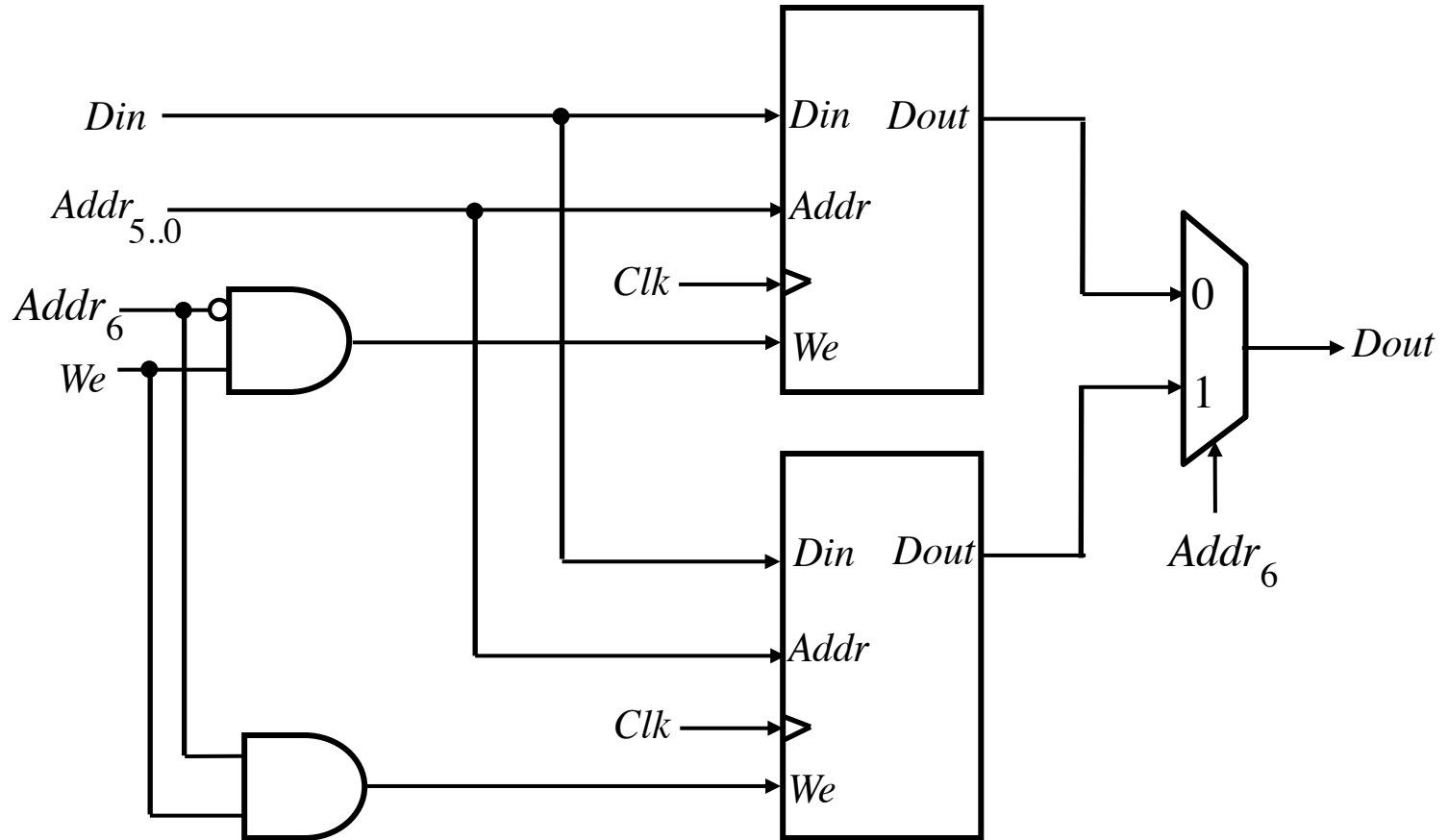C. 128x1 RAM built of two 64x1 RAMs and a minimum number of logic gates




2 LUTs, RAM mode

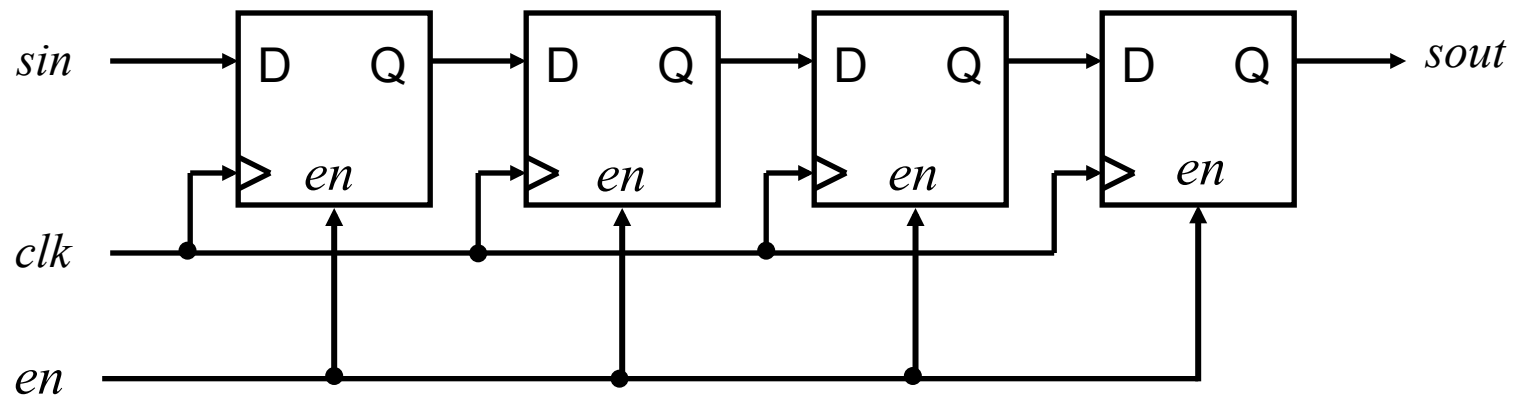- D. 4-bit shift register with the serial input *sin*, enable *en*, clock *clk*, and the serial output *sout*.



1 LUT, SR mode

 Problem 3
Variable Arithmetic
Shifter Right



variable_shifter_right.vhd (1)

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

ENTITY variable_shifter_right IS
    PORT(
        X : IN STD_LOGIC_VECTOR(15 downto 0);
        Y : IN STD_LOGIC_VECTOR(7 downto 0);
        Z : OUT STD_LOGIC_VECTOR(15 downto 0)
    );
END variable_shifter_right;

ARCHITECTURE mixed OF variable_shifter_right IS

TYPE array16 IS ARRAY (0 to 4) OF STD_LOGIC_VECTOR(15 downto 0);

SIGNAL Xi : array16;
SIGNAL Xr : array16;
```

variable_shifter_right.vhd (2)

BEGIN

XI(0) <= X;

G: FOR i IN 0 TO 3 GENERATE

 SHIFT_I: ENTITY work.fixed_shifter_right(dataflow)

 GENERIC MAP (L => 2** i)

 PORT MAP (a => XI(i) ,
 y => Xr(i));

 XI(i+1) <= XI(i) WHEN Y(i) = '0' ELSE Xr(i);

END GENERATE;

Z <= XI(4) WHEN (Y(7) OR Y(6) OR Y(5) OR Y(4)) = '0' ELSE
 (OTHERS => X(15));

END mixed;

fixed_shifter_right.vhd


```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

ENTITY fixed_shifter_right IS
    GENERIC (L : INTEGER := 1);
    PORT(
        a : IN STD_LOGIC_VECTOR(15 downto 0);
        y : OUT STD_LOGIC_VECTOR(15 downto 0)
    );
END fixed_shifter_right;

ARCHITECTURE dataflow OF fixed_shifter_right IS
BEGIN
    y(15-L downto 0) <= a(15 downto L);
    y(15 downto 15-L+1) <= (OTHERS => a(15));
END dataflow;
```

Problem 4

Testbench

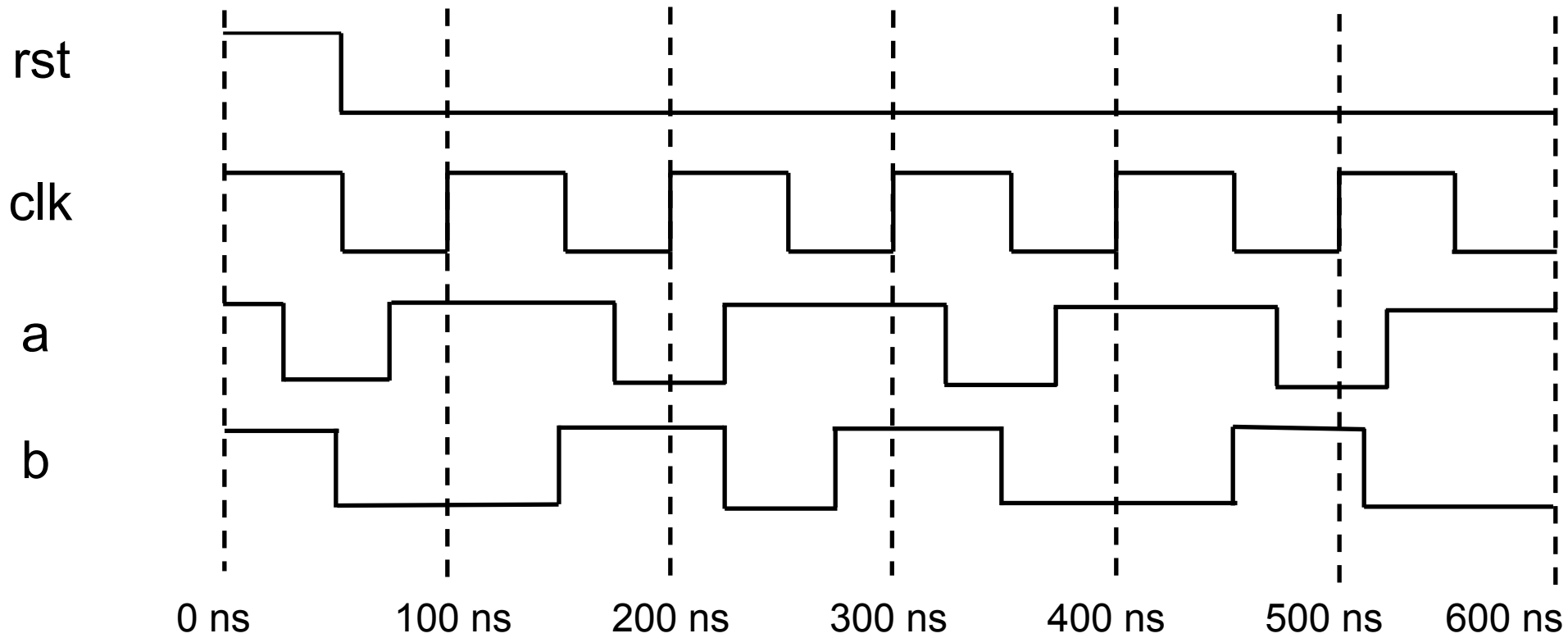

controller_tb.vhd (1)

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

ENTITY controller_tb IS
END controller_tb;

ARCHITECTURE behavioral OF controller_tb IS

SIGNAL clk: STD_LOGIC := '1';
SIGNAL rst: STD_LOGIC := '1';
SIGNAL a : STD_LOGIC := '1';
SIGNAL b : STD_LOGIC := '1';
SIGNAL x, y, z: STD_LOGIC;

CONSTANT clk_period : TIME := 100 ns;
CONSTANT reset_length : TIME := clk_period/2;
```

controller_tb.vhd (2)

BEGIN

UUT: ENTITY work.Controller(mixed)

PORT MAP (clk => clk,

rst => rst,

a => a,

b => b,

x => x,

y => y,

z => z);

clk <= NOT clk AFTER clk_period/2;

PROCESS

BEGIN

WAIT FOR reset_length;

rst <= '0';

WAIT;

END PROCESS;

controller_tb.vhd (3)

```
PROCESS
BEGIN
    WAIT FOR clk_period/4;
    a <= '0';
    WAIT FOR clk_period/2;
    a <= '1';
    WAIT FOR 3*clk_period/4;
END PROCESS;
```

controller_tb.vhd (3)

```
PROCESS
BEGIN
    WAIT FOR clk_period/2;
    b <= '0';
    WAIT FOR clk_period;
    b <= '1';
    WAIT FOR 3*clk_period/4;
    b <= '0';
    WAIT FOR clk_period/2;
    b <= '1';
    WAIT FOR 3*clk_period/4;
    b <= '0';
    WAIT FOR clk_period;
    b <= '1';
    WAIT FOR 5*clk_period/8;
    b <= '0';
    WAIT;
END PROCESS;
END behavioral;
```