


# **Class Midterm Spring 2016**


**Solutions**

# Problem 1


Given the controller, described using the ASM chart shown in Fig. 1:

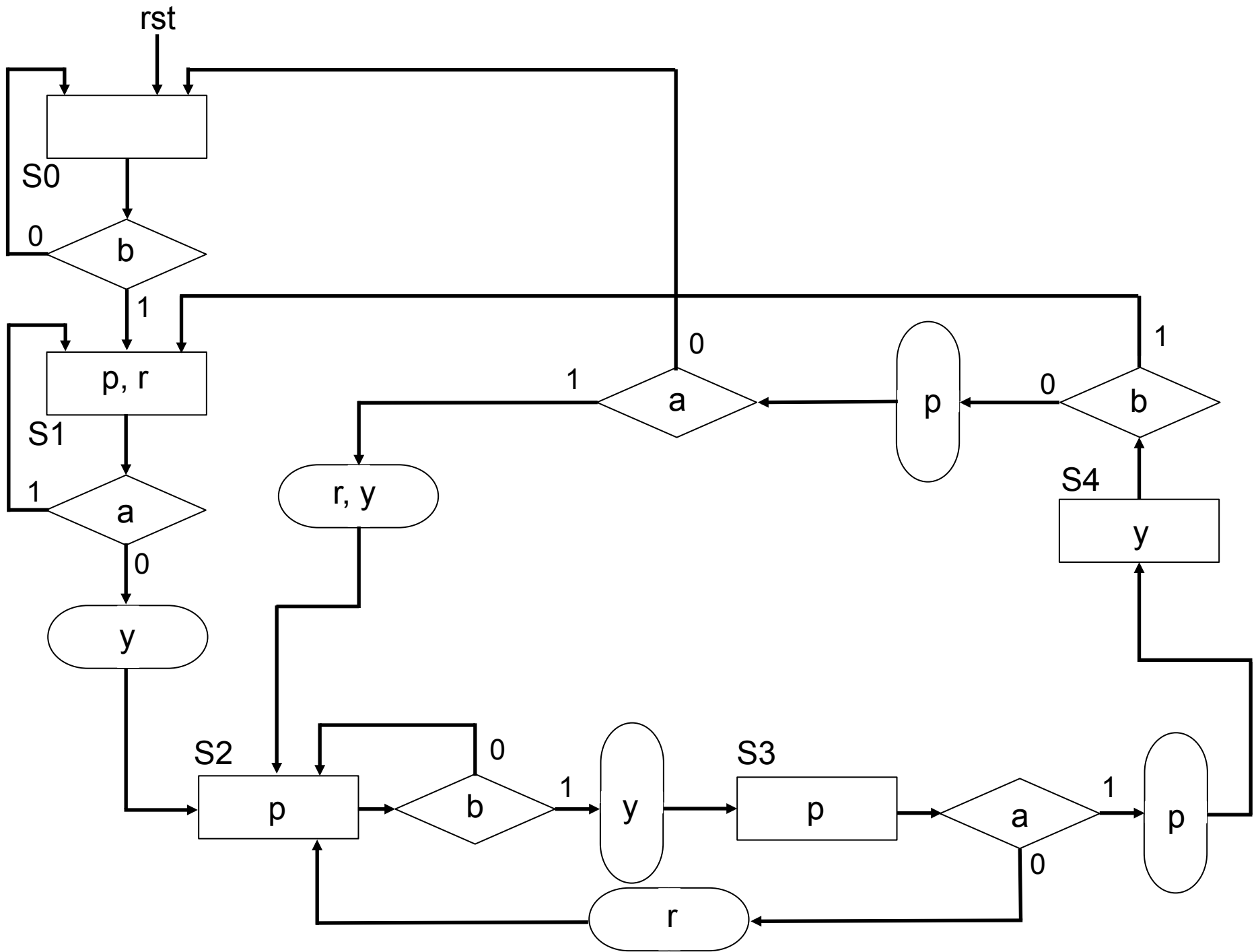- A. supplement timing waveforms provided in the answer sheet with the values of the state  $S$ , and the values of the outputs  $p$ ,  $r$ , and  $y$
- B. write the VHDL behavioral code for the next state function (only), calculating value of the next state  $S$ .




 


# FSM

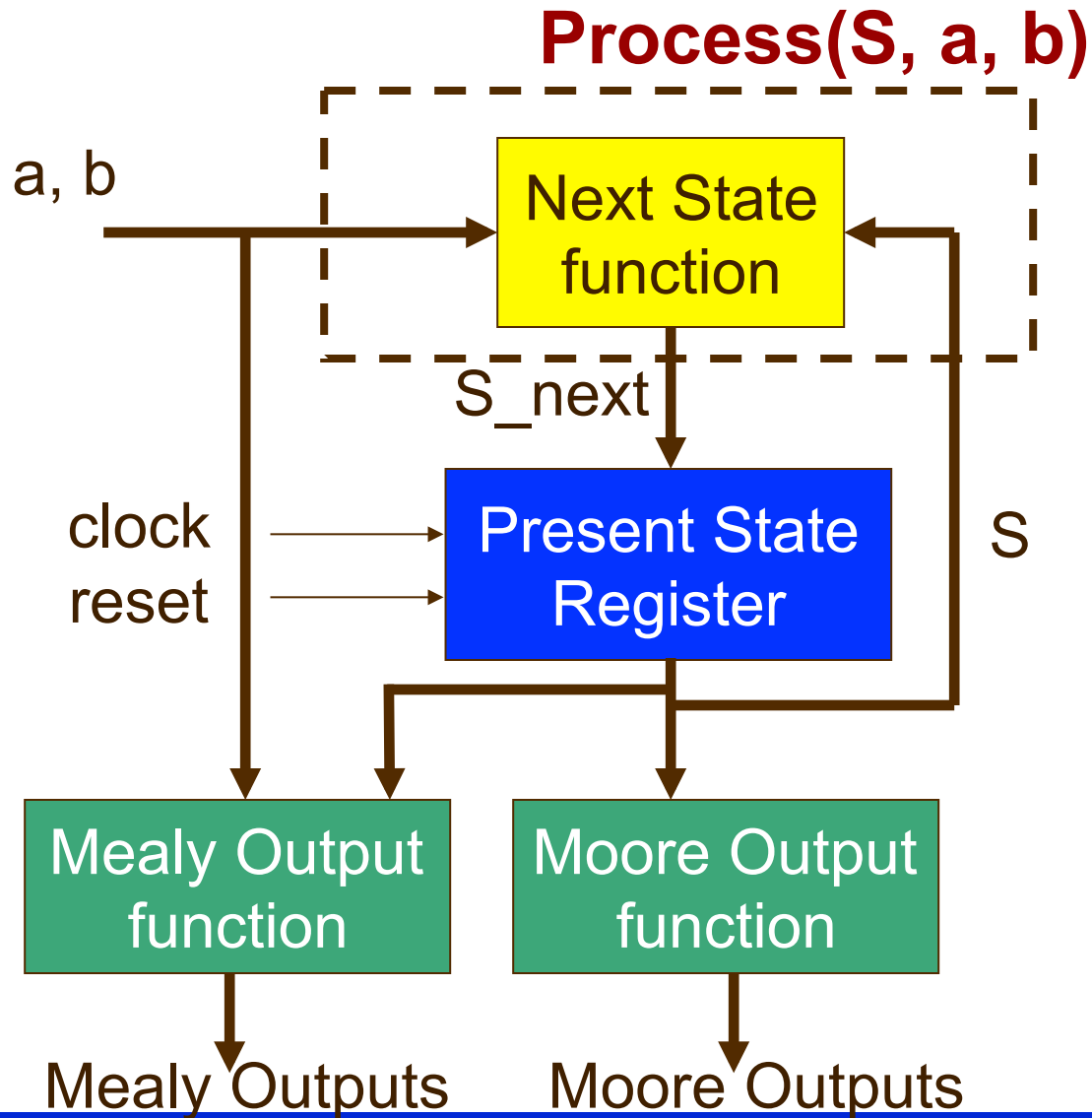

# FSM

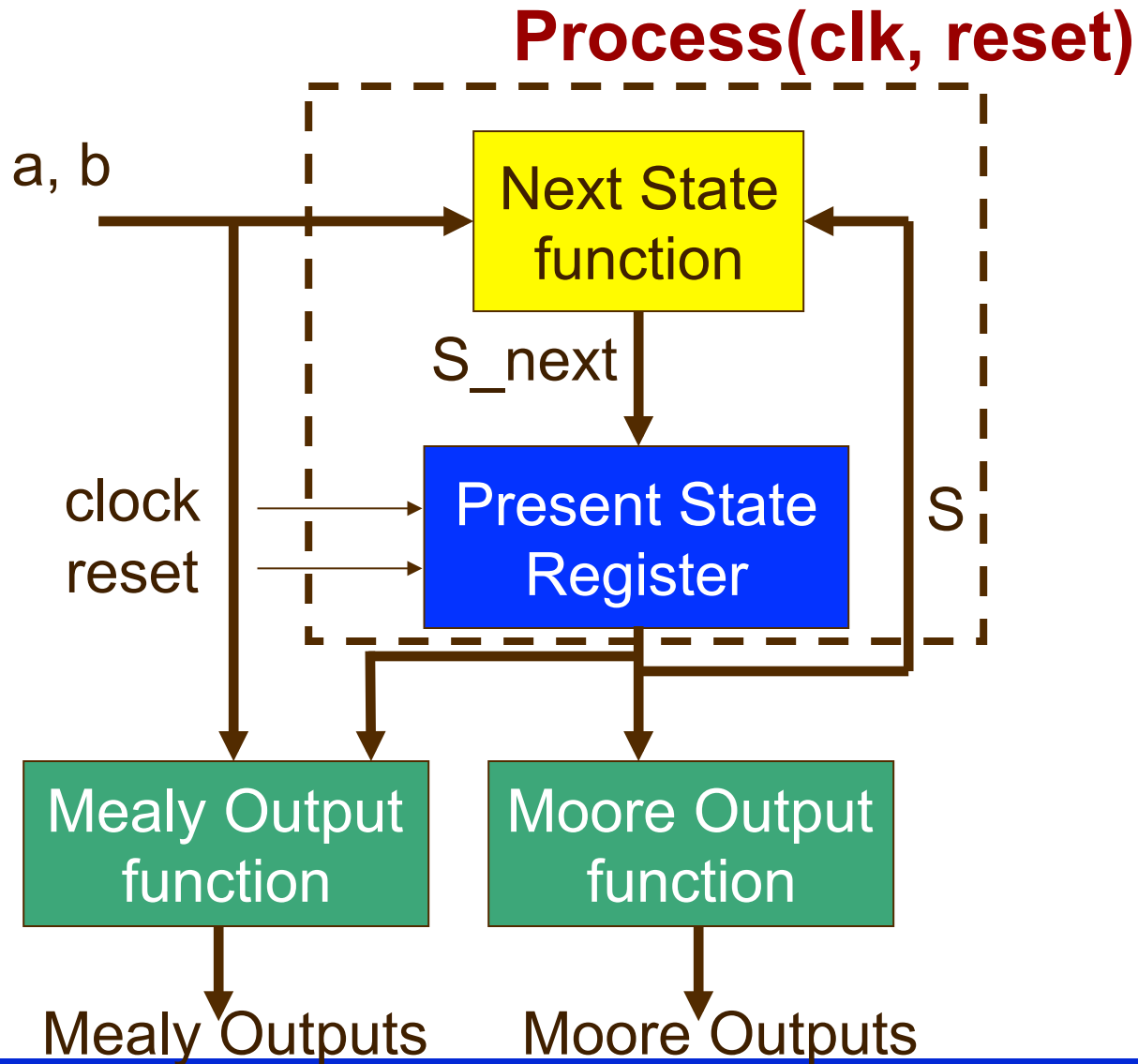

 

# Problem 1 – VHDL code (1)

---

```
PROCESS ( S, a, b )
BEGIN
  S_next <= S;
  CASE S IS
    WHEN S0 =>
      IF b = '1' THEN
        S_next <= S1;
      END IF ;
    WHEN S1 =>
      IF a = '0' THEN
        S_next <= S2;
      END IF;
    WHEN S2 =>
      IF b = '1' THEN
        S_next <= S3;
      END IF;
```




# Problem 1 – VHDL code (2)

---

```
WHEN S3 =>
  IF a = '1' THEN
    S_next <= S4;
  ELSE
    S_next <= S2;
  END IF;
WHEN S4 =>
  IF b = '1' THEN
    S_next <= S1;
  ELSIF a = '1' THEN
    S_next <= S2;
  ELSE
    S_next <= S0;
  END IF;
```

```
END PROCESS ;
```

# Problem 3 – Block diagram

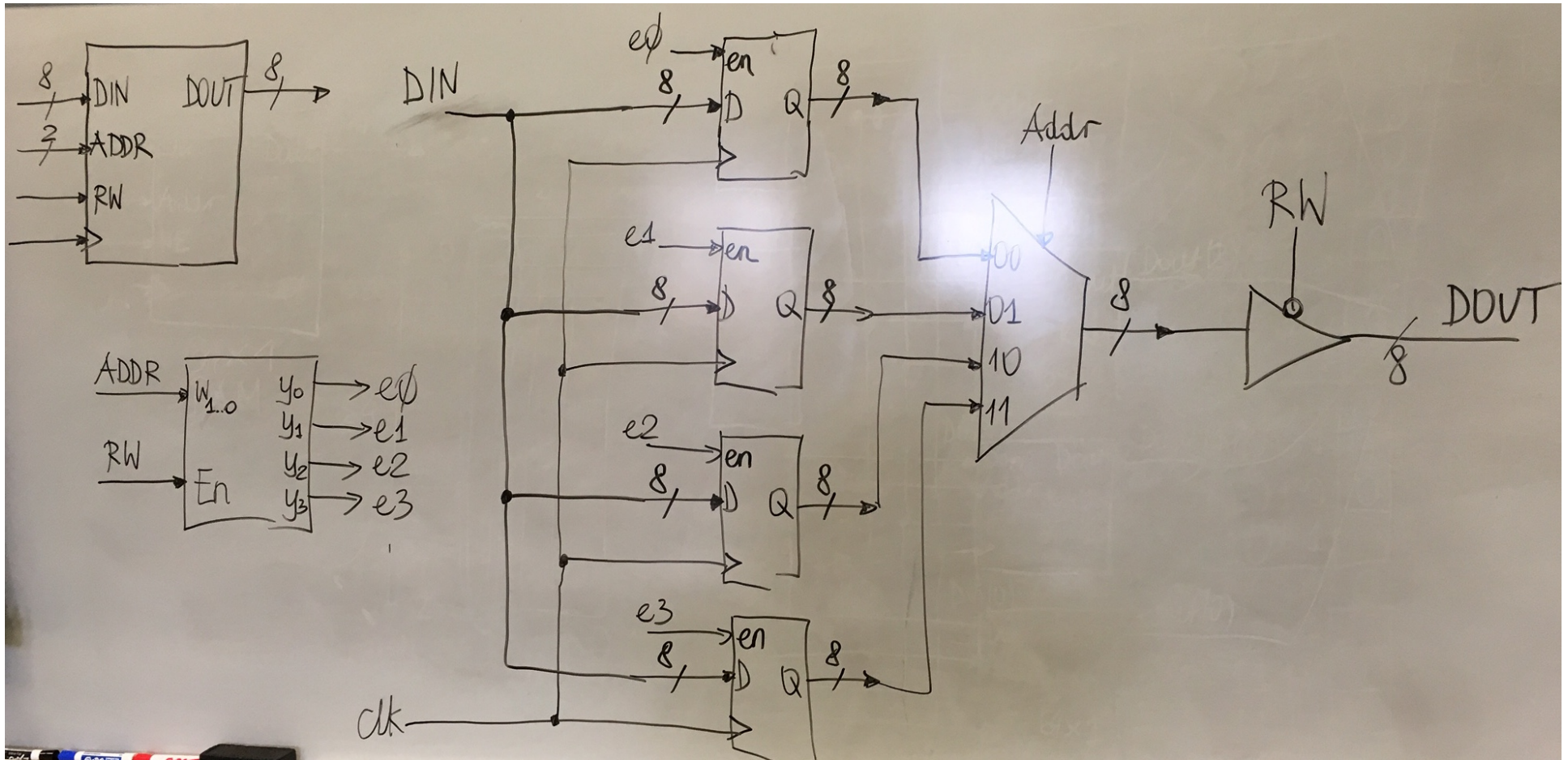

# Problem 3 – VHDL code (1)

---

```
ARCHITECTURE mixed OF problem_3 IS
```

```
SIGNAL Q0, Q1, Q2, Q3, mux_out : STD_LOGIC_VECTOR(7 DOWNTO 0);  
SIGNAL en : STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL enw : STD_LOGIC_VECTOR(2 DOWNTO 0);
```

```
BEGIN
```

```
enw <= RW & ADDR ;  
WITH enw SELECT  
    en <= "0001" WHEN "100",  
         "0010" WHEN "101",  
         "0100" WHEN "110",  
         "1000" WHEN "111",  
         "0000" WHEN OTHERS ;
```

```
WITH ADDR SELECT  
    mux_out <= Q0 WHEN "00",  
              Q1 WHEN "01",  
              Q2 WHEN "10",  
              Q3 WHEN OTHERS;
```

## Problem 3 – VHDL code (2)

---

```
DOUT <= mux_out WHEN RW='0' ELSE (OTHERS => 'Z');
```

```
PROCESS(CLK)
  IF rising_edge(CLK) THEN
    IF en(0) THEN
      Q0 <= DIN;
    END IF;
    IF en(1) THEN
      Q1 <= DIN;
    END IF;
    IF en(2) THEN
      Q2 <= DIN;
    END IF;
    IF en(3) THEN
      Q3 <= DIN;
    END IF;
  END IF;
END PROCESS;

END mixed;
```

# Problem 3 – VHDL code with for-generate (1)

---

```
ARCHITECTURE mixed OF problem_3 IS
```

```
TYPE ARRAY8 IS ARRAY 0 TO 3 OF STD_LOGIC_VECTOR(7 DOWNT0 0);
```

```
SIGNAL Q: ARRAY8;
```

```
SIGNAL mux_out : STD_LOGIC_VECTOR(7 DOWNT0 0);
```

```
SIGNAL en : STD_LOGIC_VECTOR(3 DOWNT0 0);
```

```
SIGNAL enw : STD_LOGIC_VECTOR(2 DOWNT0 0);
```

```
BEGIN
```

```
enw <= RW & ADDR ;
```

```
WITH enw SELECT
```

```
    en <= "0001" WHEN "100",  
          "0010" WHEN "101",  
          "0100" WHEN "110",  
          "1000" WHEN "111",  
          "0000" WHEN OTHERS ;
```

## Problem 3 – VHDL code with for-generate (2)

---

```
WITH ADDR SELECT
    mux_out <= Q(0) WHEN "00",
              Q(1) WHEN "01",
              Q(2) WHEN "10",
              Q(3) WHEN OTHERS;

DOUT <= mux_out WHEN RW='0' ELSE (OTHERS => 'Z');

FOR i IN 0 TO 3 GENERATE
    PROCESS(CLK)
        IF rising_edge(CLK) THEN
            IF en(i) THEN
                Q(i) <= DIN;
            END IF;
        END IF;
    END PROCESS;
END GENERATE;

END mixed;
```

## Problem 4 (1)

---

Write a complete simple testbench capable of verifying the operation of MISR (Multiple Input Signature Register) shown in Fig. 2.

The testbench should instantiate MISR, using the VHDL-93 convention, with the value of the generic C equal to X"B8". Assume that the name of the MISR entity is MISR, and the name of its architecture is behavioral.

## Problem 4 (2)

---

The test should consist of

1. resetting MISR
2. applying 128 inputs D, varying between X"00" and X"FE" with the step of 2 (i.e., values X"00", X"02", X"04", ..., X"FE"), one per clock cycle, with the input en active
3. deactivating en for 10 clock cycles
4. applying 128 inputs D, varying between X"01" and X"FF" with the step of 2 (i.e., values X"01", X"03", X"05", ..., X"FF"), one per clock cycle, with the input en active.
5. deactivating en.



## Problem 4 (3)


---

Assume that all external inputs should be changed on the falling edges of the clock.

After step 5, all inputs (other than clk) should remain stable (i.e., keep their last value) till the end of simulation.

# Block Diagram

---

 

# Problem 4 – Testbench (1)

---

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

USE ieee.std_logic_unsigned.all;

ENTITY MISR_tb IS
END MISR_tb;

ARCHITECTURE behavioral OF MISR_tb IS

SIGNAL clk : STD_LOGIC := '0';
SIGNAL rst : STD_LOGIC := '1';
SIGNAL en : STD_LOGIC := '0';
SIGNAL D, Q : STD_LOGIC_VECTOR(7 downto 0);

CONSTANT clk_period := 10ns;
CONSTANT rst_width := clk_period;
```

# Problem 4 – Testbench (2)

---

```
BEGIN
```

```
    DUT: ENTITY work.MISR(behavioral)
        GENERIC MAP (C => XB8")
        PORT MAP (
            clk => clk,
            rst => rst,
            en => en,
            D => D,
            Q => Q);
);
```

```
clk <= not clk after clk2_period/2;
```

## Problem 4 - Testbench (3)

---

```
main: PROCESS
  D <= X"00";
  WAIT for rst_width;
  rst <= '0';
  en <= '1';
  FOR i IN 0 TO 127 LOOP
    WAIT for clk_period;
    D <= D + 2;
  END LOOP;
  en <= '0';
  WAIT FOR 10*clk_period;
  en <= '1';
  D <= X"01";
  FOR i IN 0 TO 127 LOOP
    WAIT for clk_period;
    D <= D + 2;
  END LOOP;
  en <= '0';
  WAIT;
END PROCESS;
END behavioral;
```