

**ECE 448**  
**Midterm Exam – Solutions for Group 2**  
**Monday, March 2, 2020**

**Problem 1 (15 points)**

Perform the following tasks for

**a combinational Variable Logical Shifter Right,**

with the block diagram shown in Fig. 1.

A. Fill in the blanks in the code of this component given on the next page.

B. Draw a symbol of this component with the correct

- number
- direction, and
- widths

of ALL inputs and outputs.

Name each input and output, matching the VHDL code on the next page.

 


Fig. 1: Block diagram of a combinational Variable Logical Shifter Right

## Answer A:

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

ENTITY fixed_shifter_right IS
    GENERIC(L : INTEGER := 1);
    PORT(
        a : IN STD_LOGIC_VECTOR(7 downto 0);
        y : OUT STD_LOGIC_VECTOR(7 downto 0)
    );
END fixed_shifter_right;

ARCHITECTURE dataflow OF fixed_shifter_right IS
BEGIN
    y(7-L downto 0) <= a(7 downto L);
    y(7 downto 7-L+1) <= OTHERS => '0';
END dataflow;

library IEEE;
use IEEE.STD_LOGIC_1164.all;

ENTITY variable_shifter_right IS
    PORT(
        Xin : IN STD_LOGIC_VECTOR(7 downto 0);
        Yin : IN STD_LOGIC_VECTOR(5 downto 0);
        Zout : OUT STD_LOGIC_VECTOR(7 downto 0)
    );
END variable_shifter_right;

ARCHITECTURE mixed OF variable_shifter_right IS

TYPE array8 IS ARRAY (0 to 3) OF STD_LOGIC_VECTOR(7 DOWNTO 0);

SIGNAL X : array8;
SIGNAL Y : array8;

BEGIN
    X(0) <= Xin;
    G: FOR i IN 0 TO 2 GENERATE

        SHIFT_I: ENTITY work.fixed_shifter_right(dataflow)
            GENERIC MAP (L => 2**i)
            PORT MAP ( a => X(i),
                    y => Y(i));


        X(i+1) <= Y(i) WHEN Yin(1)='1' ELSE X(i);

    END GENERATE;
END mixed;
```

```
Zout <= OTHERS => '0' WHEN (Yin(5) OR Yin(4) OR Yin(3)) = '1'
      ELSE X(3);
```

END mixed;


**Answer B:**

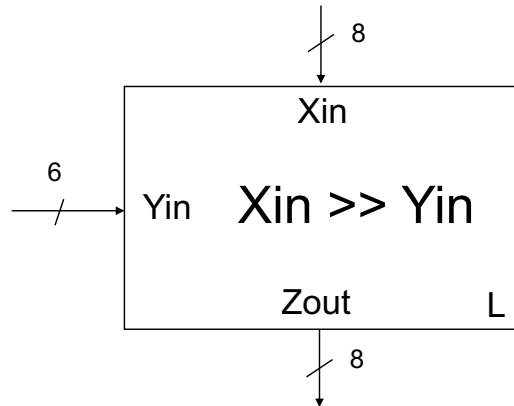
 
## Problem 2


Assuming the controller described using the given below ASM chart:

- Supplement timing waveforms given on the next page with the values of the **state S**, and the values of the **outputs p, r, and s**.
- Fill in the blanks in the fragment of the code of this component given on the next page.



**Answer A:**

 **Be careful regarding the initial value of the state S after reset!**



**Answer B:**

```
ARCHITECTURE behavioral of Controller IS
TYPE state IS (S0, S1, S2, S3, S4);
SIGNAL state_reg, state_next: state;
```

```
BEGIN
P1: PROCESS (clk, rst)
BEGIN
    IF (rst = '1') THEN
        state_reg <= S3;
    ELSIF rising_edge(clk) THEN
        state_reg <= state_next;
    END IF;
END PROCESS;
```

```
Next_State_Output:
PROCESS (state_reg, x, y)
BEGIN
    state_next <= state_reg;
    p <= '0';
    r <= '0';
    s <= '0';

    CASE state_reg IS

        WHEN S2 =>
            p <='1';
            if x='1' then
                r <='1';
                state_next <= S3;
            else
                s <='1';
                state_next <= S0;
            end if;

        WHEN S3 =>
            if y='1' then
                s <='1';
                state_next <= S2;
            else
                r <='1';
                state_next <= S4;
            end if;
```

**Please provide the code only for the cases when state\_reg = S2 and state\_reg = S3.**


### Problem 3

Perform the following tasks for a component

**taking a 4-bit input A of the type `std_logic_vector`,  
adding to it a constant, given by the generic C of the type `natural` (in the  
range 0 to 15), and returning the sum S of the type `std_logic_vector` and the  
carry out Cout of the type `std_logic`.**

- A. Draw a symbol of this component with the correct
- number
  - direction, and
  - widths
- of ALL inputs and outputs.  
Name each input and output.
- B. Write the full synthesizable code of this design entity, including entity declaration and architecture body, using the package `numeric_std`.
- C. **(bonus)** Draw an internal block diagram of this component, composed of medium logic components and/or basic logic gates for the case of  $C=6$ .

**Answer A:**

 

**Answer B:**

You can use the following table of overloaded operators in the IEEE `numeric_std` package

overloaded operator	description	data type of operand a	data type of operand b	data type of result
<code>abs a</code>	absolute value	signed		signed
<code>- a</code>	negation			
<code>a * b</code>		unsigned	unsigned, natural	unsigned
<code>a / b</code>				
<code>a mod b</code>	arithmetic operation	unsigned, natural	unsigned	unsigned
<code>a rem b</code>		signed	signed, integer	signed
<code>a + b</code>		signed, integer	signed	signed
<code>a - b</code>				
<code>a = b</code>				
<code>a /= b</code>		unsigned	unsigned, natural	boolean
<code>a &lt; b</code>	relational operation	unsigned, natural	unsigned	boolean
<code>a &lt;= b</code>		signed	signed, integer	boolean
<code>a &gt; b</code>		signed, integer	signed	boolean
<code>a &gt;= b</code>				

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;


ENTITY plusC IS
    GENERIC ( C : NATURAL RANGE 0 TO 15 := 6 ) ;
    PORT ( A : IN STD_LOGIC_VECTOR(3 downto 0);
          S : OUT STD_LOGIC_VECTOR(3 downto 0);
          Cout : OUT STD_LOGIC);
END plusC;

ARCHITECTURE dataflow OF plusC IS
    SIGNAL Sum : UNSIGNED(4 downto 0);
BEGIN
    Sum <= unsigned('0' & A) + C;
    S <= std_logic_vector(Sum(3 downto 0));
    Cout <= Sum(4);
END dataflow;

```

**Answer C:**

**Derivation:**

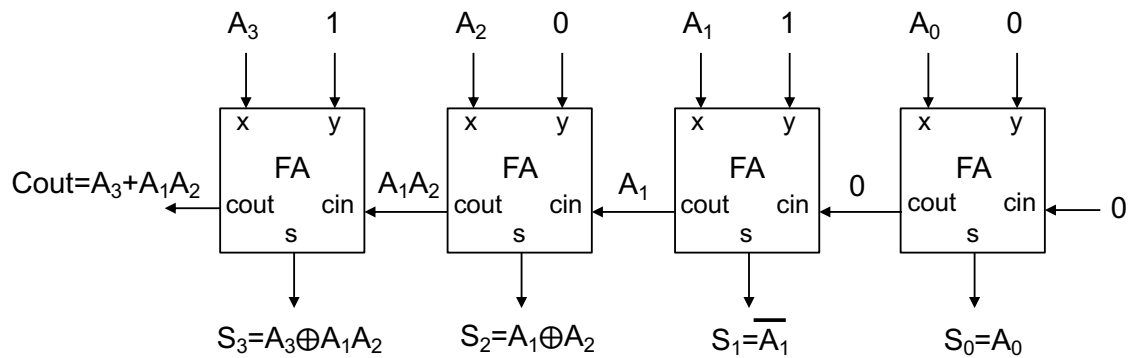

**Final Optimized Circuit:**

