 


**ECE 448  
Spring 2021  
Midterm Exam for the Lecture  
Solutions**

**Problem 1**

**A. Symbol of a 1-digit BCD adder**



**B. RTL code a 1-digit BCD adder using the numeric\_std package**

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;

ENTITY BCD_adder IS
    PORT(A, B : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
         Cin : IN STD_LOGIC;
         S : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
         Cout : OUT STD_LOGIC);
END BCD_adder;

ARCHITECTURE dataflow OF BCD_adder IS

    SIGNAL usum, usum_m10 : UNSIGNED(4 downto 0);
    SIGNAL uCin : UNSIGNED(0 downto 0);

BEGIN

    uCin(0) <= Cin;
    usum <= UNSIGNED('0' & A) + UNSIGNED(B) + uCin;
    usum_m10 <= usum - 10;
    S <= STD_LOGIC_VECTOR(usum(3 DOWNTO 0)) WHEN usum < 10 ELSE
        STD_LOGIC_VECTOR(usum_m10(3 DOWNTO 0));
    Cout <= '1' WHEN usum >= 10 ELSE
        '0';

END dataflow;
```

### C. Structural description of a 3-digit BCD adder using the VHDL-93 convention for entity instantiation

#### Version 1, using FOR-GENERATE:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY Three_digit_BCD_adder IS
    PORT(A, B : IN STD_LOGIC_VECTOR(11 DOWNTO 0);
          Cin : IN STD_LOGIC;
          S : OUT STD_LOGIC_VECTOR(11 DOWNTO 0);
          Cout : OUT STD_LOGIC);
END Three_digit_BCD_adder;

ARCHITECTURE structural OF Three_digit_BCD_adder IS

    SIGNAL Carry : STD_LOGIC_VECTOR(3 DOWNTO 0);

BEGIN

    Carry(0) <= Cin;
    G: FOR i IN 0 TO 2 GENERATE
        BCD: ENTITY work.BCD_adder(dataflow)
            PORT MAP(
                A => A(4*i+3 DOWNTO 4*i),
                B => B(4*i+3 DOWNTO 4*i),
                Cin => Carry(i),
                S => S(4*i+3 DOWNTO 4*i),
                Cout => Carry(i+1)
            );
    END GENERATE;
    Cout <= Carry(3);

END structural;
```

#### Version 2, without using FOR-GENERATE:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY Three_digit_BCD_adder IS
    PORT(A, B : IN STD_LOGIC_VECTOR(11 DOWNTO 0);
          Cin : IN STD_LOGIC;
          S : OUT STD_LOGIC_VECTOR(11 DOWNTO 0);
          Cout : OUT STD_LOGIC);
END Three_digit_BCD_adder;
```

ARCHITECTURE structural OF Three\_digit\_BCD\_adder IS

```
SIGNAL Carry : STD_LOGIC_VECTOR(2 DOWNTO 1);
```

BEGIN

```
BCD_0: ENTITY work.BCD_adder(dataflow)
```

```
PORT MAP(
```

```
  A => A(3 DOWNTO 0),
```

```
  B => B(3 DOWNTO 0),
```

```
  Cin => Cin,
```

```
  S => S(3 DOWNTO 0),
```

```
  Cout => Carry(1)
```

```
);
```

```
BCD_1: ENTITY work.BCD_adder(dataflow)
```

```
PORT MAP(
```

```
  A => A(7 DOWNTO 4),
```

```
  B => B(7 DOWNTO 4),
```

```
  Cin => Carry(1),
```

```
  S => S(7 DOWNTO 4),
```

```
  Cout => Carry(2)
```

```
);
```

```
BCD_2: ENTITY work.BCD_adder(dataflow)
```

```
PORT MAP(
```

```
  A => A(11 DOWNTO 8),
```

```
  B => B(11 DOWNTO 8),
```

```
  Cin => Carry(2),
```

```
  S => S(11 DOWNTO 8),
```


```
  Cout => Cout
```

```
);
```


END structural;

## Problem 2


### C. 2-to-4 Decoder with Enable

 

 **B. Priority Encoder (with the most significant bit of input having the highest priority)**



**C. 4-bit Up-Counter with Asynchronous Reset Active Low**

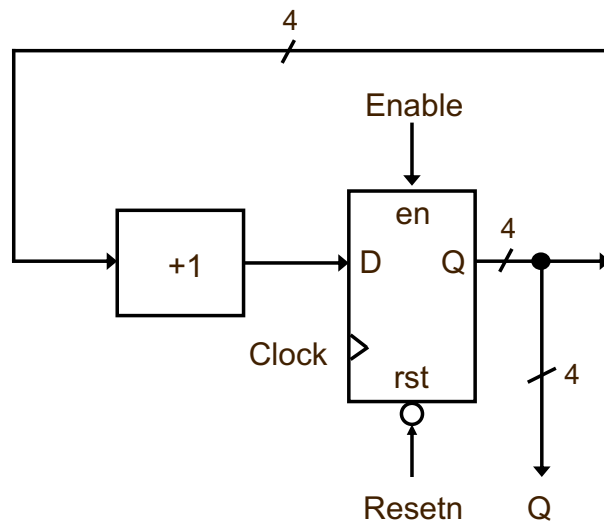

**Problem 3**

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY P3_Controller IS
    PORT ( clk, reset, go, gt1, gt2, gt3, zi : IN STD_LOGIC;
          esum, enc, en3, en2, en1, s3, s2, done : OUT STD_LOGIC);
END P3_Controller;

```

ARCHITECTURE behavioral OF P3\_Controller IS

TYPE state IS (Waiting, Calculating, afterloop);  
SIGNAL state\_reg, state\_next : state;

BEGIN

PROCESS(reset, clk)

BEGIN

IF reset = '1' THEN  
state\_reg <= Waiting;  
ELSIF rising\_edge(clk) THEN  
state\_reg <= state\_next;  
END IF;

END PROCESS;

PROCESS(state\_reg, go, gt1, gt2, gt3, zi)

BEGIN

state\_next <= state\_reg;  
esum <= '0';  
enc <= '0';  
en3 <= '0';  
en2 <= '0';  
en1 <= '0';  
s3 <= '0';  
s2 <= '0';  
done <= '0';

CASE state\_reg IS

WHEN Waiting =>

IF go = '1' THEN  
state\_next <= Calculating;  
END IF;

WHEN Calculating =>

esum <= '1';  
IF gt1 = '1' THEN  
s3 <= '0';  
en3 <= '1';  
s2 <= '0';  
en2 <= '1';  
en1 <= '1';

ELSIF gt2 = '1' THEN

s3 <= '0';  
en3 <= '1';  
s2 <= '1';  
en2 <= '1';

ELSIF gt3 = '1' THEN

s3 <= '1';  
en3 <= '1';

END IF;

```
    IF zi = '1' THEN
        state_next <= afterloop;
    ELSE
        enc <= '1';
        state_next <= Calculating;
    END IF;
    WHEN afterloop =>
        done <= '1';
        state_next <= afterloop;
    END CASE;
END PROCESS;

END Behavioral;
```