

ECE 448

Lecture 10

Finite State Machines

State Diagrams,
Algorithmic State Machine (ASM) Charts,
and VHDL Code

Required reading

- P. Chu, *FPGA Prototyping by VHDL Examples*
Chapter 5, FSM

Recommended reading

- S. Brown and Z. Vranesic,
Fundamentals of Digital Logic with VHDL Design
Chapter 8, Synchronous Sequential Circuits
Sections 8.1-8.5
Section 8.10, Algorithmic State Machine (ASM)
Charts

**Datapath
vs.
Controller**




High Performance

CoolClock

Low Power

PowerPac

Structure of a Typical Digital System

 

Controller (Control Unit)

- Controls data movement in the Datapath by switching multiplexers and enabling or disabling resources
 - enable signals for registers
 - load signals for counters and shift registers
 - select signals for muxes
- Provides signals to activate various processing tasks in the Datapath
- Determines the sequence of operations performed by the Datapath
- Follows Some 'Program' or Schedule


Programmable vs. Non-Programmable Controller

- Controller can be programmable or non-programmable
- Programmable
 - Has a program counter which points to the next instruction
 - Instructions are held in a RAM or ROM
 - Microprocessor is an example of a programmable controller
- Non-Programmable
 - Once designed, implements the same functionality
 - Another term is a “hardwired state machine,” or “hardwired FSM,” or “hardwired instructions”
 - **In this course we will be focusing on non-programmable controllers.**

Finite State Machines

- Controllers can be described as Finite State Machines (FSMs)
- Finite State Machines can be represented using
 - **State Diagrams and State Tables** - suitable for simple controllers with a relatively few inputs and outputs
 - **Algorithmic State Machine (ASM) Charts** - suitable for complex controllers with a large number of inputs and outputs
- All of these descriptions can be easily translated to the corresponding synthesizable VHDL code

Hardware Design with RTL VHDL

 

Steps of the Design Process Introduced in Class Today

1. Text description
2. Interface
3. Pseudocode (optional)
4. Block diagram of the Datapath
5. Interface divided into the Datapath and Controller
- 6. State diagram or ASM chart of the Controller**
- 7. RTL VHDL code of the Datapath, Controller, and Top-level Unit**
8. Testbench for the Datapath, Controller, and Top-Level Unit
9. Functional simulation and debugging
10. Synthesis and post-synthesis simulation
11. Implementation and timing simulation
12. Experimental testing using FPGA board

Finite State Machines Refresher



High Performance

CoolClock

Low Power

CoolGate




Finite State Machines (FSMs)

- An FSM is used to model a system that transits among a finite number of internal states. The transitions depend on the current state and external input.
- The main application of an FSM is to act as the controller of a medium to large digital system
- Design of FSMs involves
 - Defining states
 - Defining the next-state and output functions
 - Optimization / minimization
- Manual optimization/minimization is practical for small FSMs only


Moore FSM

- output is a function of the state only

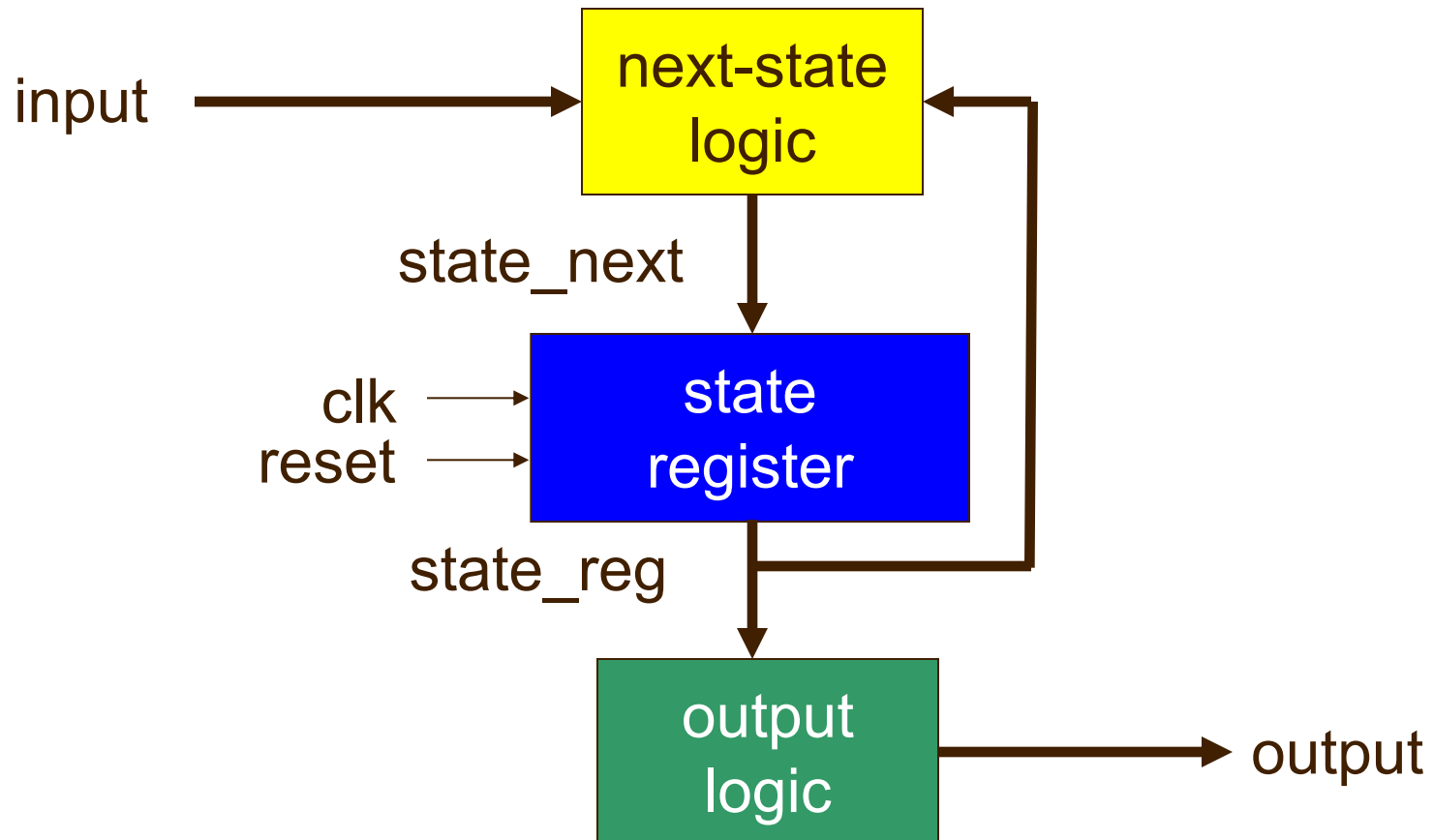

Mealy FSM

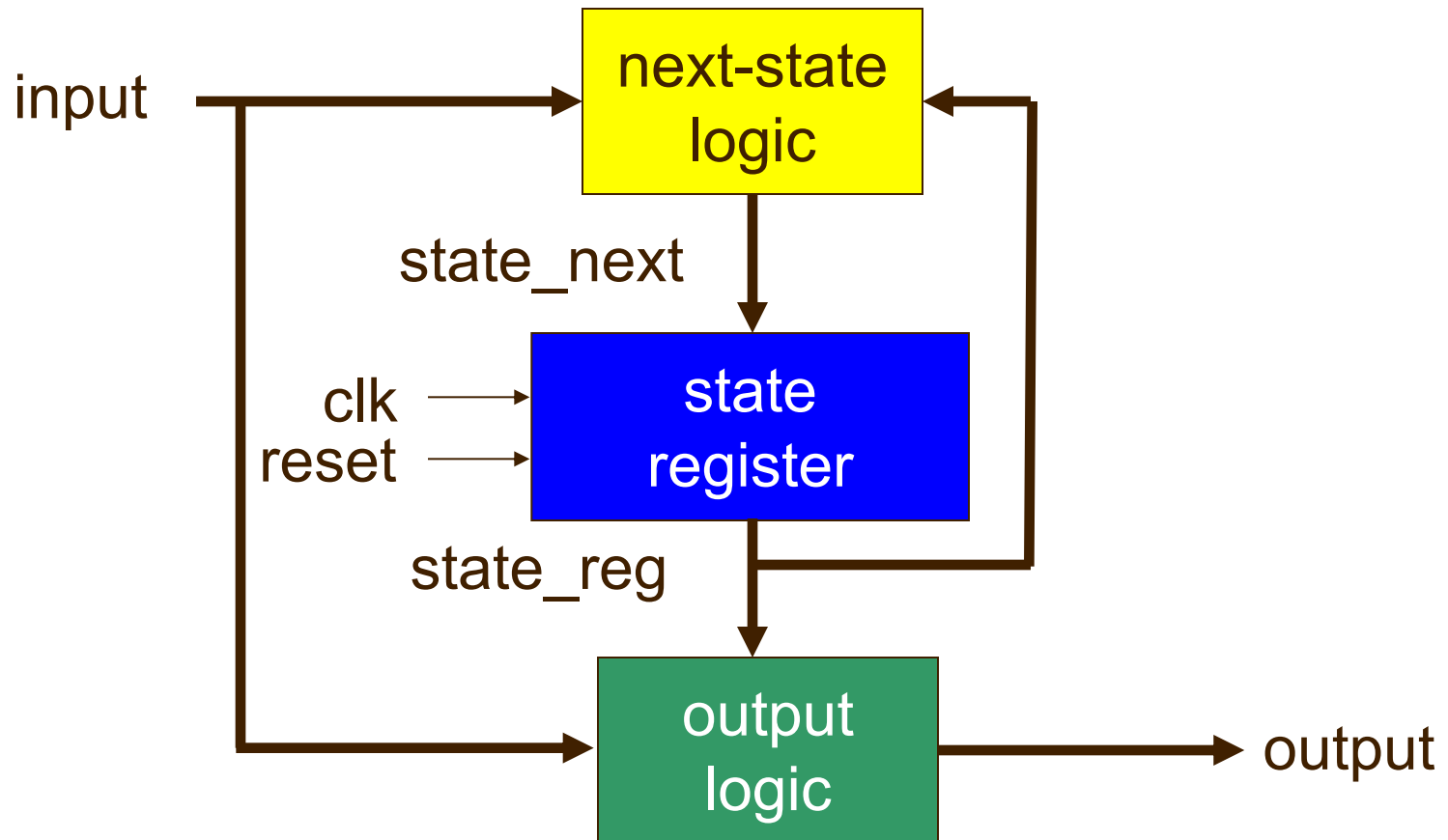- output is a function of the state and input signals



State Diagrams



High Performance


CoolClock

Low Power


PowerCache



Moore Machine

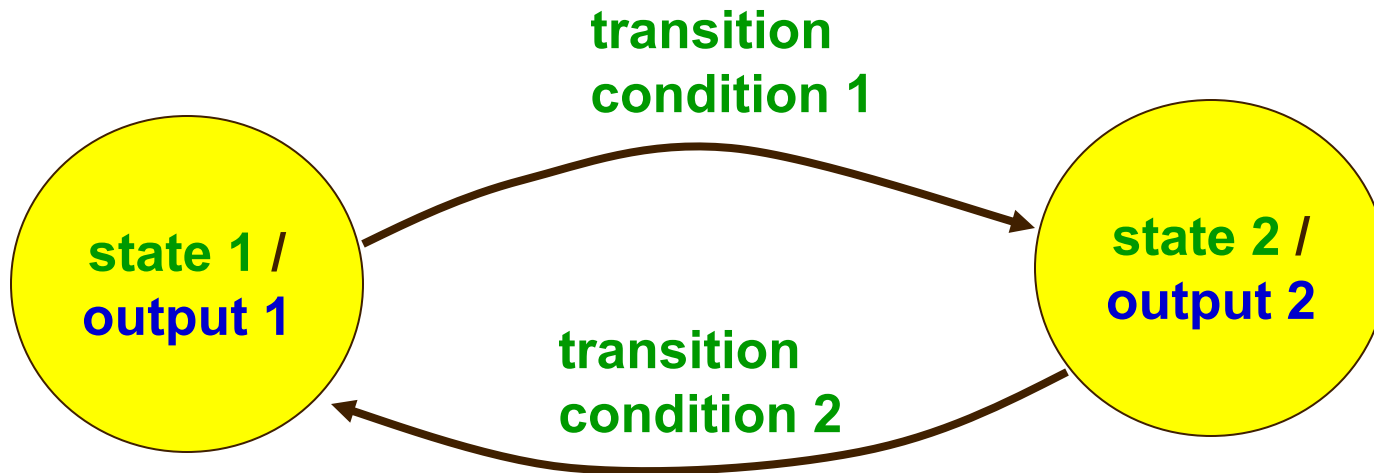


Mealy Machine

 

Moore FSM - Example 1

 
- Moore FSM that Recognizes Sequence “10”



Meaning of states:	S0: No elements of the sequence observed	S1: “1” observed	S2: “10” observed
--------------------	--	------------------	-------------------

Mealy FSM - Example 1

 
- Mealy FSM that Recognizes Sequence “10”



Meaning of states:

S0: No elements of the sequence observed	S1: “1” observed
--	------------------

Algorithmic State Machine (ASM) Charts

 

High Performance

CoolClock

Low Power

CoolClock

Algorithmic State Machine


Algorithmic State Machine –
representation of a Finite State Machine
suitable for FSMs with a larger number of
inputs and outputs compared to FSMs
expressed using state diagrams and state
tables.

ASM Chart


- Flowchart-like diagram
- Provides the same info as a state diagram
- More descriptive, better for complex digital systems

ASM describing generalized FSM

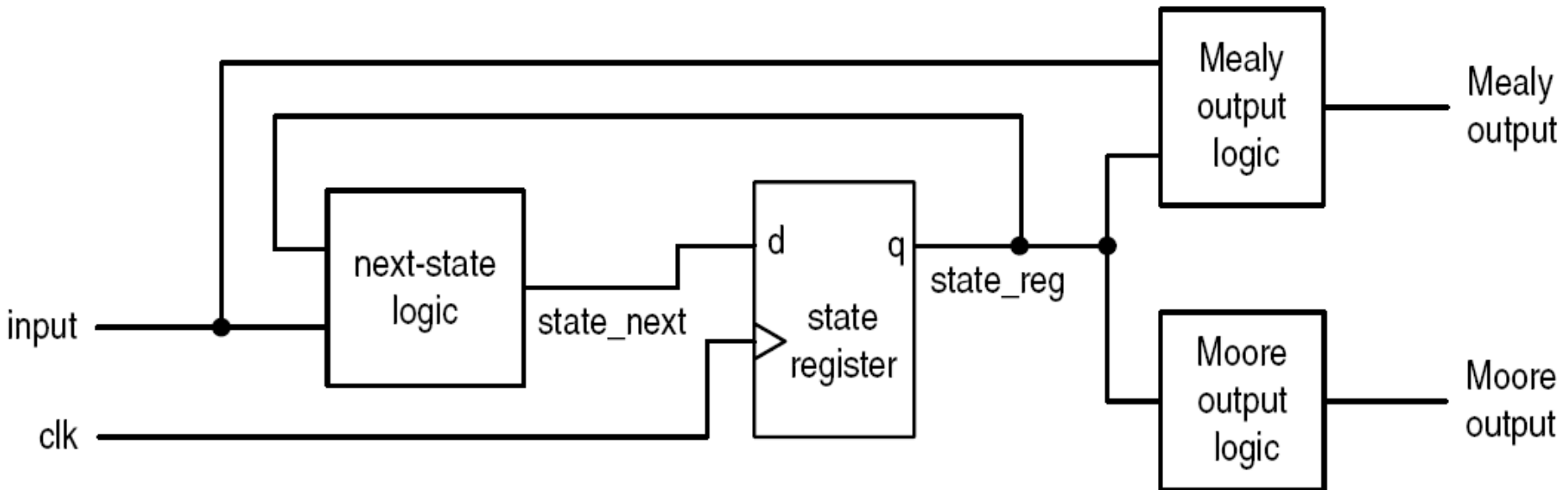
- Algorithmic state machines can model both Mealy and Moore Finite State Machines
- They can also model generalized machines that are of the mixed type




Elements used in ASM charts (1)

 

(a) State box

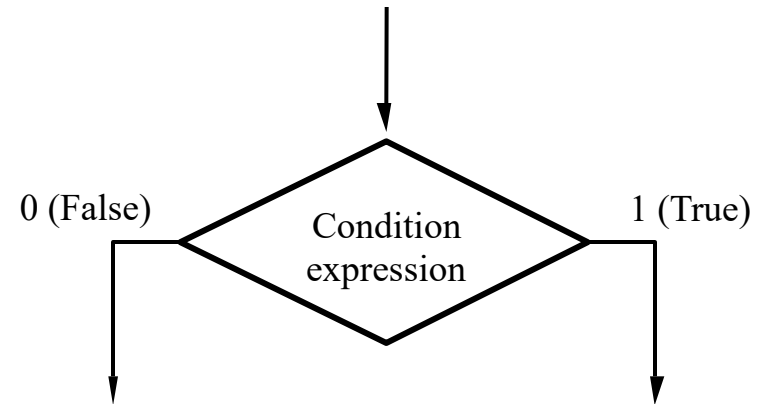


(b) Decision box

 

 (c) Conditional output box


State Box

- **State box** – represents a state.
- Equivalent to a node in a state diagram or a row in a state table.
- Contains register transfer actions or output signals
- **Moore-type outputs are listed inside of the box.**
- It is customary to write only the name of the signal that has to be asserted in the given state, e.g., z instead of $z \leq 1$.
- Also, it might be useful to write an action to be taken, e.g., $\text{count} \leq \text{count} + 1$, and only later translate it to asserting a control signal that causes a given action to take place (e.g., enable signal of a counter).




Decision Box

 - **Decision box** – indicates that a given condition is to be tested and the exit path is to be chosen accordingly. The condition expression may include one or more inputs to the FSM.



Conditional Output Box

 - **Conditional output box**
- **Denotes output signals that are of the Mealy type.**
- The condition that determines whether such outputs are generated is specified in the preceding decision box.



Simple Example

- BTND – reset controller
- BTNC – start counting from 0 to k-1


After the Counter reaches k-1, Done=1, LED LD0 on

- BTNU – resume the operation


Done=0, LED LD0 off

The current value of the counter should be displayed in the hexadecimal notation using four seven-segment displays available on the board.



After reset: Counter = 0x0000

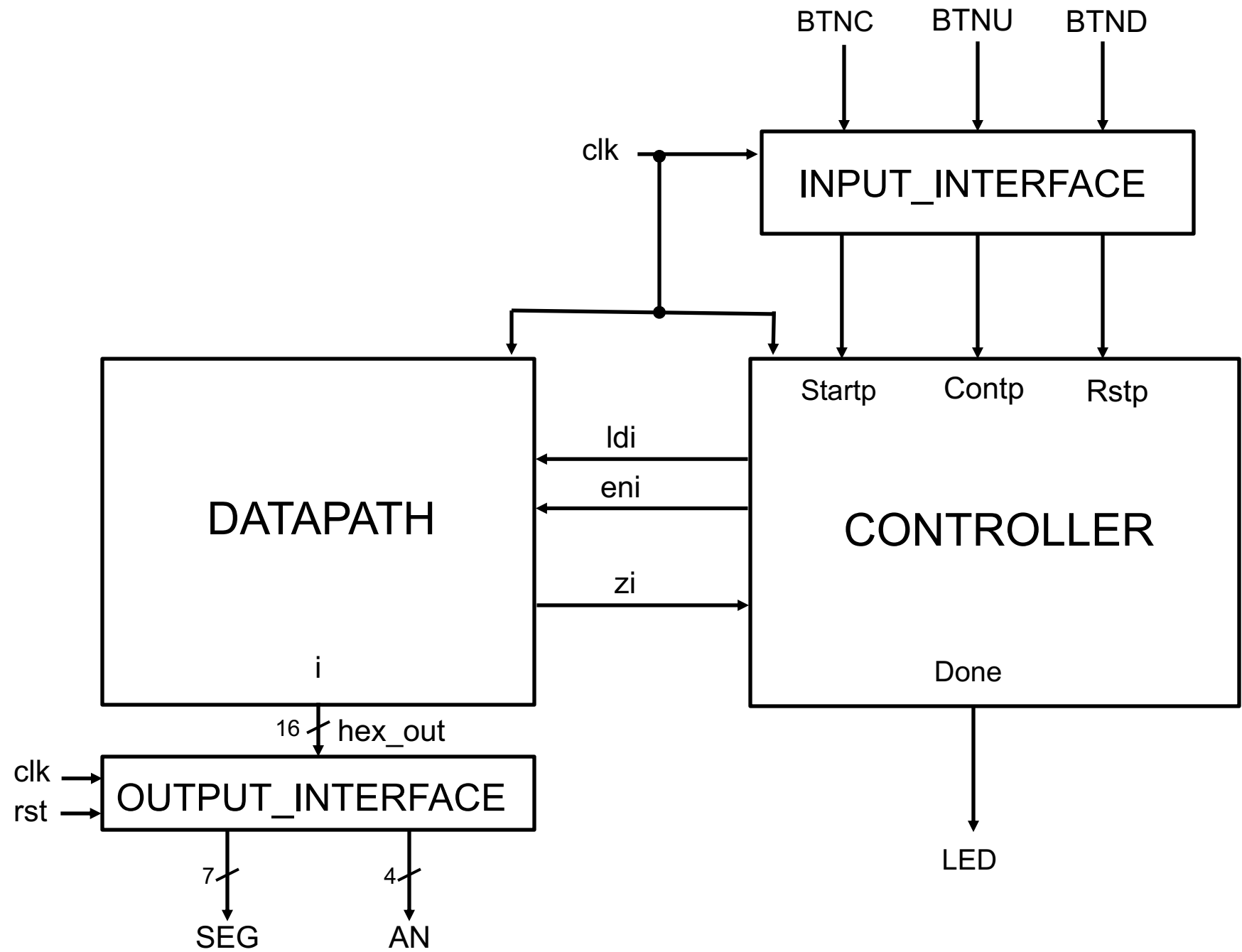


Simple Example: Datapath

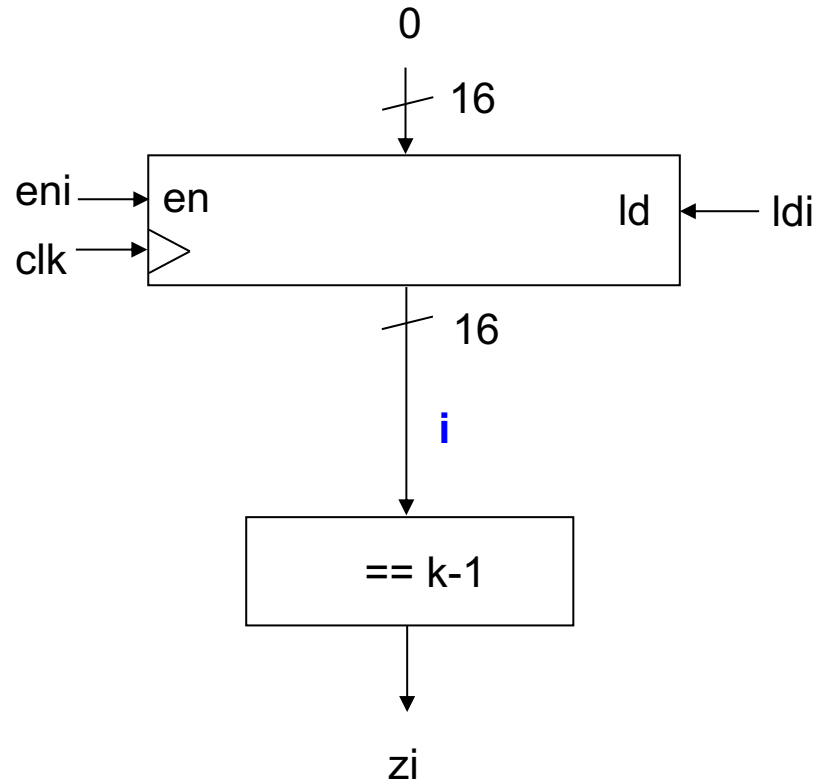

Simple Example: ASM Charts

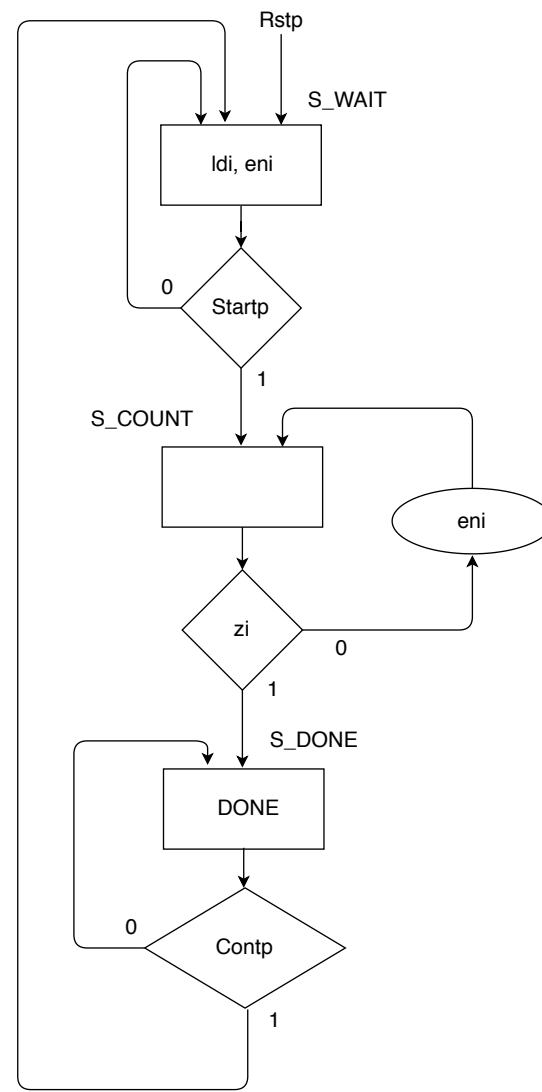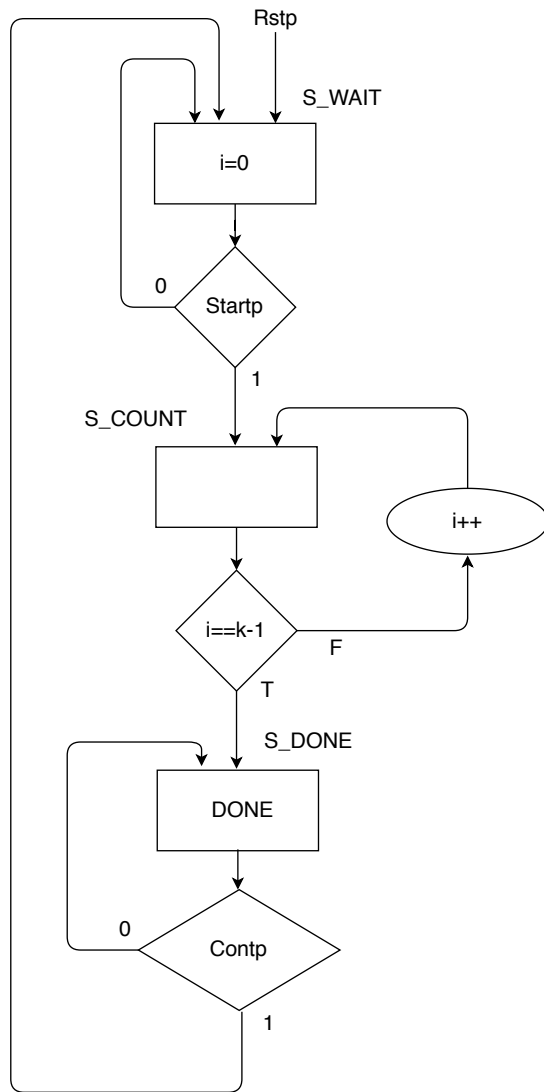

ASM Block

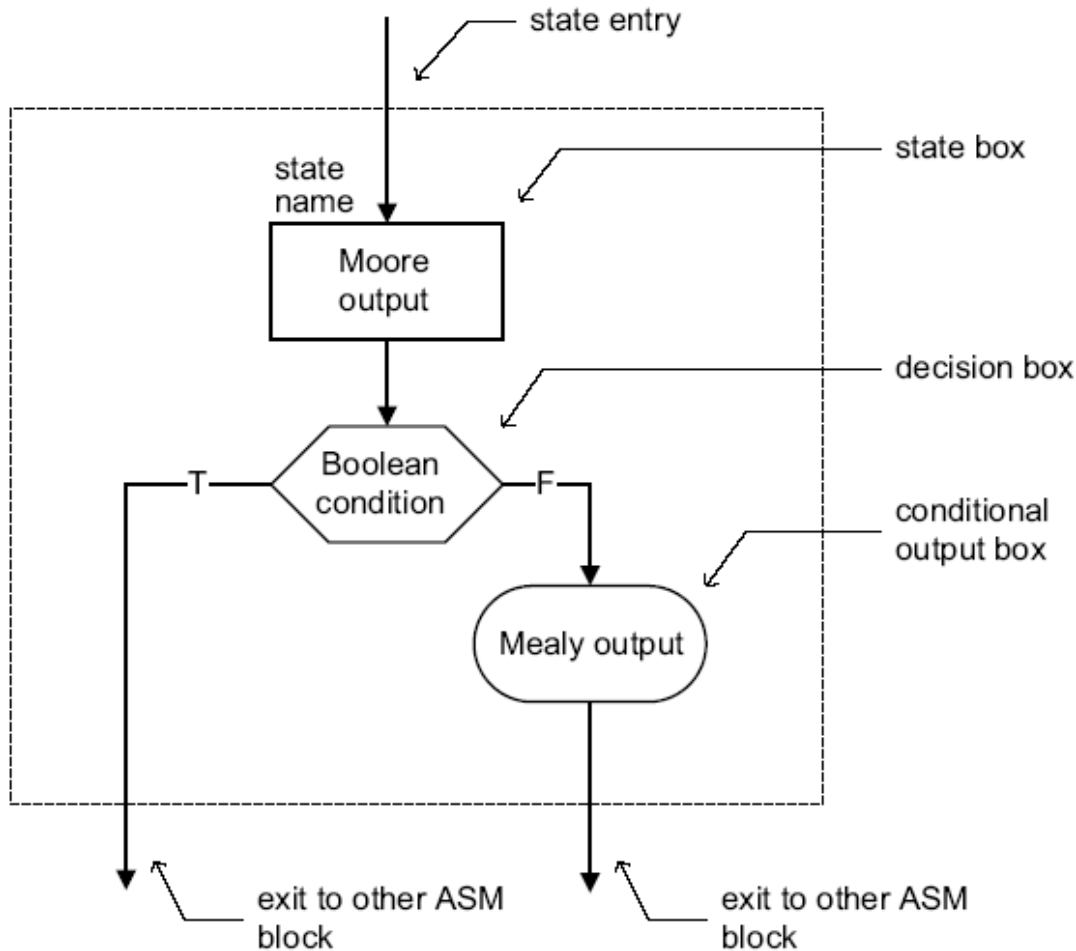


- One state box
- One or more (optional) decision boxes: with T (1) or F (0) exit paths
- One or more (optional) conditional output boxes: for Mealy outputs

Figure 10.4 ASM block.


ASM Chart Rules

- Difference between a regular flowchart and an ASM chart:
 - Transition governed by clock
 - Transition occurs between ASM blocks
- Basic rules:
 - For a given input combination, there is **one unique exit path** from the current ASM block
 - Any **closed loop** in an ASM chart **must include a state box**

Incorrect ASM Charts

 


(a)

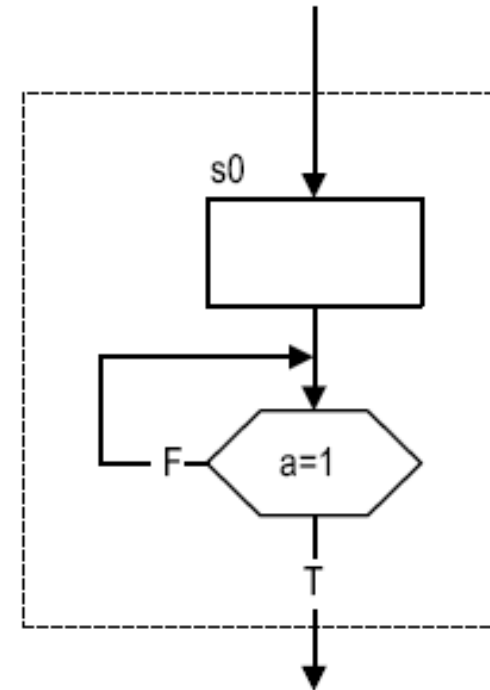

(b)


Based on RTL Hardware Design by P. Chu

Correct ASM Chart

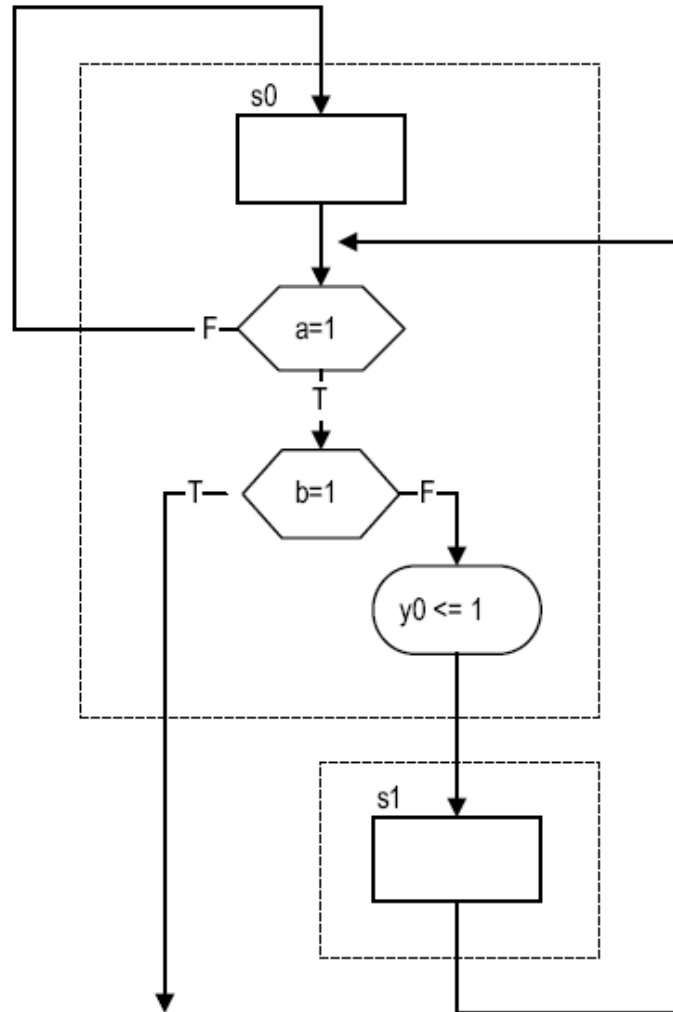

State Diagram of Moore FSM

 
- Moore FSM that Recognizes Sequence “10”



Meaning of states:


S0: No elements of the sequence observed	S1: “1” observed	S2: “10” observed
--	------------------	-------------------

ASM Chart of Moore FSM

 

State Diagram of Mealy FSM

 
- Mealy FSM that Recognizes Sequence “10”



Meaning of states:

S0: No elements of the sequence observed	S1: “1” observed
--	------------------

ASM Chart of Mealy Machine

 

Finite State Machines in VHDL



High Performance


High Clock

Low Power

Low Latency




Recommended FSM Coding Style

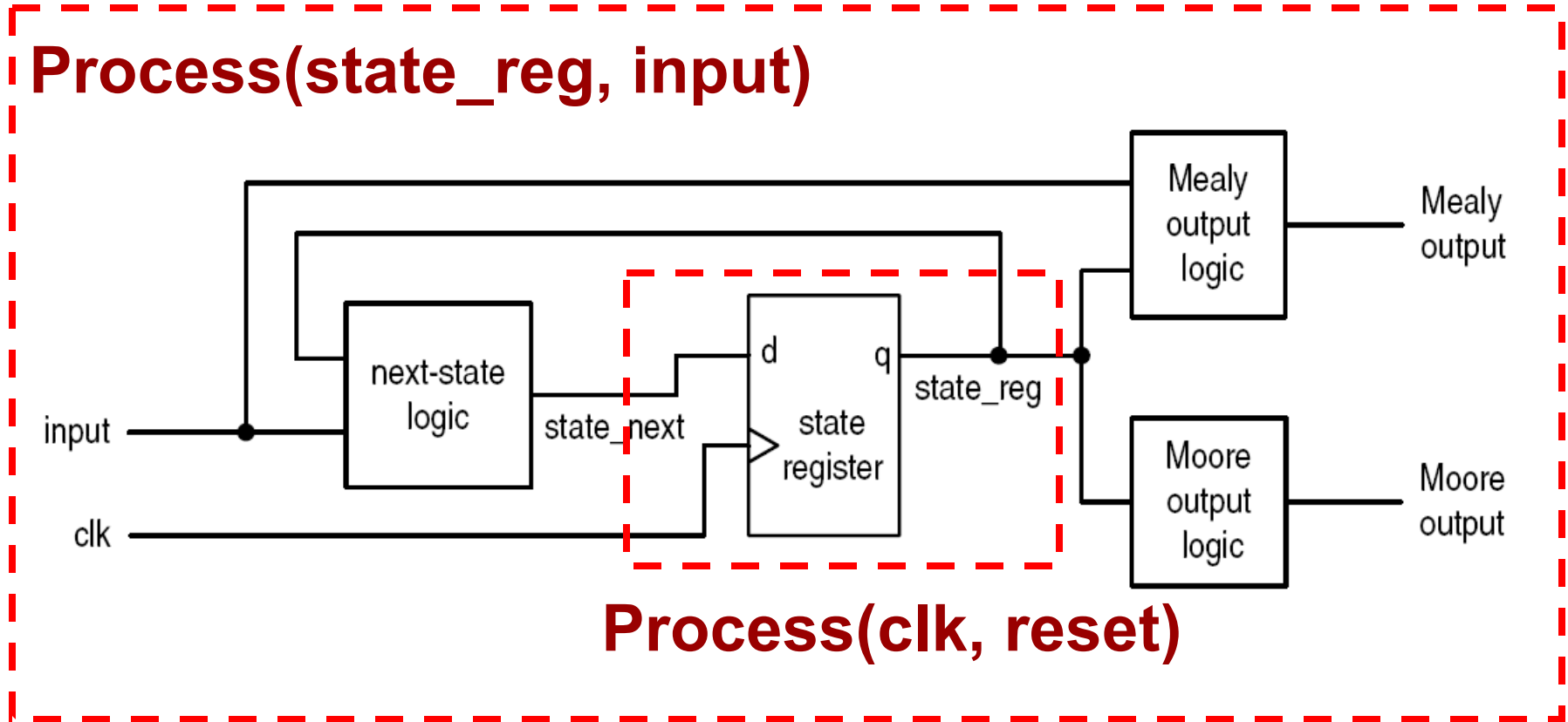

Based on RTL Hardware Design by P. Chu

ASM Chart of Moore Machine

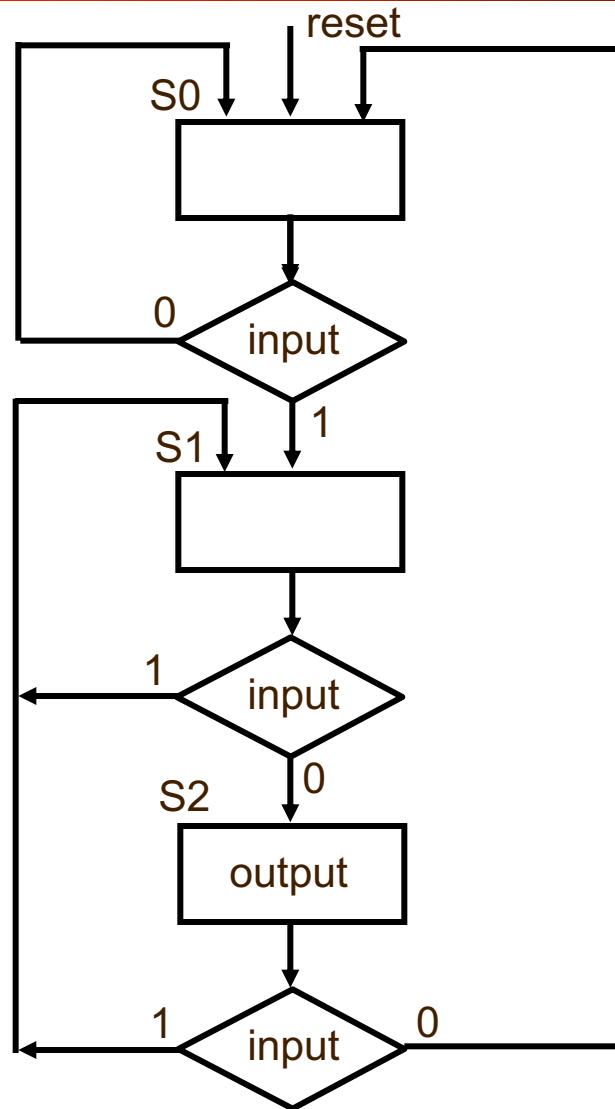

Moore FSM in VHDL (1)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY FSM_Moore IS
    PORT ( clk          : IN    STD_LOGIC ;
          reset        : IN    STD_LOGIC ;
          input        : IN    STD_LOGIC ;
          output       : OUT   STD_LOGIC);
END FSM_Moore ;
```

Moore FSM in VHDL (1)

ARCHITECTURE behavioral of FSM_Moore IS

TYPE state IS (S0, S1, S2);

SIGNAL state_reg, state_next: state;

BEGIN

U_Moore: PROCESS (clk, reset)

BEGIN

IF(reset = '1') **THEN**

state_reg <= S0;

ELSIF rising_edge(clk) **THEN**

state_reg <= state_next;

END IF;

END PROCESS;

Moore FSM in VHDL (2)

Next_State_Output:

PROCESS (state_reg, input)

BEGIN

 state_next <= state_reg;

 output <= '0';

CASE state_reg **IS**

WHEN S0 =>

IF input = '1' **THEN**

 state_next <= S1;

ELSE

 state_next <= S0;


END IF;

Moore FSM in VHDL (3)

```
    WHEN S1 =>
        IF input = '0' THEN
            state_next <= S2;
        ELSE
            state_next <= S1;
        END IF;
    WHEN S2 =>
        output <= '1' ;
        IF input = '1' THEN
            state_next <= S1;
        ELSE
            state_next <= S0;
        END IF;
END CASE;
END PROCESS;

END behavioral;
```

ASM Chart of Mealy Machine

 

Mealy FSM in VHDL (1)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY FSM_Mealy IS
    PORT ( clk : IN          STD_LOGIC ;
          reset  : IN       STD_LOGIC ;
          input  : IN       STD_LOGIC ;
          output : OUT      STD_LOGIC);
END FSM_Mealy ;
```


Mealy FSM in VHDL (1)

ARCHITECTURE behavioral of FSM_Mealy IS

TYPE state IS (S0, S1);

SIGNAL state_reg, state_next: state;

BEGIN

U_Mealy: PROCESS(clk, reset)

BEGIN

IF(reset = '1') THEN

state_reg <= S0;

ELSIF rising_edge(clk) THEN

state_reg <= state_next;

END IF;

END PROCESS;

Mealy FSM in VHDL (2)

Next_State_Output:

PROCESS (state_reg, input)

BEGIN

 state_next <= state_reg;

 output <= '0';

CASE state_reg **IS**

WHEN S0 =>

IF input = '1' **THEN**

 state_next <= S1;

ELSE

 state_next <= S0;


END IF;

Mealy FSM in VHDL (3)


```
        WHEN S1 =>
            IF input = '0' THEN
                state_next <= S0;
                output <= '1' ;
            ELSE
                state_next <= S1;
            END IF;
        END CASE;
    END PROCESS;

END behavioral;
```


ASM Chart of Moore Machine

 


ASM Chart of Mealy Machine

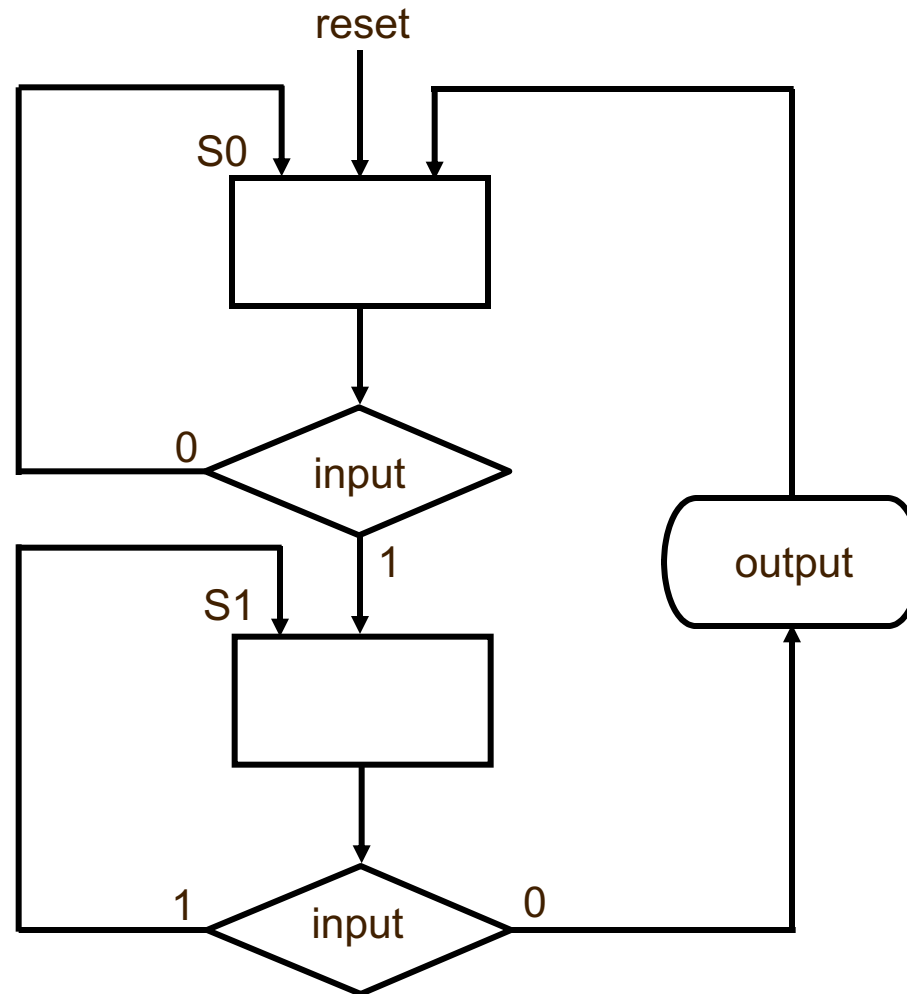

Moore & Mealy FSMs without delays

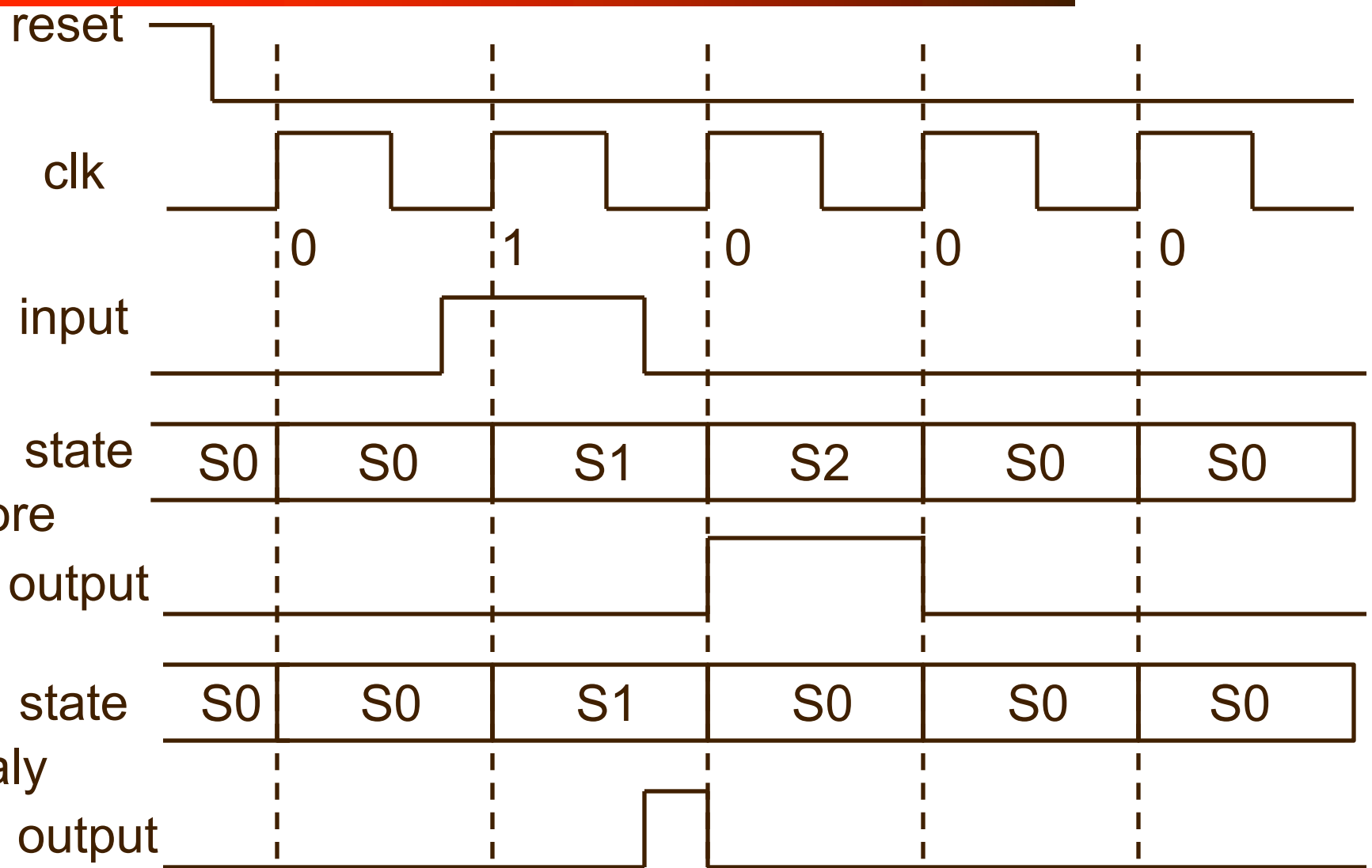

Moore & Mealy FSMs with delays

 

Moore vs. Mealy FSM (1)


- Moore and Mealy FSMs Can Be Functionally Equivalent
 - Equivalent Mealy FSM can be derived from Moore FSM and vice versa
- Mealy FSM Has Richer Description and Usually Requires Smaller Number of States
 - Smaller circuit area

Moore vs. Mealy FSM (2)

- Mealy FSM Computes Outputs as soon as Inputs Change
 - Mealy FSM responds one clock cycle sooner than equivalent Moore FSM
- Moore FSM Has No Combinational Path Between Inputs and Outputs
 - Moore FSM is less likely to affect the critical path of the entire circuit


Moore FSM

- output is a function of the state only

 

Mealy FSM

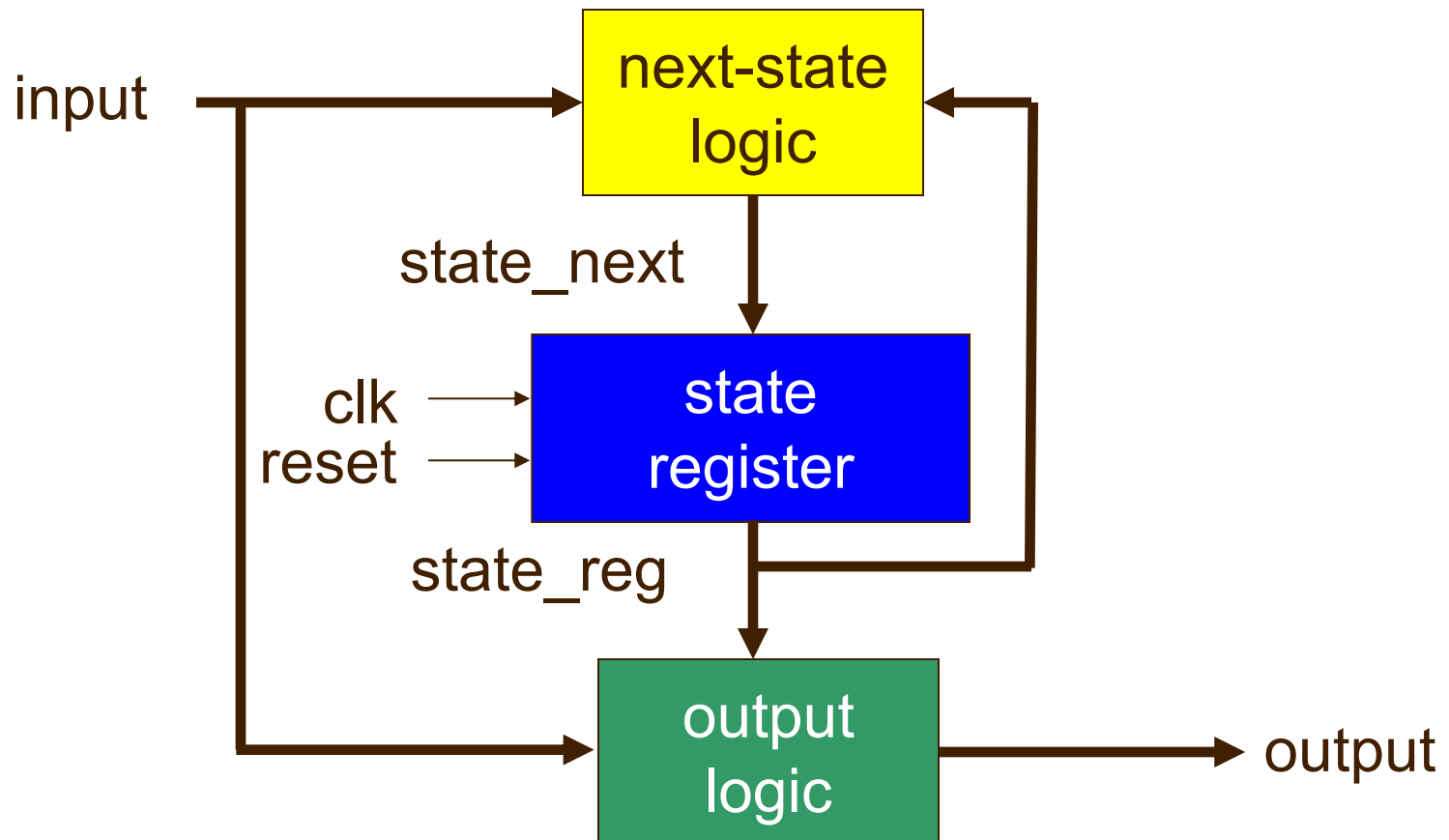- output is a function of the state and input signals



Which Way to Go?

Mealy FSM

Fewer states

Lower Area

Responds one clock cycle earlier


Moore FSM

Safer.
Less likely to affect the critical path.

ASMs representing simple FSMs

- Algorithmic state machines can model both Mealy and Moore Finite State Machines
- They can also model machines that are of the mixed type

Generalized FSM

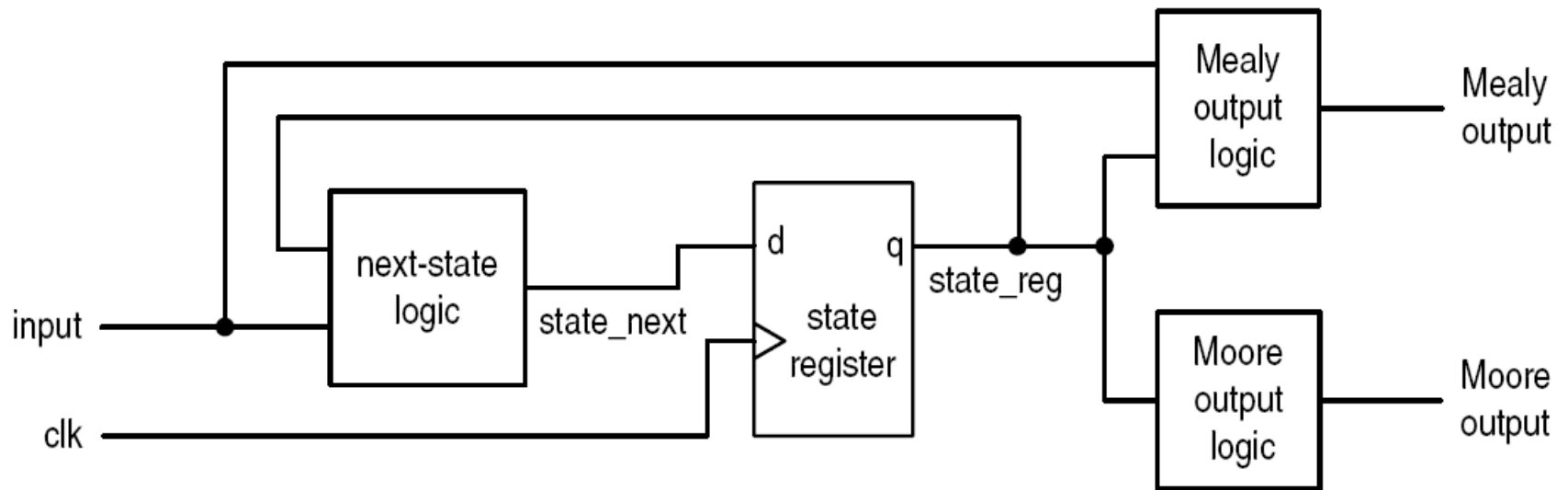

Based on RTL Hardware Design by P. Chu