

ECE 448

Lecture 4

Combinational-Circuit Building Blocks

Part 1

Reading


Required

- P. Chu, *FPGA Prototyping by VHDL Examples*
Chapter 3, RT-level combinational circuit

Recommended

- S. Brown and Z. Vranesic, *Fundamentals of Digital Logic with VHDL Design*
Chapter 6, Combinational-Circuit Building Blocks
Chapter 5.5, Design of Arithmetic Circuits Using CAD Tools

 Types of VHDL Description (Modeling Styles)




High Performance

CoolClock


Low Power

Types of VHDL Description

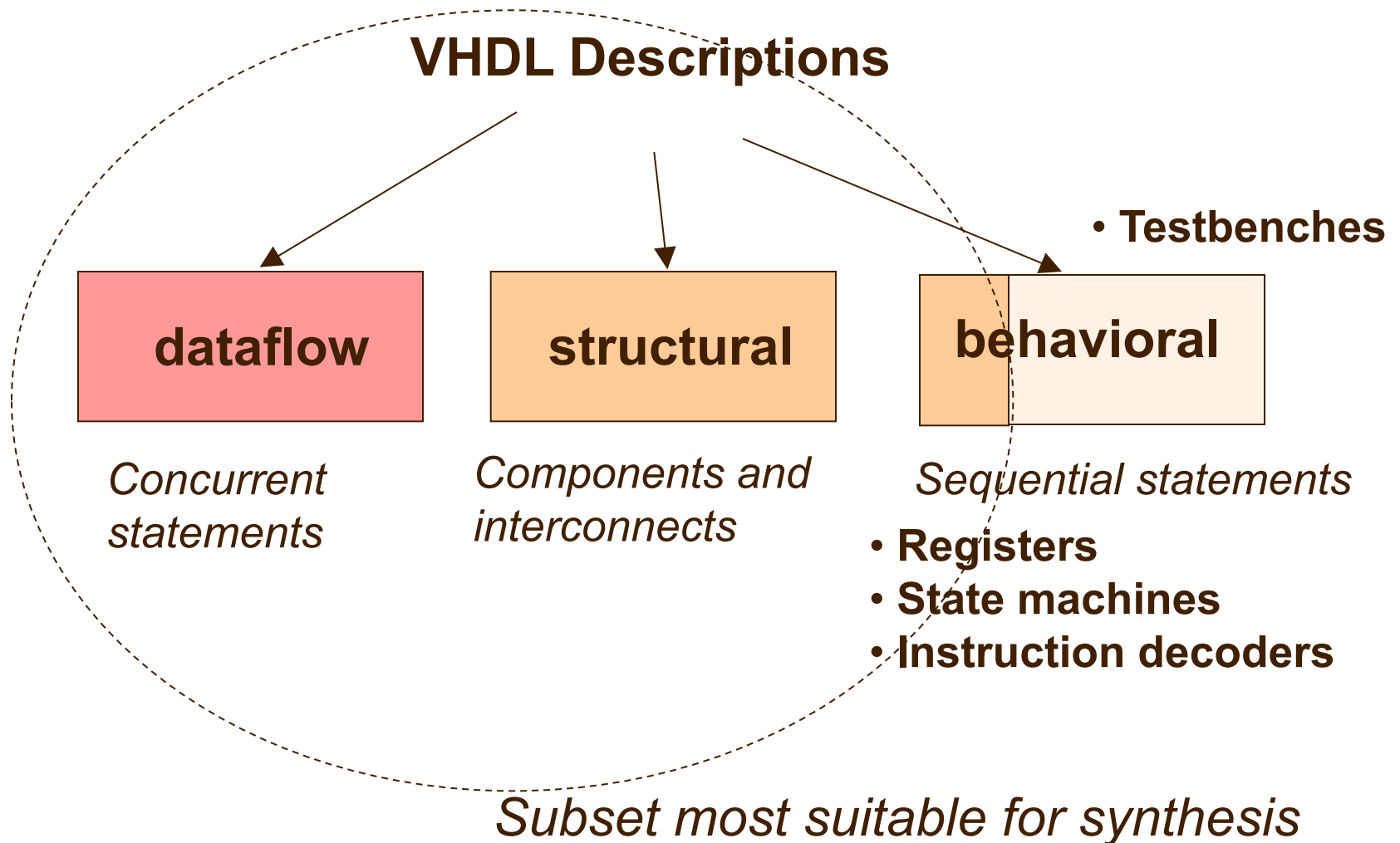

Register Transfer Level (RTL) Design Description


Today's Topic

 

- Use of medium scale-components (adders, multipliers, MUXes, ROMs)
- The designer needs to specify what happens in the circuit in every clock cycle


Synthesizable VHDL

Dataflow VHDL

 

VHDL code
synthesizable

Dataflow VHDL

 

VHDL code
synthesizable

Data-Flow VHDL

Concurrent Statements

- **simple concurrent signal assignment**
(\Leftarrow)
- **conditional concurrent signal assignment**
(when-else)
- **selected concurrent signal assignment**
(with-select-when)

Concurrent signal assignment

`<=`

```
target_signal <= expression;
```


Merging and Splitting Buses & Wires



High Performance


CoolClock

Low Power

PowerCache




Merging wires and buses

 

```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNTO 0);  
SIGNAL c: STD_LOGIC;  
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNTO 0);
```

```
d <=
```


Merging wires and buses

 

```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNTO 0);  
SIGNAL c: STD_LOGIC;  
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNTO 0);
```

```
d <= a & b & c;
```

Splitting buses

 


```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNTO 0);  
SIGNAL c: STD_LOGIC;  
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNTO 0);
```

```
a <=
```

```
b <=
```

```
c <=
```

Splitting buses

 

```
SIGNAL a: STD_LOGIC_VECTOR (3 DOWNTO 0) ;  
SIGNAL b: STD_LOGIC_VECTOR (4 DOWNTO 0) ;  
SIGNAL c: STD_LOGIC ;  
SIGNAL d: STD_LOGIC_VECTOR (9 DOWNTO 0) ;
```

```
a <= d(9 downto 6) ;
```

```
b <= d(5 downto 1) ;
```

```
c <= d(0) ;
```

Combinational-Circuit Building Blocks



High Performance

CoolClock

Low Power

CoolRun

Fixed Shifters & Rotators



High Performance

CoolClock



Low Power

CoolRunner

Fixed Logical Shift Left in VHDL

```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```

 
 
```
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```



Fixed Logical Shift Left in VHDL

```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```
 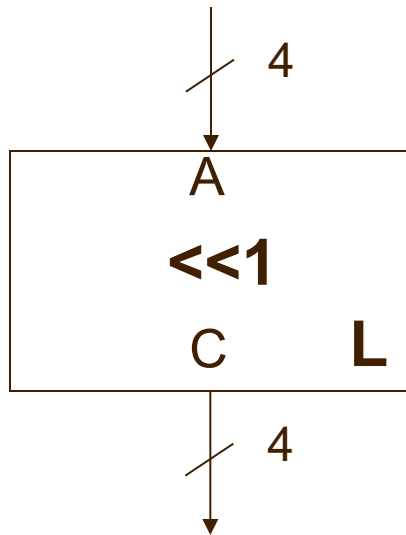
```
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```



$C \leftarrow A(2 \text{ downto } 0) \ \& \ '0';$

Logical vs. Arithmetic Shift Left: Example



Unsigned				Signed (2's complement)				
16	8	4	2	1	-8	4	2	1
	0	0	1	1	=	3		
0	0	1	1	0	=	6	(C=0)	
0	1	1	0	0	=	12	(C=0)	
1	1	0	0	0	=	8	(C=1)	
↑	↑							↑
C	product							Change of sign indicates going out of range (product invalid)
(carry)								

Carry indicates
going out of range
(product invalid)

Fixed Logical Shift Right in VHDL

```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```

 
 
```
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```



Fixed Logical Shift Right in VHDL

```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```

 
 
```
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```



```
C <= '0' & A(3 downto 1);
```

Fixed Arithmetic Shift Right in VHDL

 
 
```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```



Fixed Arithmetic Shift Right in VHDL

```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```
  
```
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```



```
C <= A(3) & A(3 downto 1);
```

Logical vs. Arithmetic Shift Right: Example

Unsigned		Signed (2's complement)	
8 4 2 1		-8 4 2 1	
1100	= 12	1100	= -4
0110	0=6 r.0	1110	0=-2 r.0
0011	0=3 r.0	1111	0=-1 r.0
0001	1=1 r.1	1111	1=-1 r.1
0000	1=0 r.1	1111	1=-1 r.1
0000	0=0 r.0	↑ ↑	
↑ ↑		quotient remainder	
quotient remainder			

Basic Formula for Integer Division

$$a/b = q \text{ remainder } r$$

Denoted by: $a/b = q \text{ r. } r$



$$a = b \cdot q + r$$

q: quotient

r: remainder

$$0 \leq r \leq b-1$$

Special case:

$$a/2 = q \text{ r. } r$$



$$a = 2 \cdot q + r$$

q: quotient

r: remainder

$$r = 0 \text{ or } 1$$

Logical vs. Arithmetic Shift Right: Example

Unsigned

8 4 2 1

$$1100 = 12$$

Signed (2's complement)



-8 4 2 1

$$1100 = -4$$

$12/2=6$	r.0	\Leftrightarrow	$12=2\cdot 6+0$	$-4/2=-2$	r.0	\Leftrightarrow	$-4=2\cdot (-2)+0$
$6/2=3$	r.0	\Leftrightarrow	$6=2\cdot 3+0$	$-2/2=-1$	r.0	\Leftrightarrow	$-2=2\cdot (-1)+0$
$3/2=1$	r.1	\Leftrightarrow	$3=2\cdot 1+1$	$-1/2=-1$	r.1	\Leftrightarrow	$-1=2\cdot (-1)+1$
$1/2=0$	r.1	\Leftrightarrow	$1=2\cdot 0+1$	$-1/2=-1$	r.1	\Leftrightarrow	$-1=2\cdot (-1)+1$
$0/2=0$	r.0	\Leftrightarrow	$0=2\cdot 0+0$				



Fixed Rotation Left in VHDL
  
```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```



Fixed Rotation Left in VHDL
 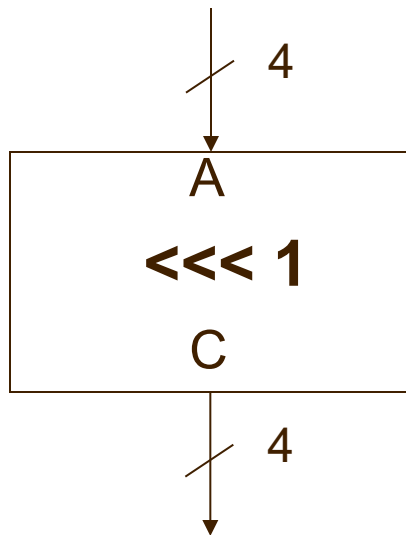
```
SIGNAL A:   STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL C:   STD_LOGIC_VECTOR(3 DOWNTO 0);
```



$C \leftarrow A(2 \text{ downto } 0) \ \& \ A(3);$

Gates



High Performance


CoolClock

Low Power

CoolFlash



Data-flow VHDL: Example

 

Data-flow VHDL: Example (1)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fulladd IS
    PORT ( x      : IN          STD_LOGIC ;
          y      : IN          STD_LOGIC ;
          cin    : IN          STD_LOGIC ;
          s      : OUT         STD_LOGIC ;
          cout   : OUT         STD_LOGIC ) ;
END fulladd ;
```

Data-flow VHDL: Example (2)

ARCHITECTURE dataflow OF fulladd IS

BEGIN


 s <= x XOR y XOR cin ;

 cout <= (x AND y) OR (cin AND x) OR (cin AND y) ;

END dataflow ;


Logic Operators

- Logic operators

 

- Logic operators precedence

Highest
↓
Lowest

 

only in VHDL-93
and above

No Implied Precedence

Wanted: $y = ab + cd$

Incorrect

$y \leq a \text{ and } b \text{ or } c \text{ and } d ;$

equivalent to

$y \leq ((a \text{ and } b) \text{ or } c) \text{ and } d ;$

equivalent to

$y = (ab + c)d$

Correct

$y \leq (a \text{ and } b) \text{ or } (c \text{ and } d) ;$



Adders

High Performance


CoolClock

Low Power

CoolRAM



Adder w/o carry in or carry out

 

Adder w/o carry in or carry out


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.numeric_std.all ;

ENTITY adder16 IS
    PORT ( X          : IN      STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          Y          : IN      STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          S          : OUT     STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
END adder16 ;

ARCHITECTURE dataflow OF adder16 IS
BEGIN
    S <= std_logic_vector(unsigned(X) + unsigned(Y));
END dataflow ;
```


Unsigned Adder vs. Signed Adder

Unsigned

 

C (carry out):
going out of range
for unsigned numbers


Signed

 

V (overflow):
going out of range
for signed numbers


Unsigned Subtractor vs. Signed Subtractor

Unsigned

 


C (carry out):
going out of range
for unsigned numbers

Signed

 

V (overflow):
going out of range
for signed numbers

16-bit Unsigned Adder

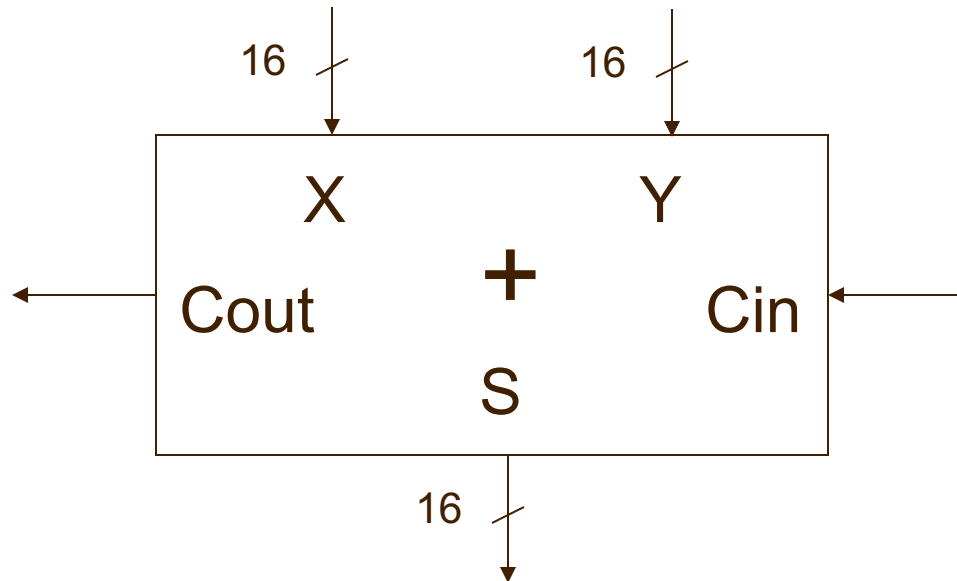

Addition of Unsigned Numbers (1)

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.numeric_std.all ;
```

```
ENTITY adder16 IS
```

```
    PORT ( Cin           : IN      STD_LOGIC ;  
          X             : IN      STD_LOGIC_VECTOR(15 DOWNTO 0) ;  
          Y             : IN      STD_LOGIC_VECTOR(15 DOWNTO 0) ;  
          S             : OUT     STD_LOGIC_VECTOR(15 DOWNTO 0) ;  
          Cout          : OUT     STD_LOGIC ) ;
```

```
END adder16 ;
```


Addition of Unsigned Numbers (3)

ARCHITECTURE dataflow OF adder16 IS

signal USum: **unsigned(16 DOWNT0 0)** ;

signal UCin: **unsigned(0 downto 0)**;

BEGIN

UCin(0) <= Cin;

USum <= unsigned('0' & X) + unsigned(Y) + UCin;

S <= std_logic_vector(USum(15 downto 0));

Cout <= USum(16) ;

END dataflow ;

Overloaded operators in IEEE numeric_std package

overloaded operator	description	data type of operand a	data type of operand b	data type of result
abs a - a	absolute value negation	signed		signed
a * b a / b a mod b a rem b a + b a - b	arithmetic operation	unsigned unsigned, natural signed signed, integer	unsigned, natural unsigned signed, integer signed	unsigned unsigned signed signed
a = b a /= b a < b a <= b a > b a >= b	relational operation	unsigned unsigned, natural signed signed, integer	unsigned, natural unsigned signed, integer signed	boolean boolean boolean boolean

Multipliers



High Performance

CoolClock

Low Power

CoolFlash



Unsigned vs. Signed Multiplication


Unsigned

$$\begin{array}{r} 1111 \\ \times 1111 \\ \hline 11100001 \end{array}$$
$$\begin{array}{r} 15 \\ \times 15 \\ \hline 225 \end{array}$$


Signed

$$\begin{array}{r} 1111 \\ \times 1111 \\ \hline 00000001 \end{array}$$
$$\begin{array}{r} -1 \\ \times -1 \\ \hline 1 \end{array}$$


8x8-bit Unsigned Multiplier

 

8x8-bit Signed Multiplier

 

8x8-bit Unsigned and Signed Multiplier

 

Multiplication of signed and unsigned numbers

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
USE ieee.numeric_std.all ;
```

entity multiply is

```
    port(  
        a : in STD_LOGIC_VECTOR(7 downto 0);  
        b : in STD_LOGIC_VECTOR(7 downto 0);  
        cu : out STD_LOGIC_VECTOR(15 downto 0);  
        cs : out STD_LOGIC_VECTOR(15 downto 0)  
    );  
end multiply;
```

architecture dataflow of multiply is
begin

-- signed multiplication

```
cs <= STD_LOGIC_VECTOR(SIGNED(a)*SIGNED(b));
```

-- unsigned multiplication

```
cu <= STD_LOGIC_VECTOR(UNSIGNED(a)*UNSIGNED(b));
```

```
end dataflow;
```


ROM



High Performance


CoolClock

Low Power

CoolFlash



ROM 8x16 example (1)

 

ROM 8x16 example (2)

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
USE ieee.numeric_std.all;
```

```
ENTITY rom IS
```

```
    PORT (
```

```
        Addr : IN STD_LOGIC_VECTOR(2 DOWNTO 0);
```

```
        Dout : OUT STD_LOGIC_VECTOR(15 DOWNTO 0)
```

```
    );
```

```
END rom;
```

ROM 8x16 example (3)

ARCHITECTURE dataflow OF rom IS

SIGNAL temp: INTEGER RANGE 0 TO 7;

TYPE vector_array IS ARRAY (0 to 7) OF STD_LOGIC_VECTOR(15 DOWNT0 0);

CONSTANT memory : vector_array :=


```
(      X"800A",  
      X"D459",  
      X"A870",  
      X"7853",  
      X"650D",  
      X"642F",  
      X"F742",  
      X"F548");
```

BEGIN

```
    temp <= to_integer(unsigned(Addr));
```

```
    Dout <= memory(temp);
```

END dataflow;

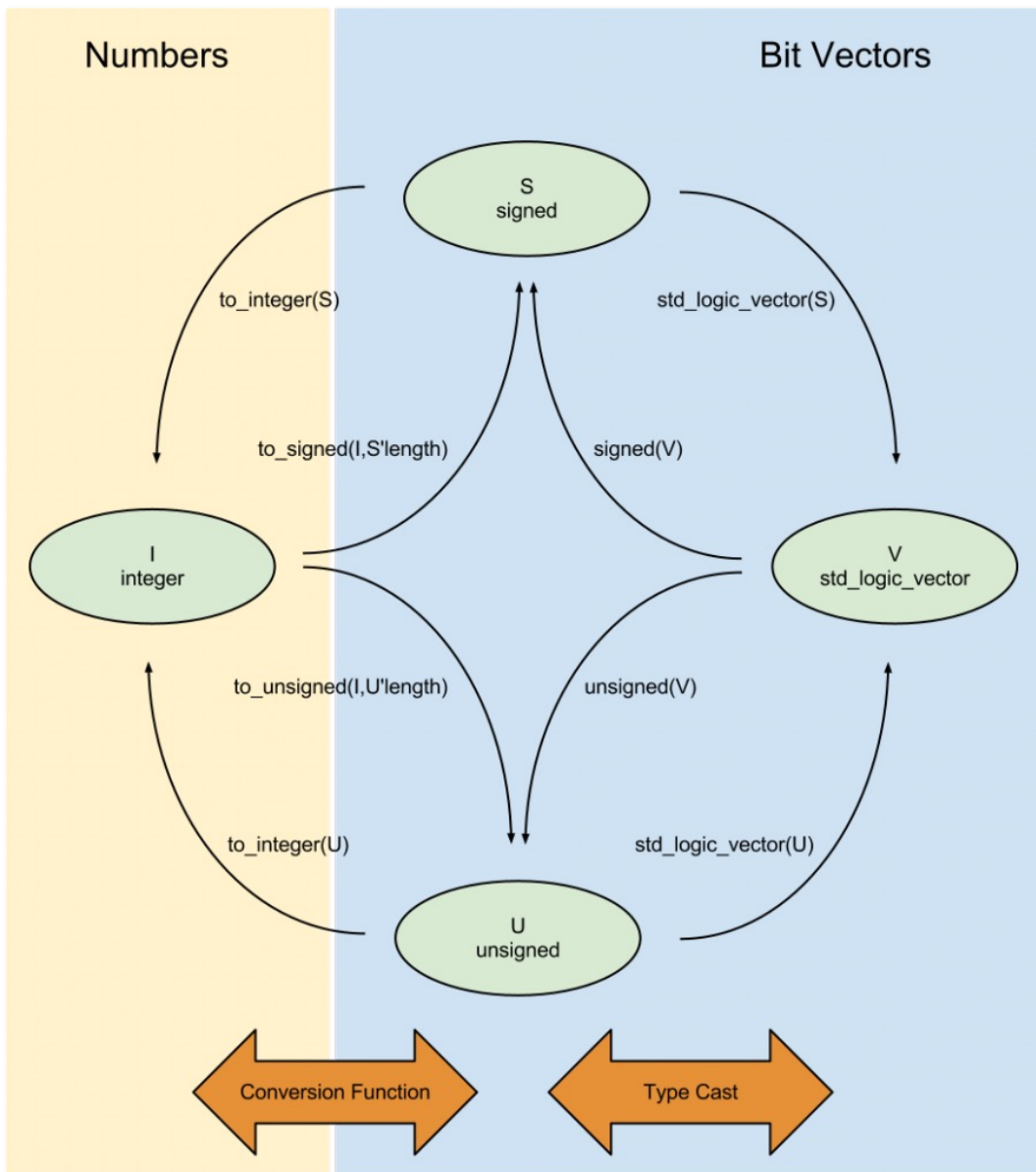

Source: VHDL Type Conversion
by Shannon Hilbert

available at <http://www.bitweenie.com/listings/vhdl-type-conversion>

ROM 8x16 example (4)

ARCHITECTURE dataflow OF rom IS

TYPE vector_array IS ARRAY (0 to 7) OF STD_LOGIC_VECTOR(15 DOWNT0 0);

CONSTANT memory : vector_array :=

```
(      X"800A",  
      X"D459",  
      X"A870",  
      X"7853",  
      X"650D",  
      X"642F",  
      X"F742",  
      X"F548");
```

BEGIN

```
Dout <= memory(to_integer(unsigned(Addr)));
```

END dataflow;

Overloaded operators in IEEE numeric_std package

overloaded operator	description	data type of operand a	data type of operand b	data type of result
abs a - a	absolute value negation	signed		signed
a * b a / b a mod b a rem b a + b a - b	arithmetic operation	unsigned unsigned, natural signed signed, integer	unsigned, natural unsigned signed, integer signed	unsigned unsigned signed signed
a = b a /= b a < b a <= b a > b a >= b	relational operation	unsigned unsigned, natural signed signed, integer	unsigned, natural unsigned signed, integer signed	boolean boolean boolean boolean

- E.g.,

```
signal a, b, c, d: unsigned(7 downto 0);  
. . .  
a <= b + c;  
d <= b + 1;  
e <= (5 + a + b) - c;
```


- E.g.

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
use ieee.numeric_std.all;
```

```
...
```

```
signal s1, s2, s3, s4, s5, s6: std_logic_vector(3 downto 0);
```

```
signal u1, u2, u3, u4, u6, u7: unsigned(3 downto 0);
```

```
signal sg: signed(3 downto 0);
```

– Ok

`u3 <= u2 + u1; --- ok, both operands unsigned`

`u4 <= u2 + 1; --- ok, operands unsigned and natural`

– Wrong

`u5 <= sg; -- type mismatch`

`u6 <= 5; -- type mismatch`

– Fix

`u5 <= unsigned(sg); -- type casting`

`u6 <= to_unsigned(5,4); -- conversion function`

– Wrong

```
u7 <= sg + u1; -- + undefined over the types
```

– Fix

```
u7 <= unsigned(sg) + u1; -- ok, but be careful
```

– Wrong

```
s3 <= u3; -- type mismatch
```

```
s4 <= 5; -- type mismatch
```

– Fix

```
s3 <= std_logic_vector(u3); -- type casting
```

```
s4 <= std_logic_vector(to_unsigned(5,4));
```

– Wrong

```
s5 <= s2 + s1; + undefined over std_logic_vector
```

```
s6 <= s2 + 1; + undefined
```

– Fix

```
s5 <= std_logic_vector(unsigned(s2) + unsigned(s1));
```

```
s6 <= std_logic_vector(unsigned(s2) + 1);
```