

ECE 448

Lecture 5

Combinational-Circuit Building Blocks

Part 2

Reading

Required

- P. Chu, *FPGA Prototyping by VHDL Examples*
Chapter 3, RT-level combinational circuit

Recommended

- S. Brown and Z. Vranesic, *Fundamentals of Digital Logic with VHDL Design*
Chapter 6, Combinational-Circuit Building Blocks
Chapter 5.5, Design of Arithmetic Circuits Using CAD Tools

Types of VHDL Description (Modeling Styles)




High Performance

CoolClock

Low Power


Low Power

Types of VHDL Description

 

Register Transfer Level (RTL) Design Description

Today's Topic

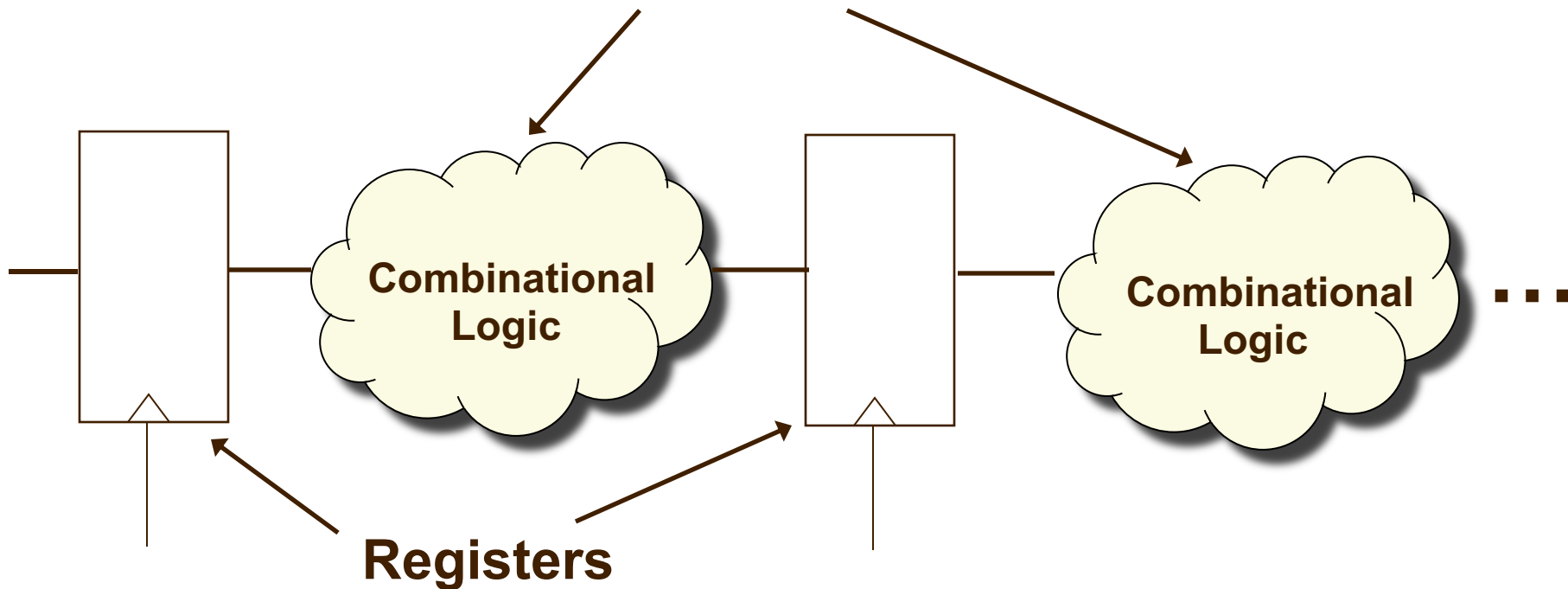

- Use of medium scale-components (adders, multipliers, MUXes, ROMs)
- The designer needs to specify what happens in the circuit in every clock cycle

Data-Flow VHDL

Concurrent Statements

- simple concurrent signal assignment
(\Leftarrow)
- conditional concurrent signal assignment
(when-else)
- selected concurrent signal assignment
(with-select-when)

Concurrent signal assignment

`<=`

```
target_signal <= expression;
```

Conditional concurrent signal assignment

When - Else

```
target_signal <= value1 when condition1 else  
                value2 when condition2 else  
                . . .  
                valueN-1 when conditionN-1 else  
                valueN;
```


Selected concurrent signal assignment

With –Select-When

```
with choice_expression select  
    target_signal <= expression1 when choices_1,  
                        expression2 when choices_2,  
                        . . .  
                        expressionN when choices_N;
```

Multiplexers



High Performance


CoolClock

Low Power

PowerPC



2-to-1 Multiplexer

 


(a) Graphical symbol

s	f
0	w_0
1	w_1

(b) Truth table

VHDL:

2-to-1 Multiplexer

 

(a) Graphical symbol

s	f
0	w_0
1	w_1


(b) Truth table

VHDL: **$f \leq w1$ WHEN $s = '1'$ ELSE $w0$;**

or


$f \leq w0$ WHEN $s = '0'$ ELSE $w1$;

Cascade of two multiplexers

 

VHDL:

Cascade of two multiplexers

 

VHDL:

```
y <= w1 WHEN s1 = '1' ELSE  
w2 WHEN s2 = '1' ELSE  
w3 ;
```

Operators

- Relational operators

=	/=	<	<=	>	>=
---	----	---	----	---	----

- Logic and relational operators precedence

Highest						
↓	not					
↓	=	/=	<	<=	>	>=
↓	and	or	nand	nor	xor	xnor
Lowest						

Priority of logic and relational operators

compare $a = bc$

Incorrect

... when $a = b$ **and** c else ...

equivalent to


... when $(a = b)$ **and** c else ...

Correct

... when $a = (b$ **and** $c)$ else ...

4-to-1 Multiplexer

(a) Graphic symbol

 


(b) Truth table

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

4-to-1 Multiplexer

(a) Graphic symbol

 

(b) Truth table

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

WITH s SELECT

**$f \leq w_0$ WHEN "00",
 w_1 WHEN "01",
 w_2 WHEN "10",
 w_3 WHEN OTHERS ;**

Decoders



High Performance

CoolClock

Low Power

Low Power




2-to-4 Decoder

(a) Truth table

En	w_1	w_0	y_3	y_2	y_1	y_0
1	0	0				
1	0	1				
1	1	0				
1	1	1				
0	–	–				

(b) Graphical symbol

 


2-to-4 Decoder

(a) Truth table

En	w_1	w_0	y_3	y_2	y_1	y_0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	–	–	0	0	0	0

(b) Graphical symbol

 


2-to-4 Decoder

(a) Truth table

En	w_1	w_0	y_3	y_2	y_1	y_0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	–	–	0	0	0	0

(b) Graphical symbol

 

```
Enw <= En & w ;  
WITH Enw SELECT  
y <= "0001" WHEN "100",  
      "0010" WHEN "101",  
      "0100" WHEN "110",  
      "1000" WHEN "111",  
      "0000" WHEN OTHERS ;
```


VHDL code for a 2-to-4 Decoder entity

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY dec2to4 IS
    PORT ( w      : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          En     : IN      STD_LOGIC ;
          y      : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END dec2to4 ;

ARCHITECTURE dataflow OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR(2 DOWNTO 0) ;
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "0001" WHEN "100",
        "0010" WHEN "101",
        "0100" WHEN "110",
        "1000" WHEN "111",
        "0000" WHEN OTHERS ;
END dataflow ;
```

Encoders

 

High Performance


CoolClock

Low Power

PowerPC




Priority Encoder

 


w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0			
0	0	0	1			
0	0	1	-			
0	1	-	-			
1	-	-	-			

Priority Encoder

 

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	-	-	0
0	0	0	1	0	0	1
0	0	1	-	0	1	1
0	1	-	-	1	0	1
1	-	-	-	1	1	1

Priority Encoder

 

```
y <= "11" WHEN w(3) = '1' ELSE  
      "10" WHEN w(2) = '1' ELSE  
      "01" WHEN w(1) = '1' ELSE  
      "00" ;
```

```
z <= '0' WHEN w = "0000" ELSE '1' ;
```

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	-	-	0
0	0	0	1	0	0	1
0	0	1	-	0	1	1
0	1	-	-	1	0	1
1	-	-	-	1	1	1

VHDL code for a Priority Encoder entity

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY priority IS
    PORT ( w   : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          y   : OUT   STD_LOGIC_VECTOR(1 DOWNTO 0) ;
          z   : OUT   STD_LOGIC ) ;
END priority ;

ARCHITECTURE dataflow OF priority IS
BEGIN
    y <= "11" WHEN w(3) = '1' ELSE
        "10" WHEN w(2) = '1' ELSE
        "01" WHEN w(1) = '1' ELSE
        "00" ;
    z <= '0' WHEN w = "0000" ELSE '1' ;
END dataflow ;
```

Buffers



High Performance


CoolClock

Low Power



CoolFlash



Tri-state Buffer

 

(a) A tri-state buffer

  


(b) Equivalent circuit



e	x	f
0	0	
0	1	
1	0	0
1	1	1

(c) Truth table

Tri-state Buffer

 

(a) A tri-state buffer

  


(b) Equivalent circuit


e	x	f
0	0	Z
0	1	Z
1	0	0
1	1	1

(c) Truth table


Four types of Tri-state Buffers

 


(a)

 

(b)

 


(c)

 


(d)


Four types of Tri-state Buffers

 


f <= x WHEN (e = '1') ELSE 'Z';

 

f <= not x WHEN (e = '1') ELSE 'Z';

 

f <= x WHEN (e = '0') ELSE 'Z';

 

f <= not x WHEN (e = '0') ELSE 'Z';

Tri-state Buffer entity (1)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY tri_state IS
    PORT ( e:  IN STD_LOGIC;
          x:  IN STD_LOGIC;
          f:  OUT STD_LOGIC
        );
END tri_state;
```

Tri-state Buffer entity (2)

ARCHITECTURE dataflow OF tri_state IS

BEGIN

f <= x WHEN (e = '1') ELSE 'Z';

END dataflow;

**Describing
Combinational Logic
Using
Dataflow Design Style**



High Performance


CoolClock

Low Power

CoolRAM

MLU Example

MLU Block Diagram

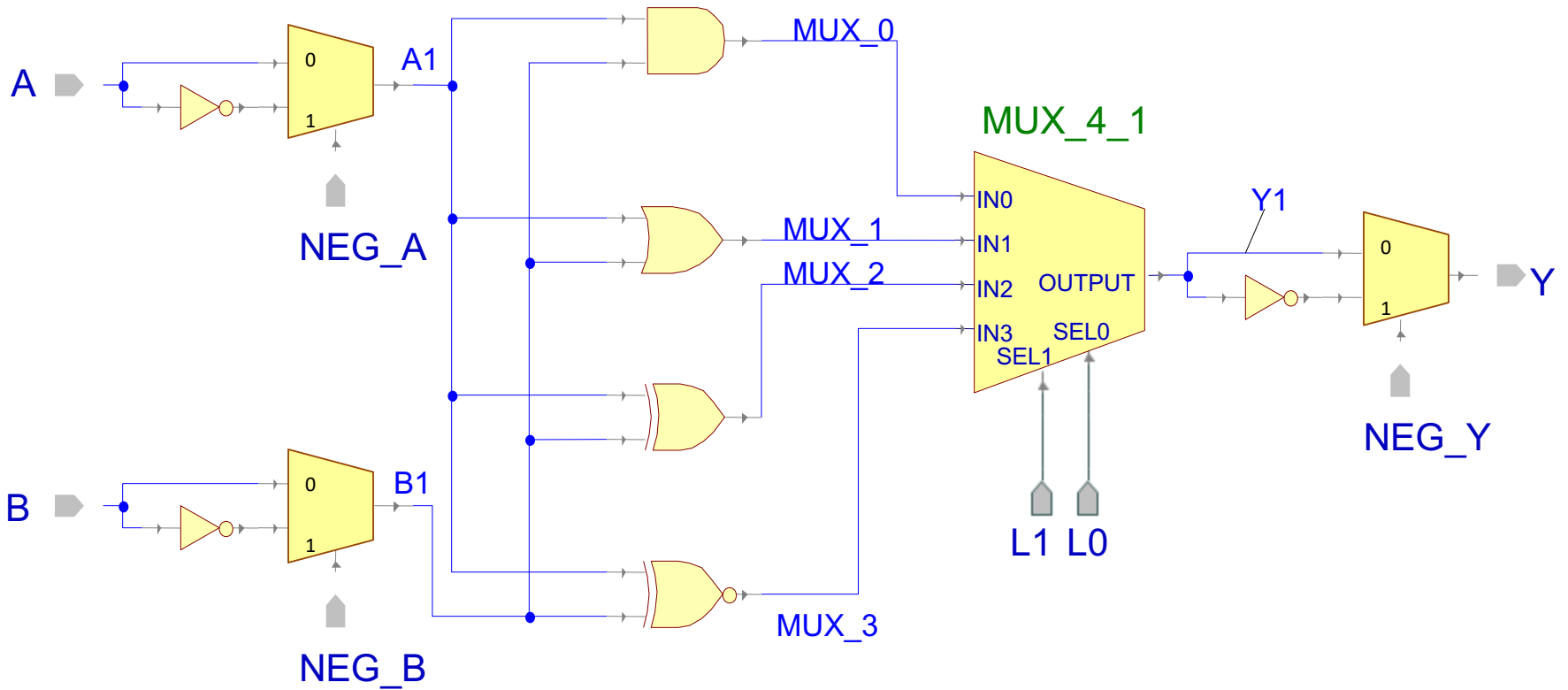

MLU: Entity Declaration

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY mlu IS
    PORT(
        NEG_A : IN STD_LOGIC;
        NEG_B : IN STD_LOGIC;
        NEG_Y : IN STD_LOGIC;
        A :     IN STD_LOGIC;
        B :     IN STD_LOGIC;
        L1 :    IN STD_LOGIC;
        L0 :    IN STD_LOGIC;
        Y :     OUT STD_LOGIC
    );
END mlu;
```

MLU: Architecture Declarative Section

```
ARCHITECTURE mlu_dataflow OF mlu IS
```

```
SIGNAL A1 : STD_LOGIC;  
SIGNAL B1 : STD_LOGIC;  
SIGNAL Y1 : STD_LOGIC;  
SIGNAL MUX_0 : STD_LOGIC;  
SIGNAL MUX_1 : STD_LOGIC;  
SIGNAL MUX_2 : STD_LOGIC;  
SIGNAL MUX_3 : STD_LOGIC;  
SIGNAL L: STD_LOGIC_VECTOR(1 DOWNT0 0);
```


MLU - Architecture Body

```
BEGIN
  A1<= NOT A WHEN (NEG_A='1') ELSE
    A;
  B1<= NOT B WHEN (NEG_B='1') ELSE
    B;
  Y <= NOT Y1 WHEN (NEG_Y='1') ELSE
    Y1;

  MUX_0 <= A1 AND B1;
  MUX_1 <= A1 OR B1;
  MUX_2 <= A1 XOR B1;
  MUX_3 <= A1 XNOR B1;

  L <= L1 & L0;

  with (L) select
    Y1 <= MUX_0 WHEN "00",
          MUX_1 WHEN "01",
          MUX_2 WHEN "10",
          MUX_3 WHEN OTHERS;

END mlu_dataflow;
```

The background is a light blue collage of various electronic components and devices. At the top center is a large integrated circuit (IC) chip. Below it is another IC chip. To the left and right are various other components like capacitors, resistors, and smaller ICs. In the bottom left and right corners, there are images of mobile phones and a keyboard. The text is centered over this collage.

**Logic Implied Most Often by
Conditional and Selected
Concurrent Signal
Assignments**

Data-Flow VHDL

Concurrent Statements

- simple concurrent signal assignment
(\Leftarrow)
- conditional concurrent signal assignment
(when-else)
- selected concurrent signal assignment
(with-select-when)

Conditional concurrent signal assignment


When - Else

```
target_signal <= value1 when condition1 else  
                value2 when condition2 else  
                . . .  
                valueN-1 when conditionN-1 else  
                valueN;
```

Most often implied structure

When - Else
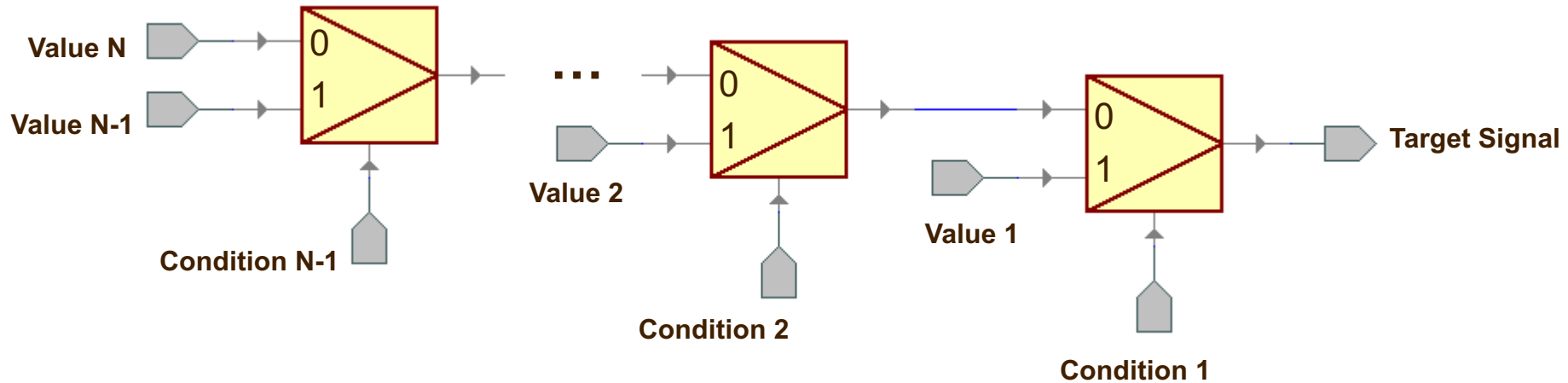
```
target_signal <= value1 when condition1 else  
                value2 when condition2 else  
                . . .  
                valueN-1 when conditionN-1 else  
                valueN;
```



Data-Flow VHDL

Concurrent Statements

- **simple concurrent signal assignment**
(\Leftarrow)
- **conditional concurrent signal assignment**
(when-else)
- **selected concurrent signal assignment**
(with-select-when)

Selected concurrent signal assignment

With –Select-When

```
with choice_expression select  
    target_signal <= expression1 when choices_1,  
                       expression2 when choices_2,  
                       . . .  
                       expressionN when choices_N;
```


Selected concurrent signal assignment

- `choice_expression`
 - Discrete type or 1-D array
 - With finite possible values
- `choices_k`
 - A value of the data type used for `choice_expression`
- Choices must be
 - Mutually exclusive
 - All inclusive
 - `OTHERS` can be used as a last choice
- `target_signal` and `expressions(1..N)` must have the same type

Most Often Implied Structure

With –Select-When
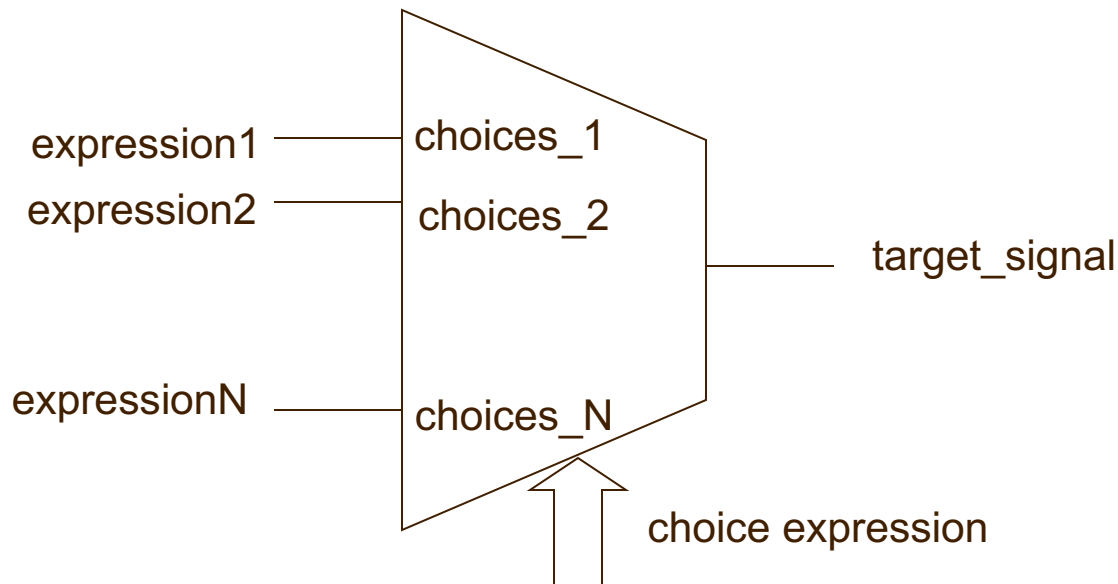
```
with choice_expression select  
    target_signal <= expression1 when choices_1,  
                    expression2 when choices_2,  
                    . . .  
                    expressionN when choices_N;
```



Allowed formats of *choices_k*

WHEN value

WHEN value_1 | value_2 | | value N

WHEN OTHERS


Allowed formats of *choices_k* - example

```
WITH sel SELECT
    y <= a WHEN "000",
        c WHEN "001" | "111",
        d WHEN OTHERS;
```

Corresponding circuit

```
WITH sel SELECT
```

```
  y <= a WHEN "000",  
    c WHEN "001" | "111",  
    d WHEN OTHERS;
```

 

when-else vs. with-select-when (1)

"when-else" should be used when:

- 1) there is only one condition (and thus, only one else), as in the 2-to-1 MUX
- 2) conditions are independent of each other (e.g., they test values of different signals)
- 3) conditions reflect priority (as in priority encoder); one with the highest priority need to be tested first.

when-else vs. with-select-when (2)

"with-select-when" should be used when there is

- 1) more than one condition
- 2) conditions are closely related to each other (e.g., represent different ranges of values of the same signal)
- 3) all conditions have the same priority (as in the 4-to-1 MUX).