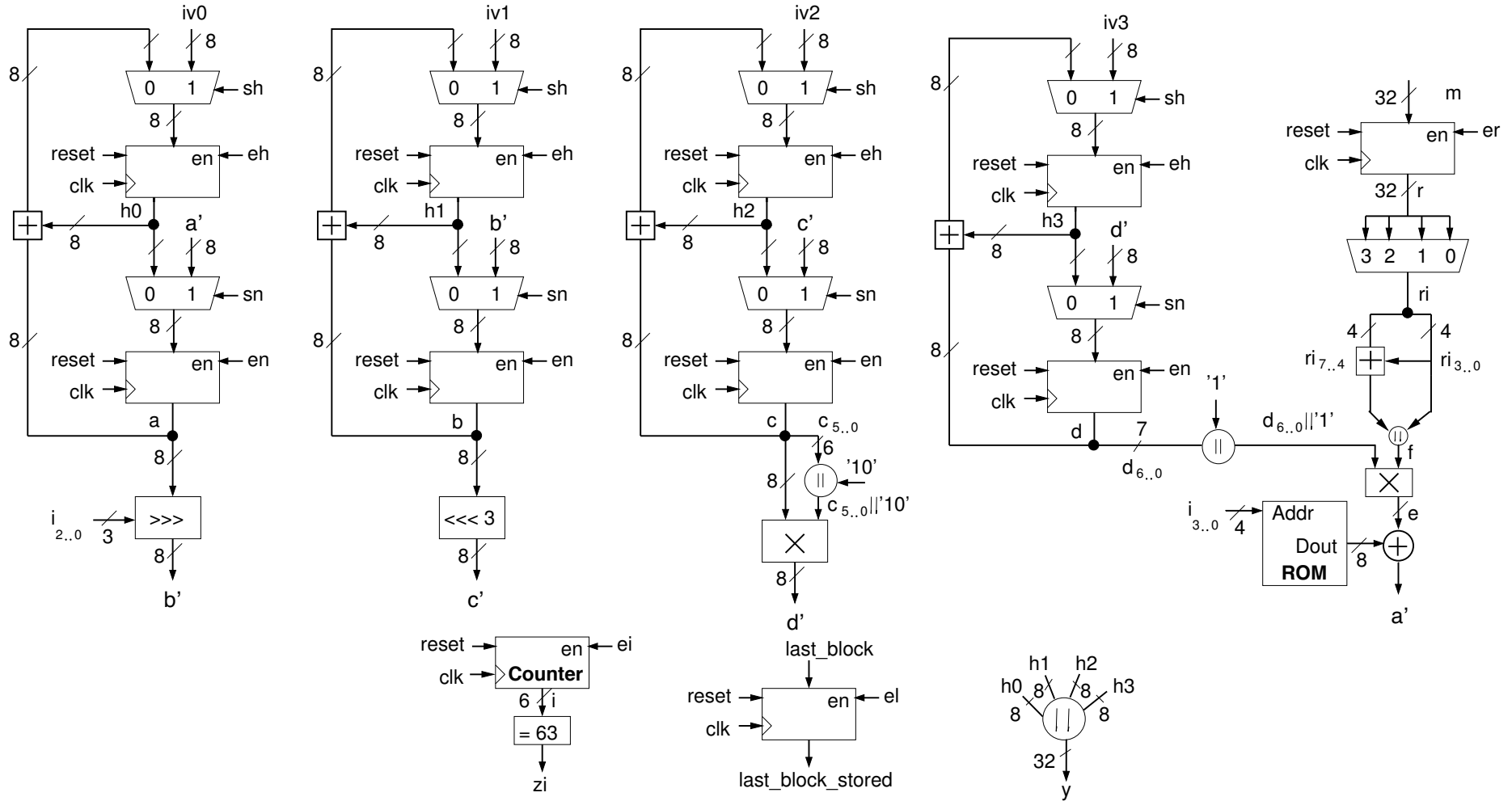


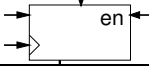
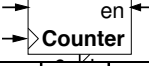
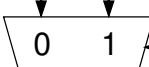
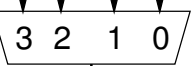
 
 
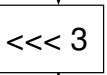
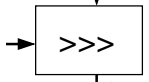
 

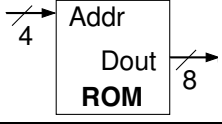
 
Timing Analysis – Class Exercise 2

Block diagram of a cryptographic hash function is shown below:



**Please note that this block diagram contains connections by name!
For example, two 8-bit buses denoted by a' are assumed to be connected.**

Assume the following notation and timing parameters of basic components:

Symbol	Logic/Arithmetic Component	Notation for a delay	Value of the delay
	Register	d_{REG}	1 ns
	Counter	d_{COUNT}	1 ns
	2-to-1 Multiplexer	d_{MUX2}	3 ns
	4-to-1 Multiplexer	d_{MUX4}	4 ns
	Adder modulo 2^8 (8-bit adder with carry out discarded) Adder modulo 2^4 (4-bit adder with carry out discarded)	d_{ADD8} d_{ADD4}	9 ns 5 ns
	Multiplier modulo 2^8 (8-bit multiplier with the MSB of the result discarded)	d_{MUL8}	15 ns
	Rotator by a constant	d_{CROT}	0 ns
	Variable rotator of an 8-bit input	d_{VRROT}	9 ns
	6-bit Comparator with a constant	d_{COMP6}	7 ns
	Bitwise XOR	d_{XOR}	2 ns
	16x8 ROM	$d_{ROM16x8}$	5 ns
	Concatenation	d_{CONC}	0 ns

Additionally, assume that the setup time of all registers is $t_{setup} = 1$ ns.

Tasks:

Determine the critical path of this circuit and express it in terms of a sum of variables representing delays and setup times of all major components.

Calculate:

1. Critical path delay
2. Minimum clock period
3. Maximum clock frequency
4. Slack for the target clock frequency equal to 25 MHz.

Timing Analysis – Class Exercise 2

Solutions

Question:

Determine the critical path of this circuit and express it in terms of a sum of variables representing delays and setup times of all major components.

Answer:

$$d_{\text{critical_path}} = d_{\text{REG}} + d_{\text{MUX4}} + d_{\text{ADD4}} + d_{\text{MUL8}} + d_{\text{XOR}} + d_{\text{MUX2}} + t_{\text{setup}}$$

Calculations:

1. Critical path delay

$$d_{\text{critical_path}} = (1 + 4 + 5 + 15 + 2 + 3 + 1) \text{ ns} = 31 \text{ ns}$$

2. Minimum clock period

$$T_{\text{clk}} = d_{\text{critical_path}} = 31 \text{ ns}$$

3. Maximum clock frequency

$$F_{\text{clk}} = 1/T_{\text{clk}} = 1/31 \text{ ns} = 1000/31 \text{ MHz} = 32.3 \text{ MHz}$$

4. Slack for the target clock frequency equal to 25 MHz.

$$\text{Slack} = 1/(25 \text{ MHz}) - 31 \text{ ns} = 40 \text{ ns} - 31 \text{ ns} = 9 \text{ ns}$$