


Software Implementation of Sensitization Attacks on Obfuscated Circuits

By John McLaughlin
ECE 646 Project Presentation

Theoretical Background

Key-based Hardware Obfuscation

 - Randomly add extra gates into a digital circuit
- One of the inputs to these gates is a “key” input
- Without the proper key, the circuit will malfunction



Sensitization Attack

- Determining key bits by “sensitizing” them to outputs
- Attacker has a fully functioning chip with unknown, accurately loaded key
- Attacker has chip’s netlist with key gates, but unknown key
- Find input sequence that propagates a key bit to an output in the netlist
- Check output of other chip when applying that input sequence
- Repeat for each key bit






Project

Description of Project

 
- Python script that performs a sensitization attack
- Input: .bench file, describes a digital circuit at gate level
- Output: Results of sensitization attack for each key bit



Finding propagating values

- Propagate_forward(input1)
 - Check type of gate input1 is going to
 - Set other input, input2, to **propagating value**
 - Propagate_backward(input2)
 - Other input propagated backward?
 - Yes: Is gate output a circuit output?
 - Yes: Return true
 - No: Propagate_forward(gate output)
 - No: Return false



PROPAGATING VALUES	
AND	1
OR	0
XOR	0
XNOR	1

 

Finding muting values


- Propagate_backward(wire)
 - Check gate type that wire is outputting from
 - Are any of the inputs key bits?
 - Yes: Set other input to **muting value**
 - Otherwise, set gate inputs to appropriate values
 - Is the gate input a circuit input?
 - Yes: Set circuit input, return true
 - No: Propagate_backward(input)

MUTING VALUES	
AND	0
NAND	0
OR	1
NOR	1

  

Algorithm -- Main Loop

 
- Loop i through `unsolved_keys[]`
 - `Propagate_forward(unsolved_keys[i])`
 - Did key propagate to output?
 - Yes: Print out results
 - Set key value
 - Set $i = 0$
 - No: Print that key is not sensitizable



Discoveries




Discoveries

 - Muting inputs to XOR, XNOR, or NOT gates require an extra gate (AND, OR, NAND, NOR)
- Cannot perform sensitization attacks on circuits with only XOR, XNOR, and NOT gates



Discoveries (2)

   - Propagating through NOR, NAND, or NOT gates require extra gates
 - NOR and NAND gates propagate the opposite value
 - Add a NAND or XOR gate to first gate's output, feed a 1 to other input, or
 - Add a NOR or XNOR gate to first gate's output, feed a 0 to other input, or
 - Add a NOT gate to first gate's output



End

- Special Thanks to
 - Dr. Sasan
 - Dr. Gaj
 - Shervin Roshanisefat
 - Hadi Mardani Kamali
 - Kimia Zamiri Azar





Questions?