ECE 545
Lecture 5

Dataflow Modeling in VHDL


Required reading

- P. Chu, *RTL Hardware Design using VHDL*

Chapter 4, Concurrent Signal Assignment Statements of VHDL


Chapter 6.3, Realization of VHDL Data Types

Types of VHDL Description

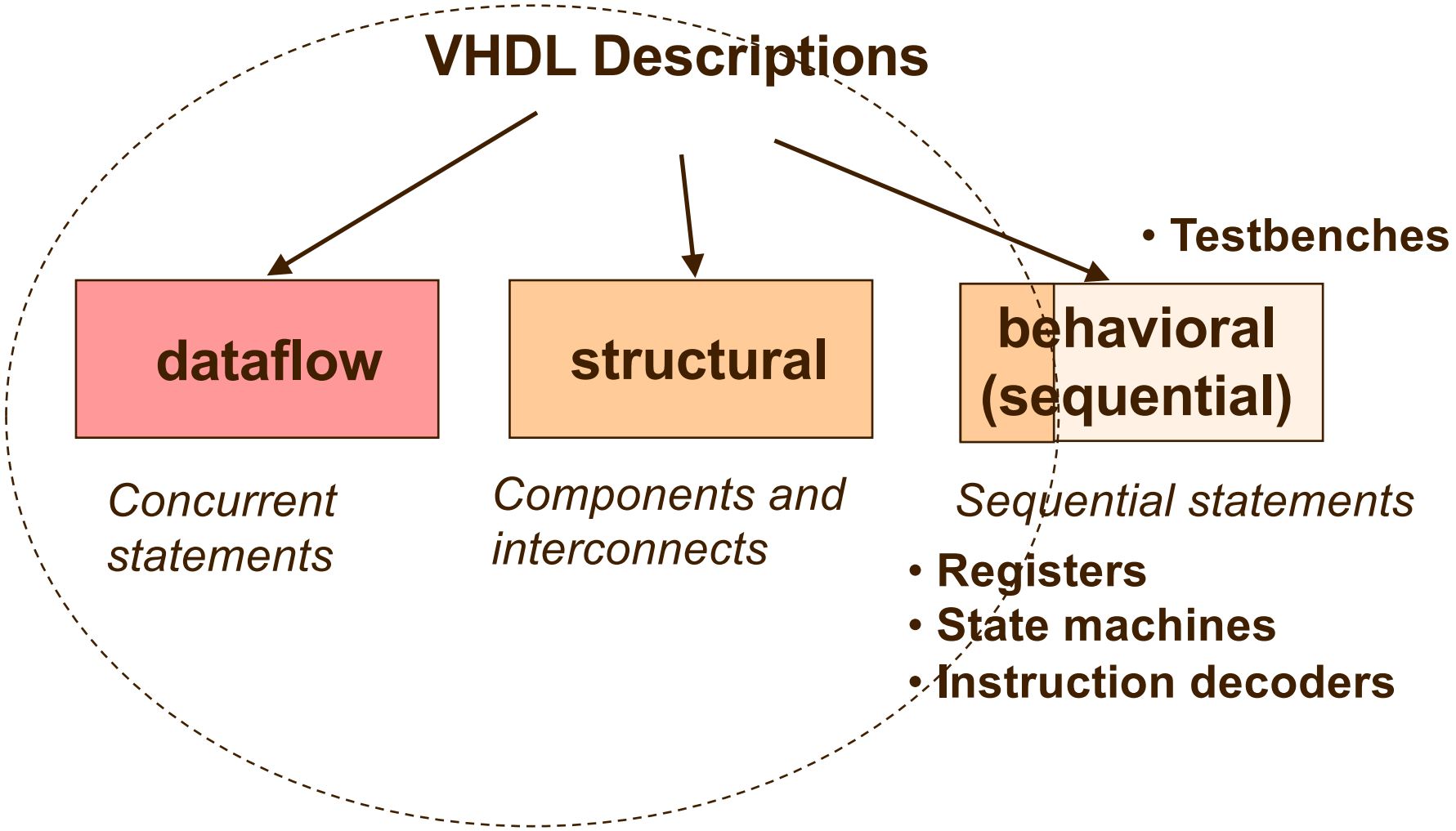


Synthesizable VHDL

Dataflow VHDL Description

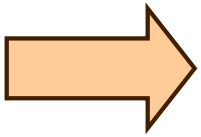


VHDL code synthesizable

Dataflow VHDL Description

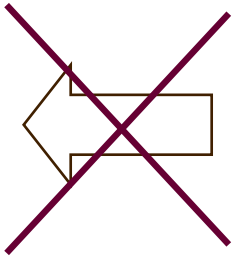

VHDL code synthesizable

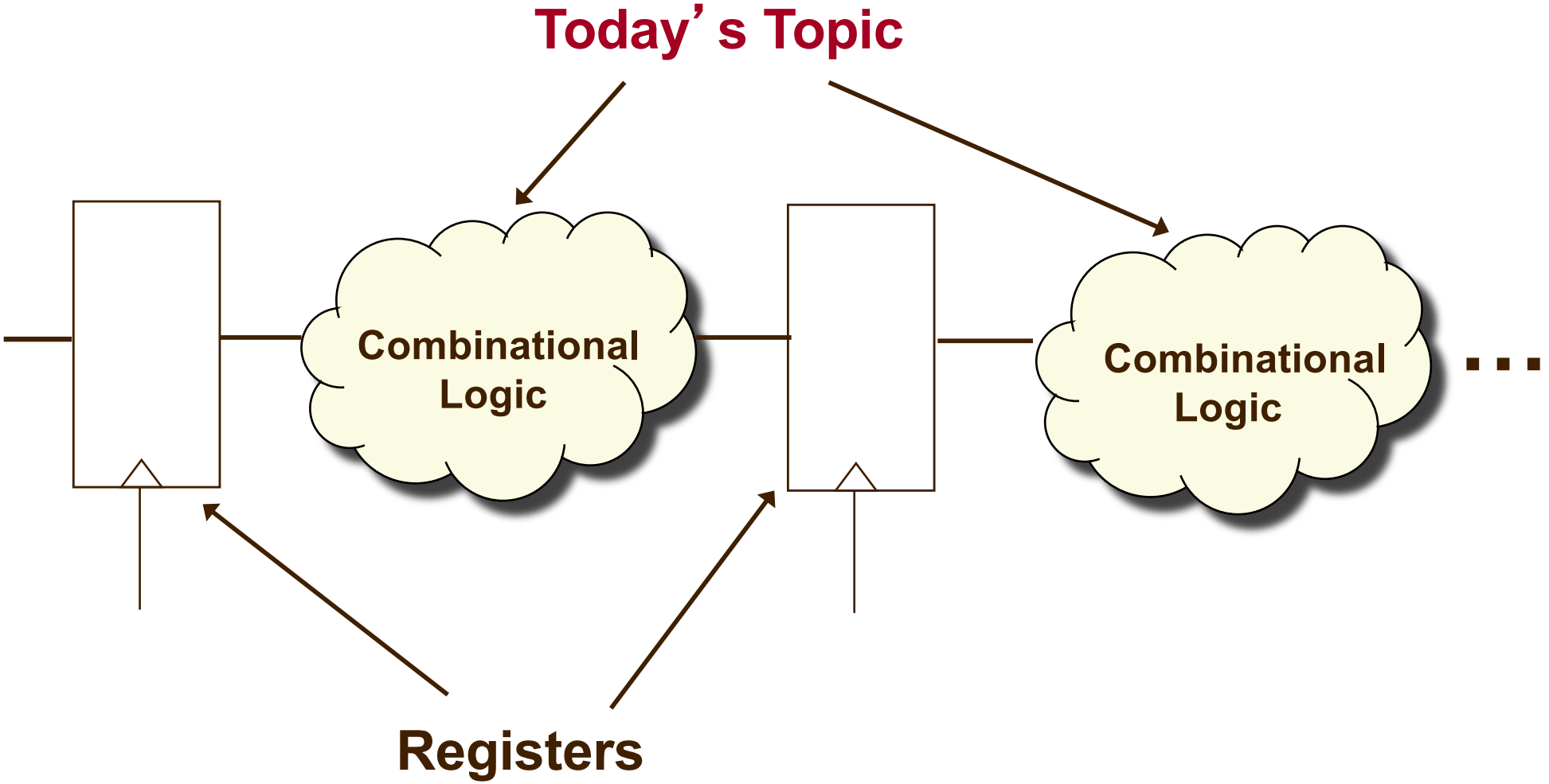Register Transfer Level (RTL) Design Description



Data-Flow VHDL

Concurrent Statements

- **simple concurrent signal assignment**
  (⇐)
- **conditional concurrent signal assignment**
  (when-else)
- **selected concurrent signal assignment**
  (with-select-when)

Simple concurrent signal assignment

<=

```
target_signal <= expression;
```

Conditional concurrent signal assignment

When - Else

```
target_signal <= value1 when condition1 else
                 value2 when condition2 else
                   . . .
                 valueN-1 when conditionN-1 else
                 valueN;
```

Selected concurrent signal assignment


With –Select-When

```
with choice_expression select
   target_signal <= expression1 when choices_1,
                    expression2 when choices_2,
                        . . .
                    expressionN when choices_N;
```

Data-Flow VHDL

Concurrent Statements

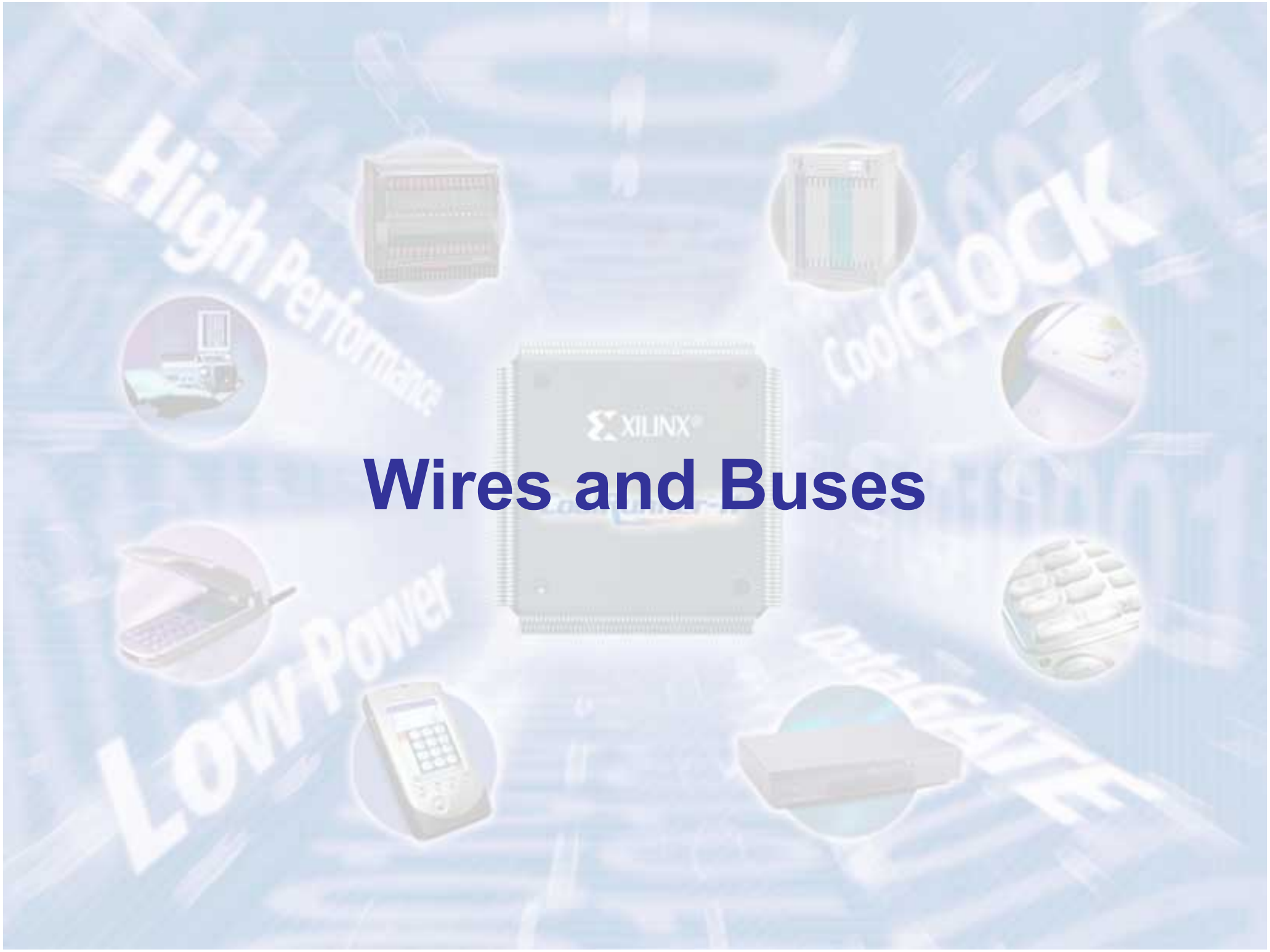
- **simple concurrent signal assignment (⇐)**
- **conditional concurrent signal assignment (when-else)**
- **selected concurrent signal assignment (with-select-when)**




Wires and Buses

Signals


SIGNAL a : STD_LOGIC;

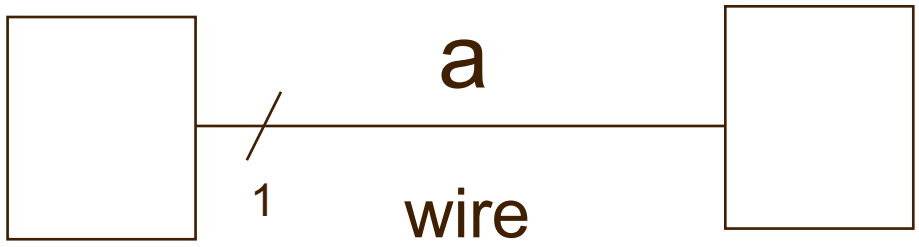

SIGNAL b : STD_LOGIC_VECTOR(7 DOWNTO 0);

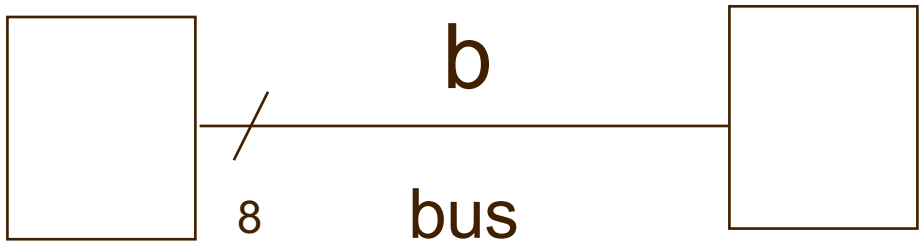


Merging wires and buses

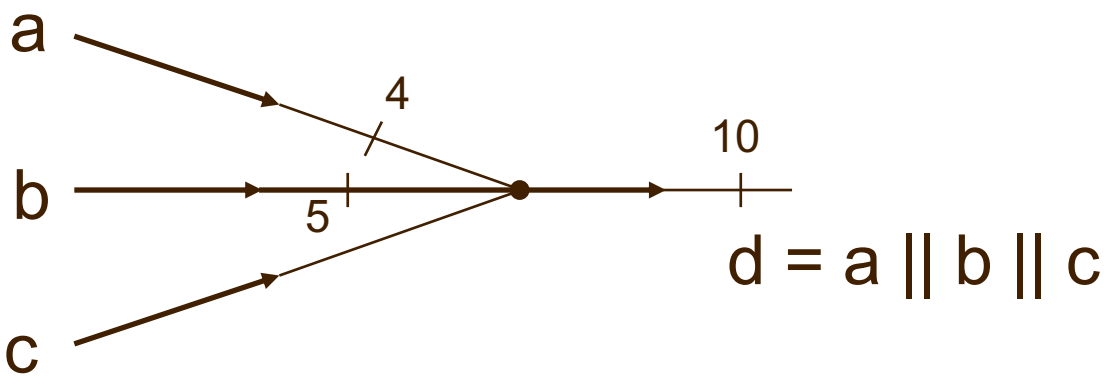


```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNTO 0);
SIGNAL c: STD_LOGIC;
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNTO 0);


d <=
```


Merging wires and buses

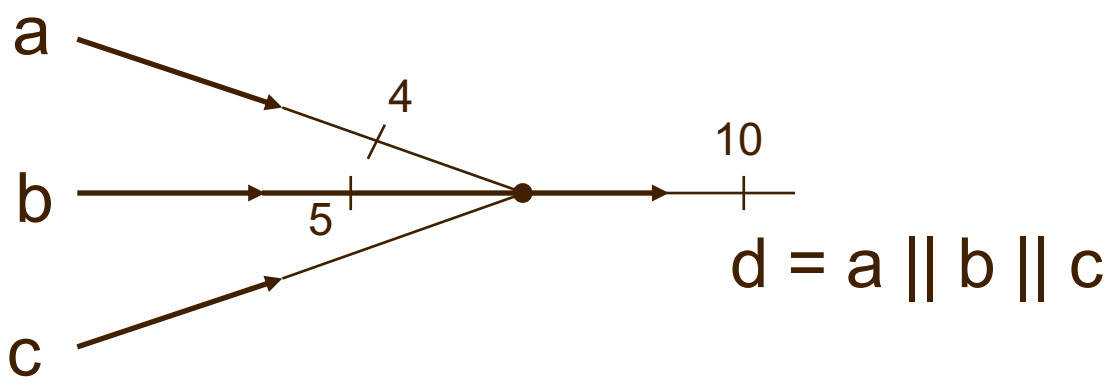


```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNTO 0);
SIGNAL c: STD_LOGIC;
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNTO 0);

d <= a & b & c;
```


Splitting buses

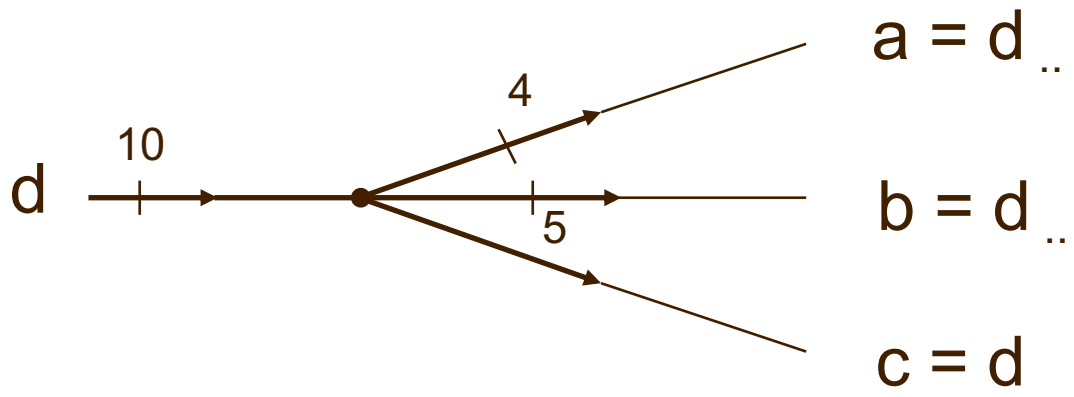


```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNTO 0);
SIGNAL c: STD_LOGIC;
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNTO 0);

a <=
b <=
c <=
```


Splitting buses

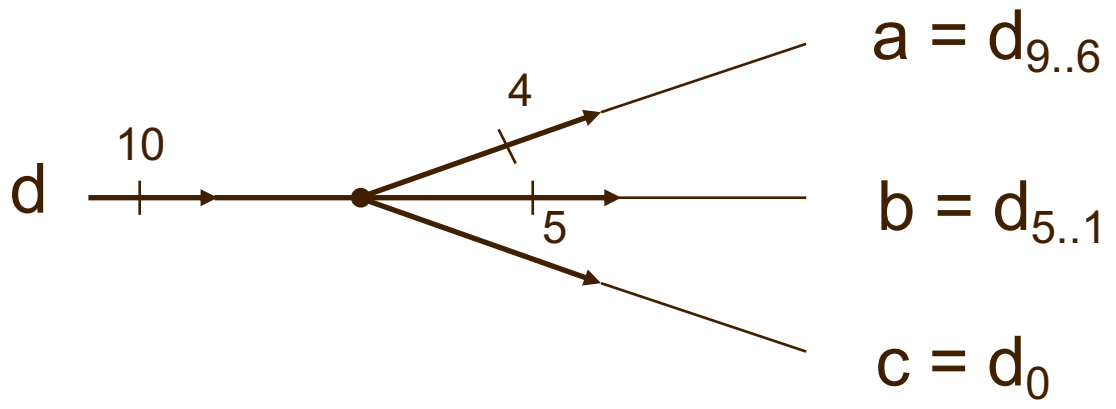


```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL b: STD_LOGIC_VECTOR(4 DOWNTO 0);
SIGNAL c: STD_LOGIC;
SIGNAL d: STD_LOGIC_VECTOR(9 DOWNTO 0);

a <= d(9 downto 6);
b <= d(5 downto 1);
c <= d(0);
```

Data-flow VHDL: Example

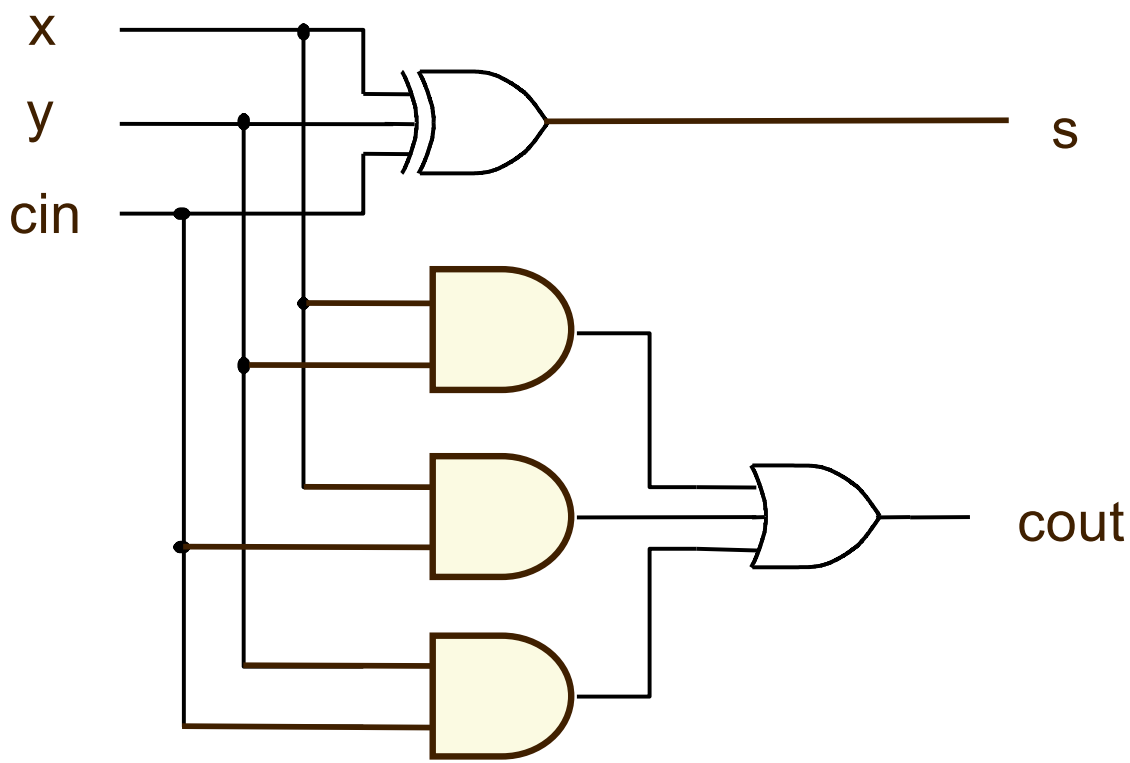

Data-flow VHDL: Example (1)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fulladd IS
        PORT ( x      : IN      STD_LOGIC ;
               y      : IN      STD_LOGIC ;
               cin    : IN      STD_LOGIC ;
               s      : OUT     STD_LOGIC ;
               cout   : OUT     STD_LOGIC ) ;
END fulladd ;
```

Data-flow VHDL: Example (2)

```
ARCHITECTURE dataflow OF fulladd IS
BEGIN
        s     <=  x XOR y XOR cin ;
        cout  <=  (x AND y) OR (cin AND x) OR (cin AND y) ;
END dataflow ;
```

equivalent to

```
ARCHITECTURE dataflow OF fulladd IS
BEGIN
        cout  <=  (x AND y) OR (cin AND x) OR (cin AND y) ;
        s     <=  x XOR y XOR cin ;
END dataflow ;
```

Logic Operators

- Logic operators



- Logic operators precedence



No Implied Precedence

Wanted: y **= ab + cd**

Incorrect

y <= a **and** b **or** c **and** d ;

equivalent to

y <= ((a **and** b) **or** c) **and** d ;


equivalent to

y = (ab + c)d

Correct

y <= (a **and** b) **or** (c **and** d) ;

arith_result <= a + b + c – 1;

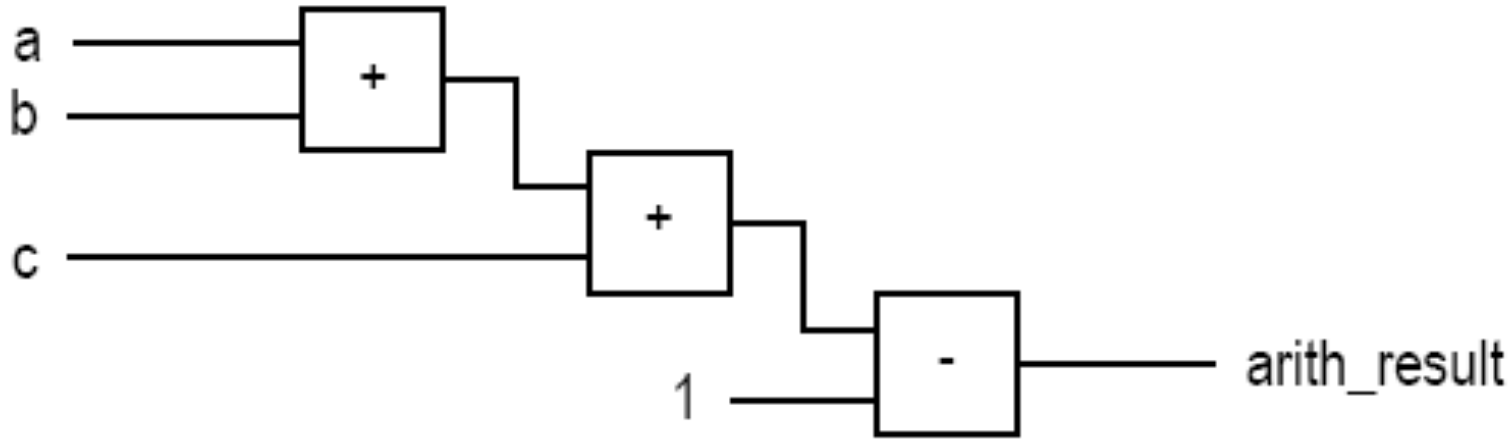

Signal assignment statement with a closed feedback loop

- a signal appears in both sides of a concurrent assignment statement
- E.g.,
  q <= ((**not q**) **and** (**not** en)) **or** (d **and** en);
- Syntactically correct
- Form a closed feedback loop
- Should be avoided

Data-Flow VHDL

Concurrent Statements

- **simple concurrent signal assignment (⇐)**
- **conditional concurrent signal assignment (when-else)**
- **selected concurrent signal assignment (with-select-when)**

Conditional concurrent signal assignment


When - Else

```
target_signal <= value1 when condition1 else
                 value2 when condition2 else
                   . . .
                 valueN-1 when conditionN-1 else
                 valueN;
```

Most often implied structure


When - Else
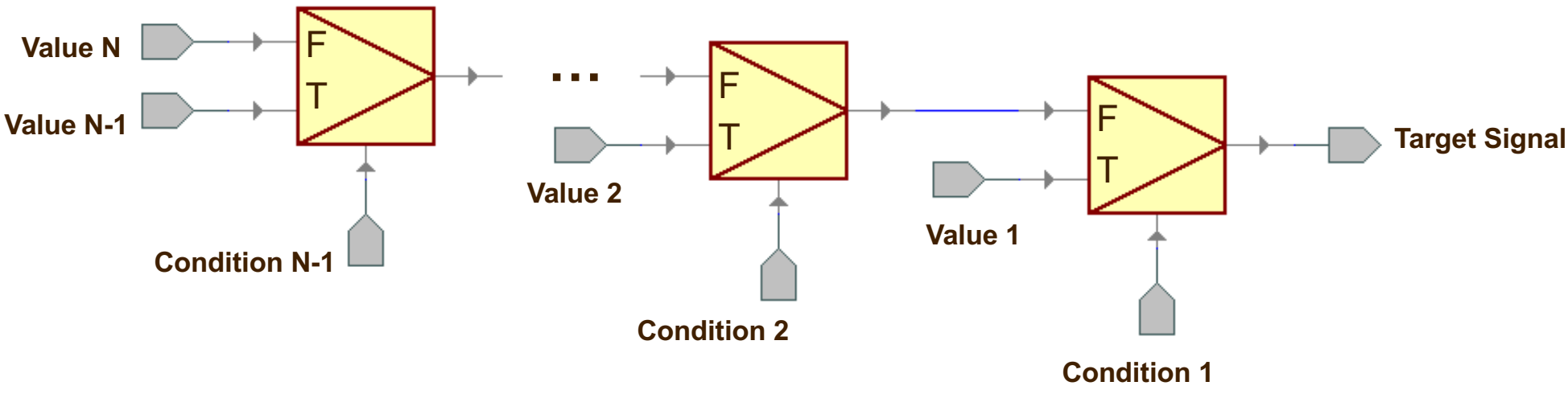
```
target_signal <= value1 when condition1 else
                 value2 when condition2 else
                    . . .
                 valueN-1 when conditionN-1 else
                 valueN;
```




2-to-1 “abstract” mux

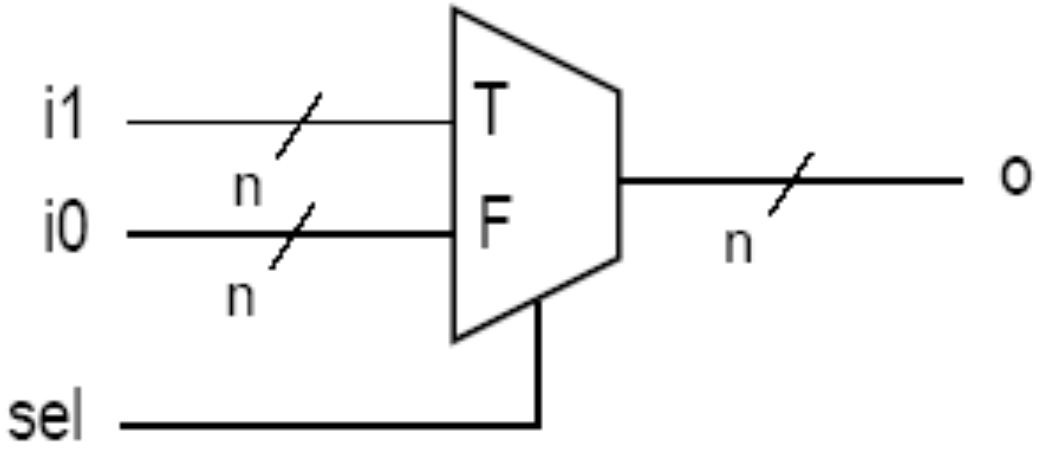
- sel has a data type of boolean
- If sel is true, the input from “T” port is connected to output.
- If sel is false, the input from “F” port is connected to output.




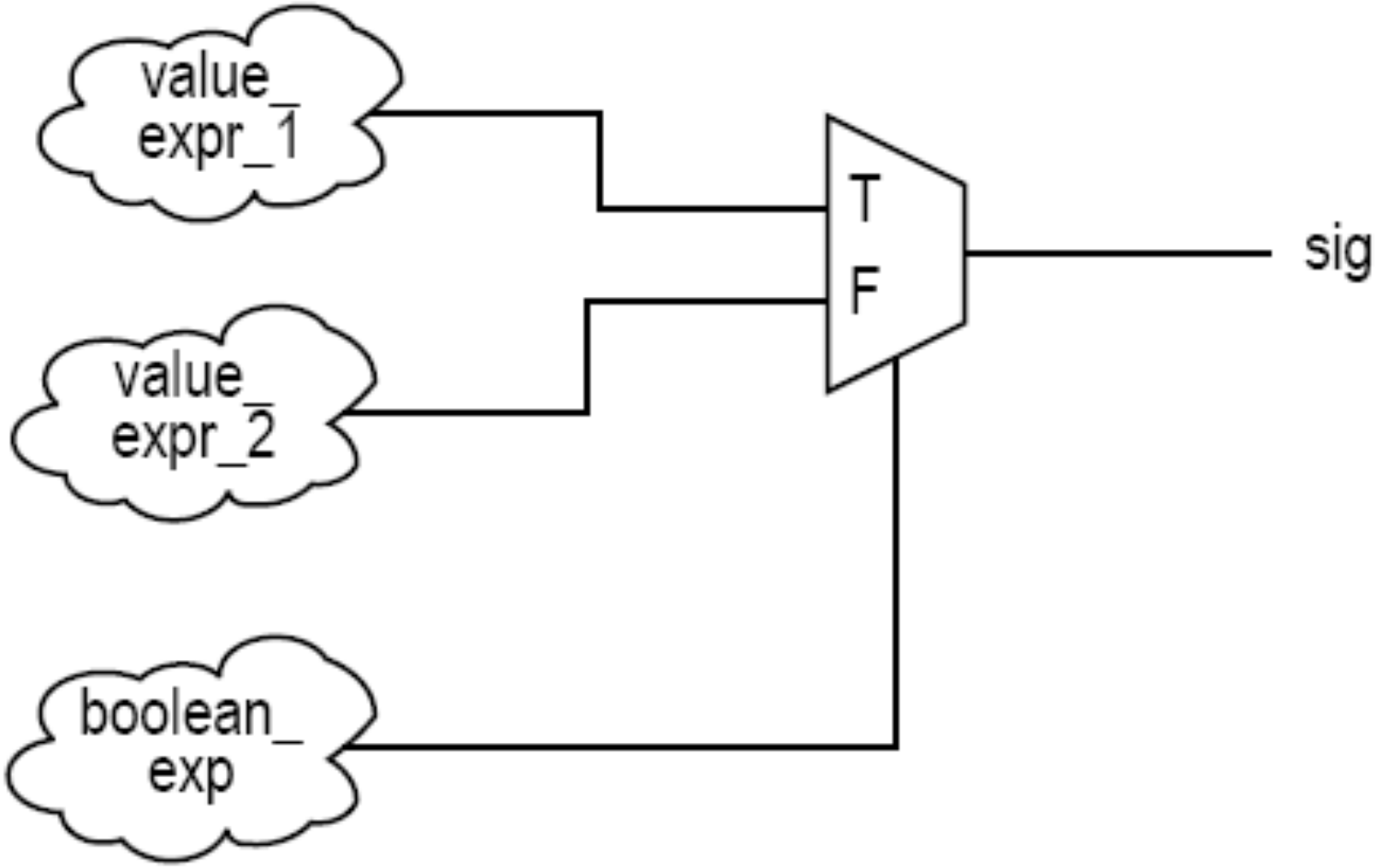
```
signal_name <= value_expr_1 when boolean_expr_1 else
               value_expr_2;
```


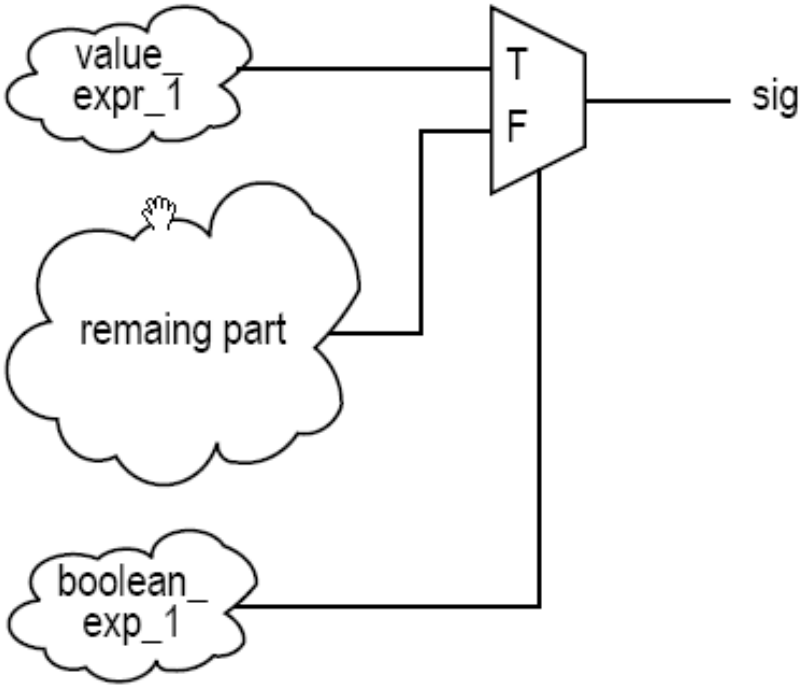
```
signal_name <= value_expr_1 when boolean_expr_1 else
               value_expr_2 when boolean_expr_2 else
               value_expr_3 when boolean_expr_3 else
               value_expr_4;
```




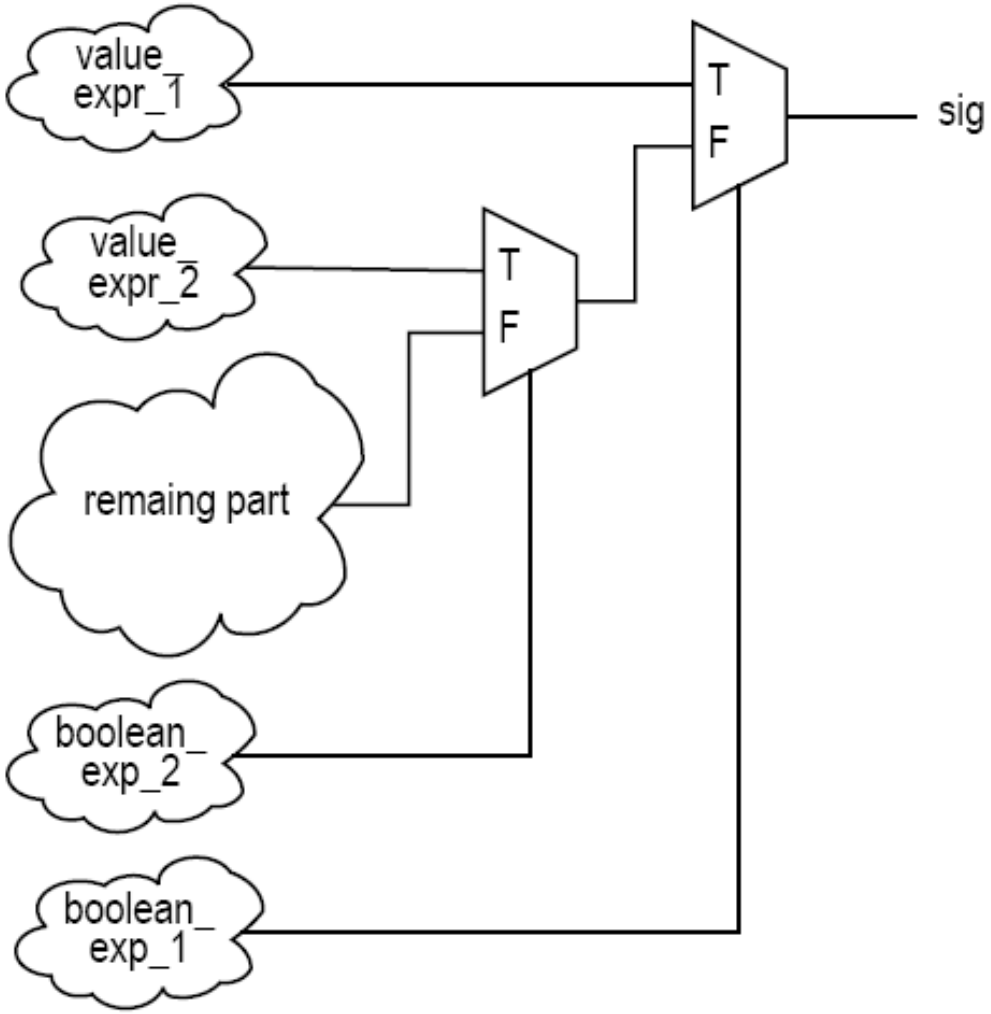


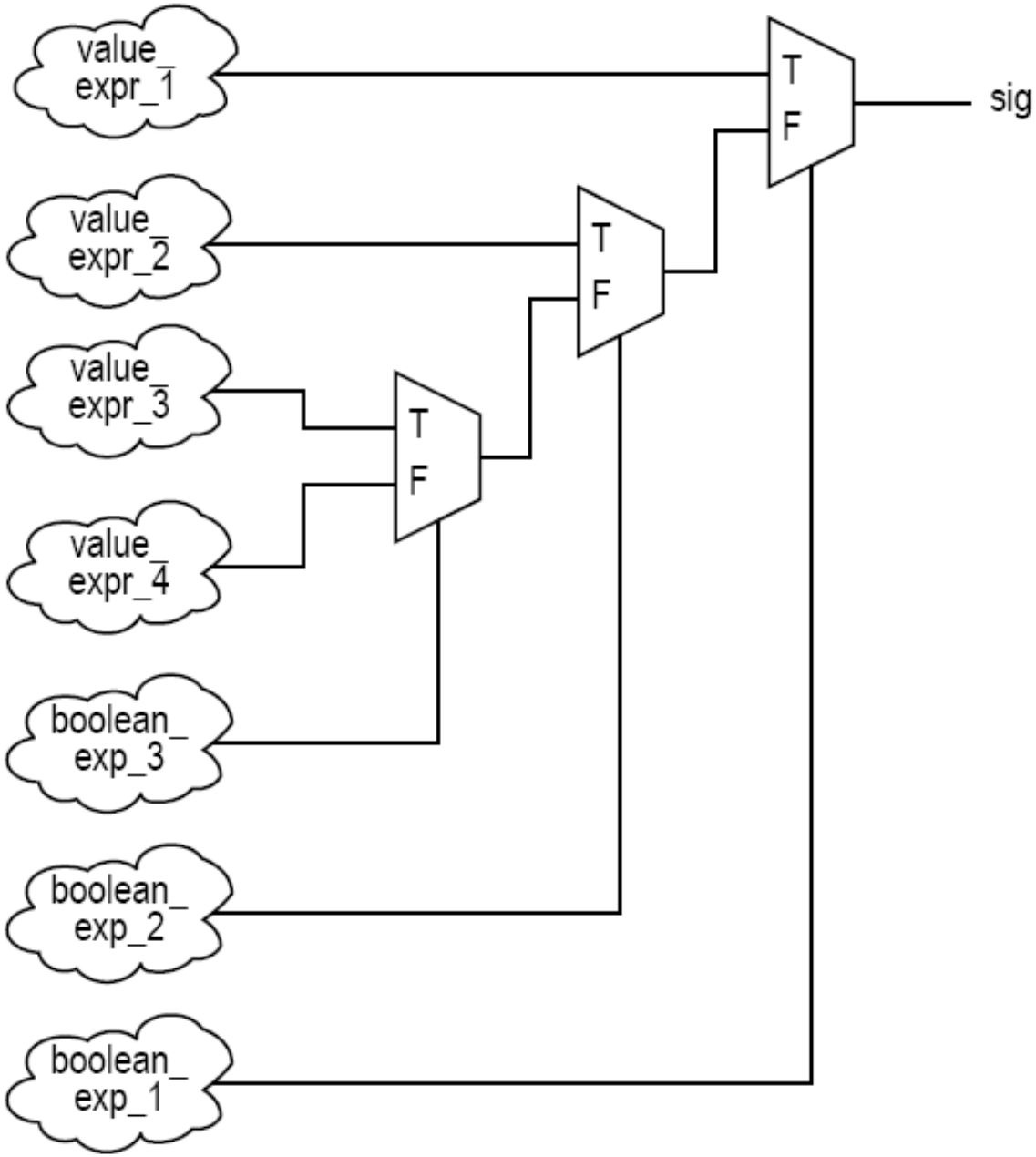
value_
expr_1
value_
expr_2
value_
expr_3
value_
expr_4
boolean_
exp_3
boolean_
exp_2
boolean_
exp_1
T
F
T
F
T
F
sig

- E.g.,
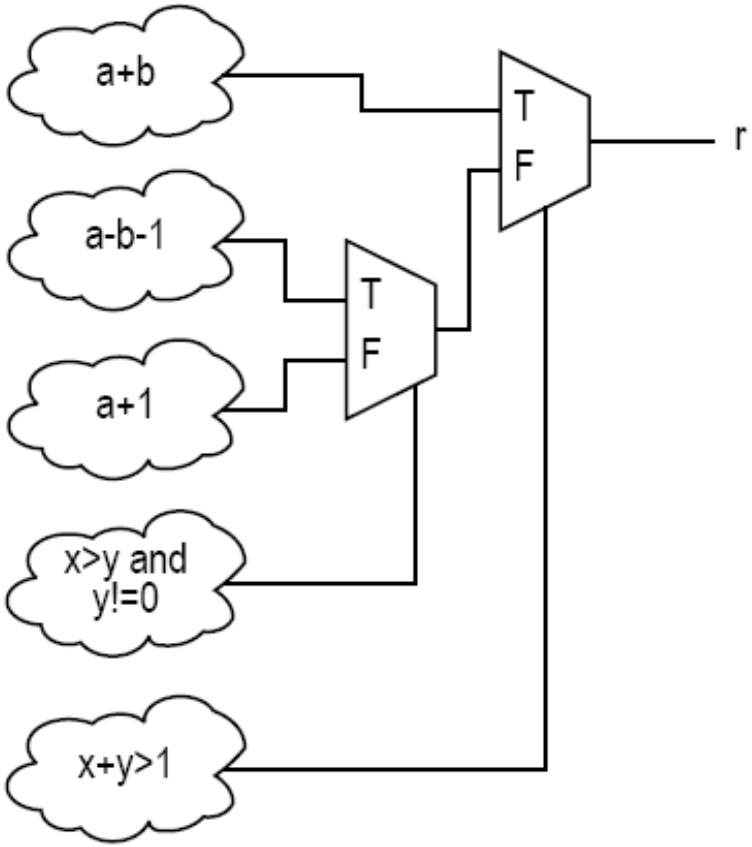
```
. . .
signal a,b,r: unsigned(7 downto 0);
signal x,y: unsigned(3 downto 0);
. . .
r <= a+b when x+y>1 else
     a-b-1 when x>y and y!=0 else
     a+1;
```



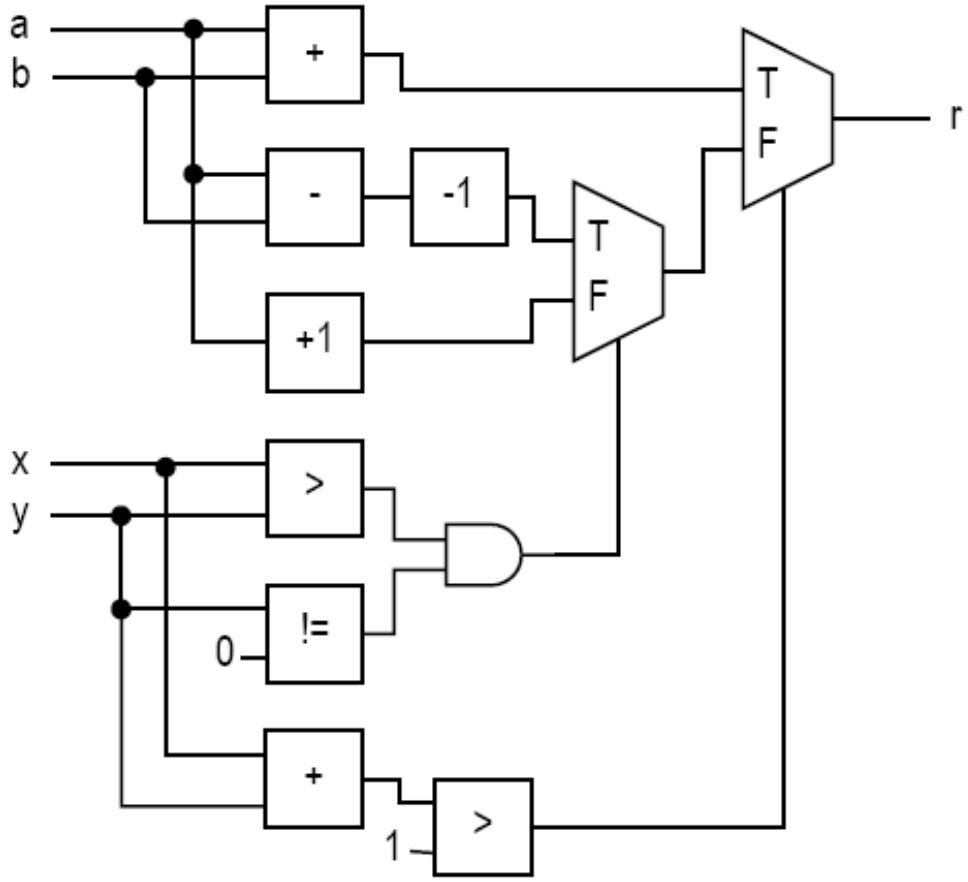

Signed and Unsigned Types

Behave exactly **like**

STD_LOGIC_VECTOR

plus, they determine whether a given vector should be treated as a signed or unsigned number.

Require


USE ieee.numeric_std.all;

Operators

- Relational operators

```
=      /=      <      <=      >      >=
```

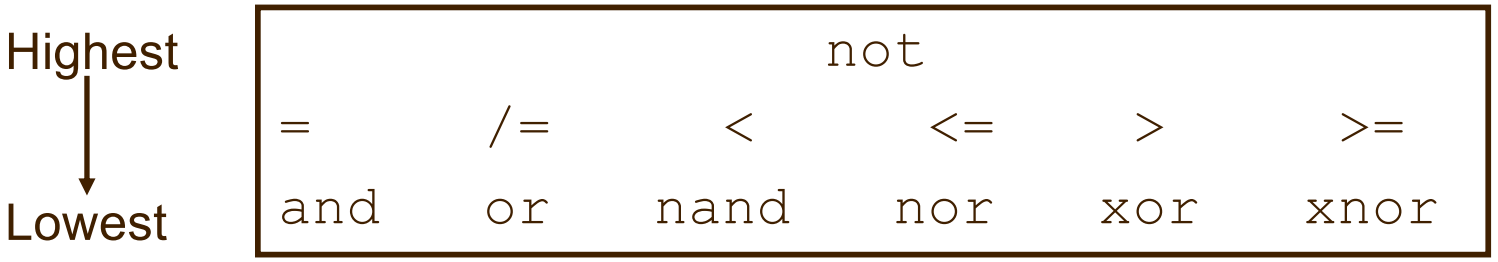- Logic and relational operators precedence



Priority of logic and relational operators

compare a = bc

Incorrect

… when a = b **and** c else …

equivalent to

… when (a = b) **and** c else …

Correct

… when a = (b **and** c) else …

Data-Flow VHDL

Concurrent Statements

- **simple concurrent signal assignment (⇐)**
- **conditional concurrent signal assignment (when-else)**
- **selected concurrent signal assignment (with-select-when)**

Selected concurrent signal assignment


With –Select-When

```
with choice_expression select
   target_signal <= expression1 when choices_1,
                    expression2 when choices_2,
                        . . .
                    expressionN when choices_N;
```

Most Often Implied Structure

With –Select-When
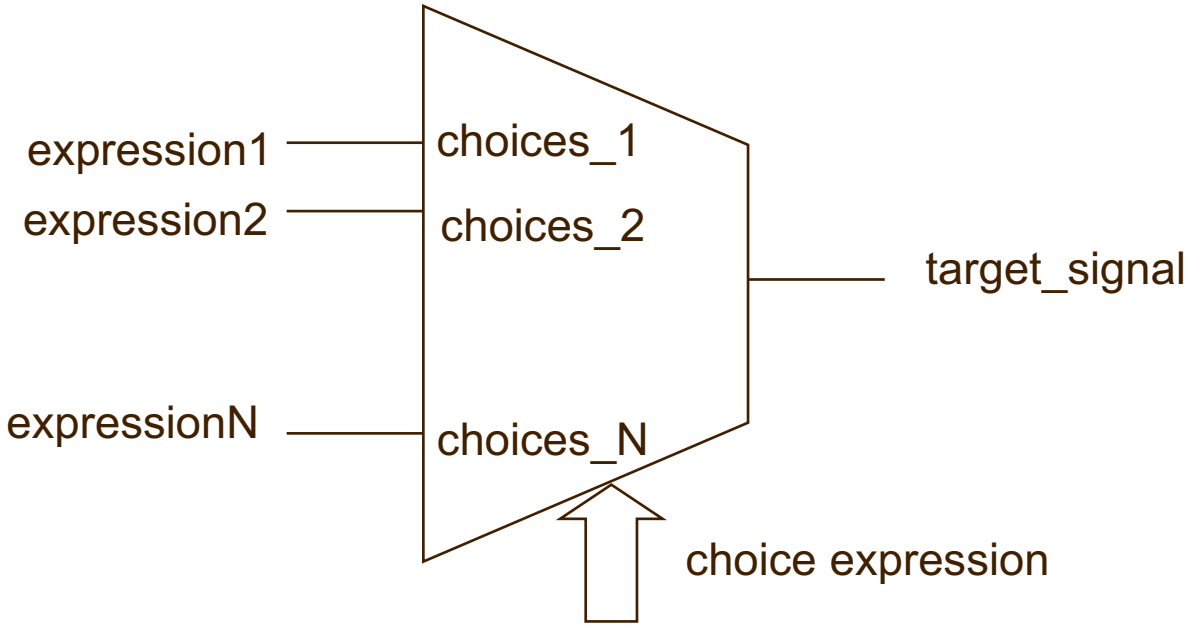
```
with choice_expression select
   target_signal <= expression1 when choices_1,
                    expression2 when choices_2,
                        . . .
                    expressionN when choices_N;
```



Allowed formats of *choices_k*

WHEN value

WHEN value_1 | value_2 | .... | value N

WHEN OTHERS

Allowed formats of *choice_k - example*

```
WITH sel SELECT
     y <= a WHEN "000",
           c WHEN "001" | "111",
           d WHEN OTHERS;
```

Syntax

- Simplified syntax:

```
with select_expression select
    signal_name <=
        value_expr_1 when choice_1,
        value_expr_2 when choice_2,
        value_expr_3 when choice_3,
            . . .
        value_expr_n when choice_n;
```

- select_expression
  - Discrete type or 1-D array
  - With finite possible values
- choice_i
  - A value of the data type
- Choices must be
  - mutually exclusive
  - all inclusive
  - **others** can be used as last choice_i

E.g., 4-to-1 mux

```
architecture sel_arch of mux4 is
begin
    with s select
      x <= a when "00",
           b when "01",
           c when "10",
           d when others;
end sel_arch ;
```

input s	output x
0 0	a
0 1	b
1 0	c
1 1	d

- Can “11” be used to replace **others**?

```
with s select
   x <= a when "00",
        b when "01",
        c when "10",
        d when "11";
```

E.g., 2-to-2^2 binary decoder

```
architecture sel_arch of decoder4 is
begin
    with sel select
      x <= "0001" when "00",
           "0010" when "01",
           "0100" when "10",
           "1000" when others;
end sel_arch ;
```

input s	output x
0 0	0001
0 1	0010
1 0	0100
1 1	1000

E.g., simple ALU

```
architecture sel_arch of simple_alu is
   signal sum, diff, inc: std_logic_vector(7 downto 0);
begin
   inc <= std_logic_vector(signed(src0)+1);
   sum <= std_logic_vector(signed(src0)+signed(src1));
   diff <= std_logic_vector(signed(src0)-signed(src1));
   with ctrl select
      result <= inc            when "000"|"001"|"010"|"011",
                sum            when "100",
                diff           when "101",
                src0 and src1  when "110",
                src0 or src1   when others;
end sel_arch;
```

input ctrl	output result
0 – –	src0 + 1
1 0 0	src0 + src1
1 0 1	src0 - src1
1 1 0	src0 **and** src1
1 1 1	src0 **or** src1


E.g., Truth table

```
library ieee;
use ieee.std_logic_1164.all;
entity truth_table is
    port(
        a,b: in  std_logic;
        y: out   std_logic
    );
end truth_table;
architecture a of truth_table is
    signal tmp: std_logic_vector(1 downto 0);
begin
    tmp <= a & b;
    with tmp select
        y <= '0' when "00",
             '1' when "01",
             '1' when "10",
             '1' when others; -- "11"
end a;
```

input	output
a b	y
0 0	0
0 1	1
1 0	1
1 1	1


Conceptual implementation

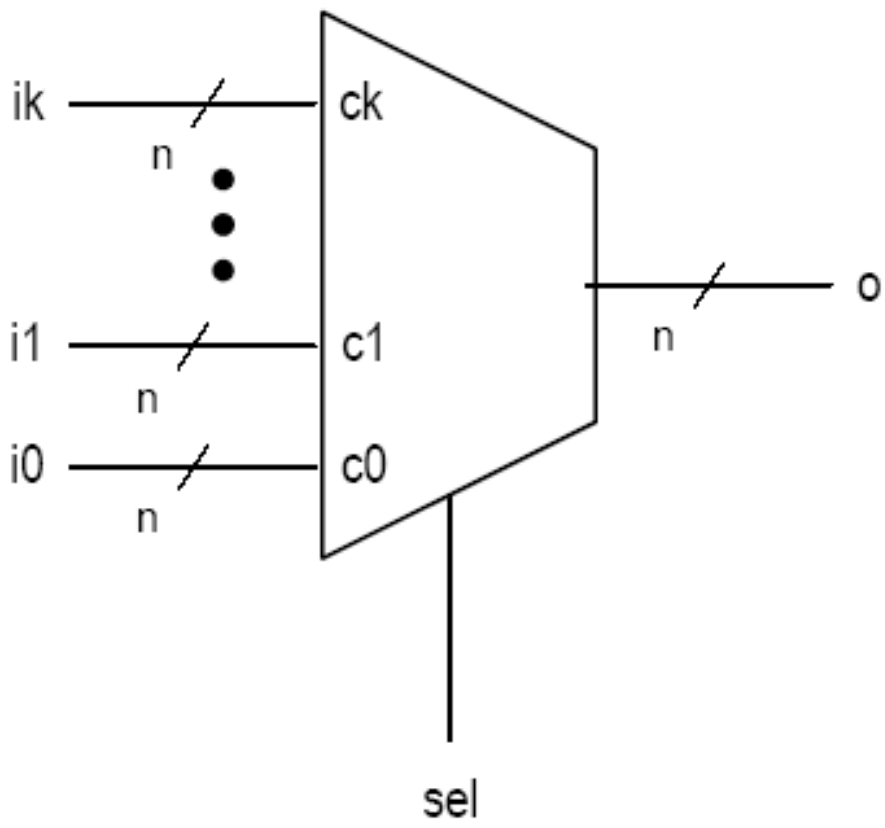- Achieved by a multiplexing circuit
- Abstract (k+1)-to-1 multiplexer
  - sel is with a data type of (k+1) values: c0, c1, c2, . . . , ck




– select_expression is with a data type of 5 values: c0, c1, c2, c3, c4

```
with select_expression select
    sig <= value_expr_0 when c0,
           value_expr_1 when c1,
           value_expr_n when others;
```

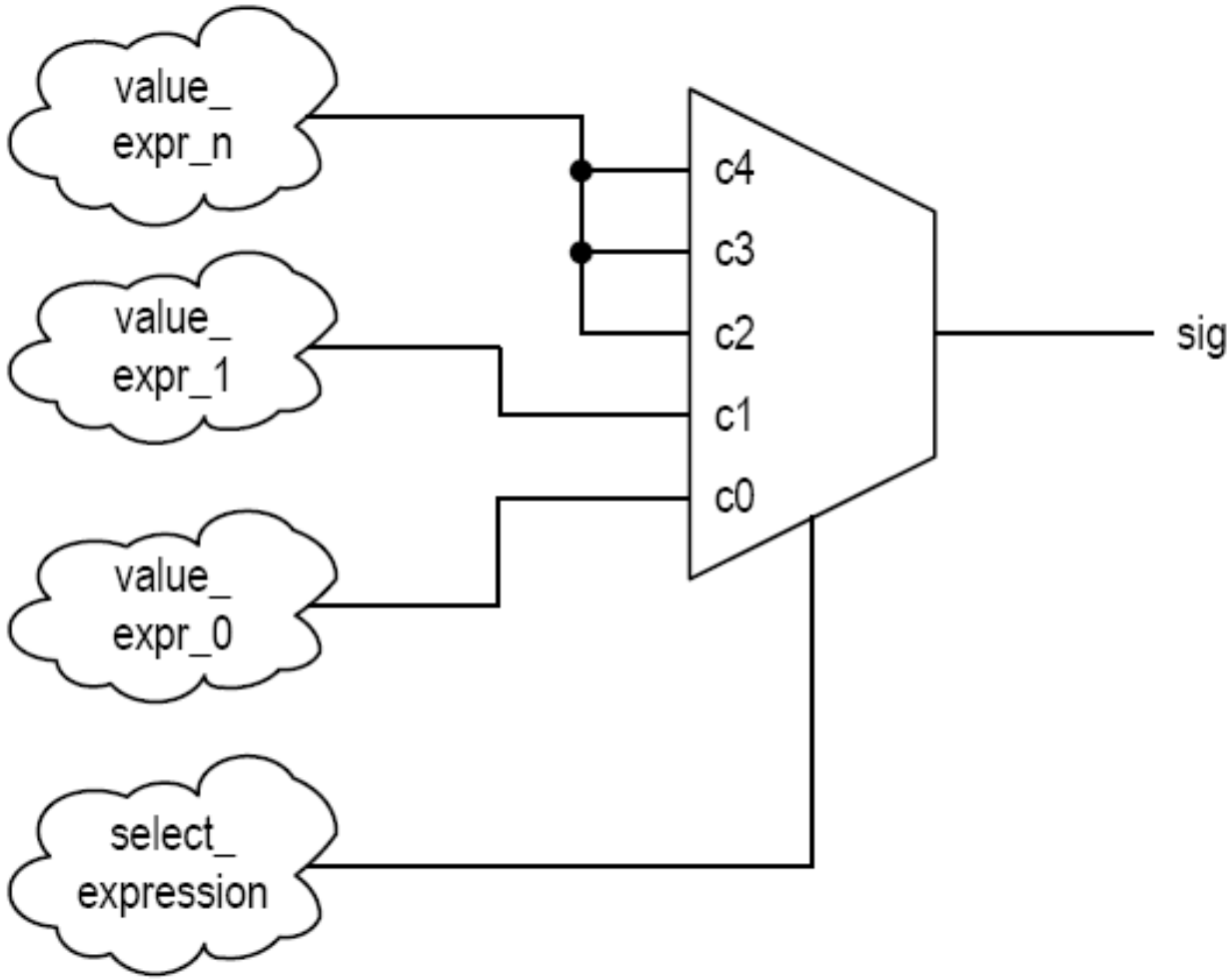
value_
expr_n
value_
expr_1
value_
expr_0
select_
expression
c4
c3
c2
c1
c0
sig

- E.g.,
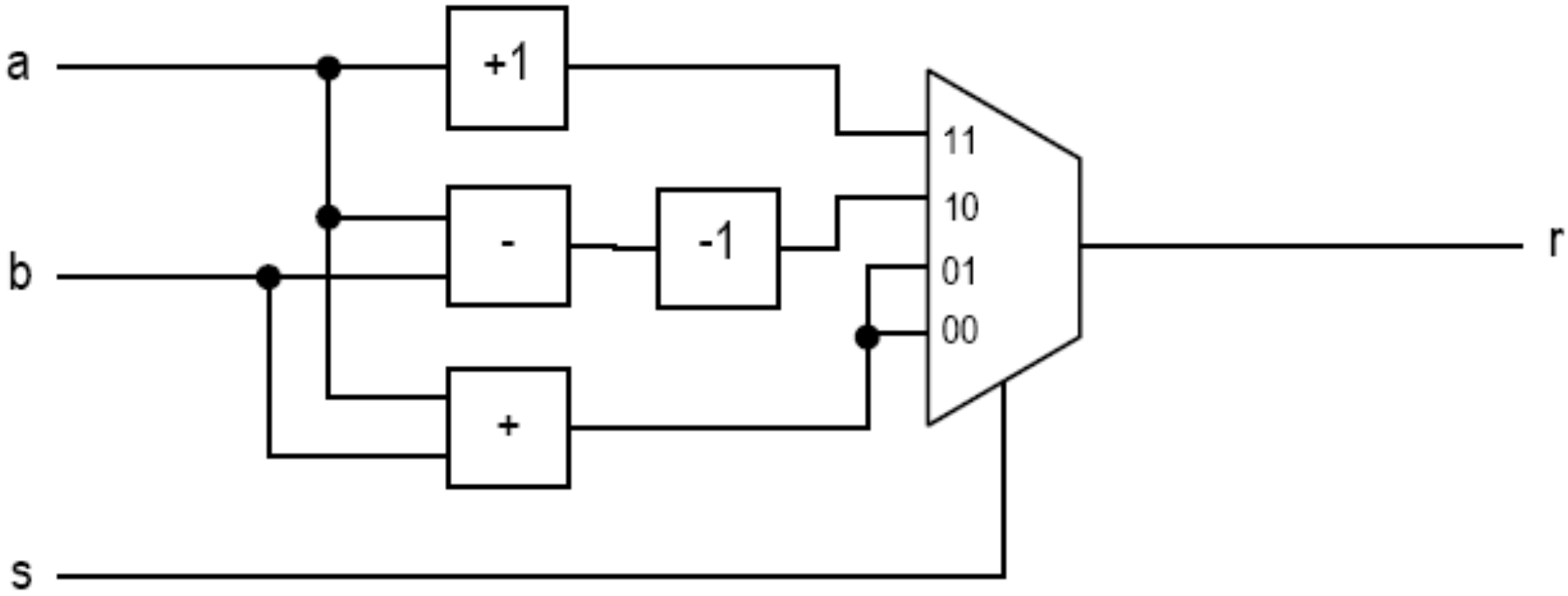
```
signal a,b,r: unsigned(7 downto 0);
signal s: std_logic_vector(1 downto 0);
    . . .
    with s select
        r <= a+1    when "11",
             a-b-1  when "10",
             a+b    when others;
```



3. Conditional vs. selected signal assignment

- Conversion between conditional vs. selected signal assignment
- Comparison

From selected assignment to conditional assignment

```
with sel select
    sig <= value_expr_0 when c0,
           value_expr_1 when c1|c3|c5,
           value_expr_2 when c2|c4,
           value_expr_n when others;
```

```
sig <=
    value_expr_0 when (sel=c0) else
    value_expr_1 when (sel=c1) or (sel=c3) or (sel=c5) else
    value_expr_2 when (sel=c2) or (sel=c4) else
    value_expr_n;
```

From conditional assignment to selected assignment

```
sig <= value_expr_0 when bool_exp_0 else
       value_expr_1 when bool_exp_1 else
       value_expr_2 when bool_exp_2 else
       value_expr_n;
```

```
sel(2) <= '1' when bool_exp_0 else '0';
sel(1) <= '1' when bool_exp_1 else '0';
sel(0) <= '1' when bool_exp_2 else '0';
with sel select
   sig <= value_expr_0 when "100"|"101"|"110"|"111",
          value_expr_1 when "010"|"011",
          value_expr_2 when "001",
          value_expr_n when others;
```

Comparison

- Selected signal assignment:
  - good match for a circuit described by a functional table
  - E.g., binary decoder, multiplexer
  - Less effective when an input pattern is given a preferential treatment

- Conditional signal assignment:
  - good match for a circuit that needs to give preferential treatment for certain conditions or to prioritize the operations
  - E.g., priority encoder
  - Can handle complicated conditions. e.g.,

```
pc_next <=
    pc_reg + offset when (state=jump and a=b) else
    pc_reg + 1 when (state=skip and flag='1') else
. . .
```

– May “over-specify” for a functional table based circuit.

– E.g., mux

```
x <= a when (s="00") else
     b when (s="01") else
     c when (s="10") else
     d;

x <= c when (s="10") else
     a when (s="00") else
     b when (s="01") else
     d;

x <= c when (s="10") else
     b when (s="01") else
     a when (s="00") else
     d;
```

when-else vs. with-select-when (1)

"when-else" should be used when:

1) there is only one condition (and thus, only one else), as in the 2-to-1 MUX

2) conditions are independent of each other (e.g., they test values of different signals)

3) conditions reflect priority (as in priority encoder); one with the highest priority need to be tested first.

when-else vs. with-select-when (2)

"with-select-when" should be used when there is

1) more than one condition
2) conditions are closely related to each other (e.g., represent different ranges of values of the same signal)
3) all conditions have the same priority (as in the 4-to-1 MUX).

Use of '-'

- In conventional logic design
  - '-' as input value: shorthand to make table compact
  - E.g.,

input	output
req	code
1 0 0	10
1 0 1	10
1 1 0	10
1 1 1	10
0 1 0	01
0 1 1	01
0 0 1	00
0 0 0	00

input	output
req	code
1 – –	10
0 1 –	01
0 0 1	00
0 0 0	00

– '-' as output value: help simplification

– E.g.,

'-' assigned to 1: a + b

'-' assigned to 0: a'b + ab'

input $a\ b$	output f
0 0	0
0 1	1
1 0	1
1 1	–

Use ‘-’ in VHDL

- As input value (against our intuition):
- Wrong:

```
y <= "10" when req="1--" else
     "01" when req="01-" else
     "00" when req="001" else
     "00";
```

- Fix #1:

```
y <= "10" when req(2)='1' else
     "01" when req(2 downto 1)="01" else
     "00" when req(2 downto 0)="001" else
     "00";
```

- Fix #2:

```
. . .
use ieee.numeric_std.all;
. . .
y <= "10" when std_match(req,"1--") else
     "01" when std_match(req,"01-") else
     "00" when std_match(req,"001") else
     "00";
```

- Wrong:

```
with req select
    y <= "10" when "1--",
         "01" when "01-",
         "00" when "001",
         "00" when others;
```

- Fix:


```
with req select
    y <= "10" when "100"|"101"|"110"|"111",
         "00" when "010"|"011",
         "00" when others;
```

- ‘-’ as an output value in VHDL
- May work with some software

```
sel <= a & b;
with sel select
    y <= '0' when "00",
         '1' when "01",
         '1' when "10",
         '-' when others;
```

Use and synthesis of ‘Z’

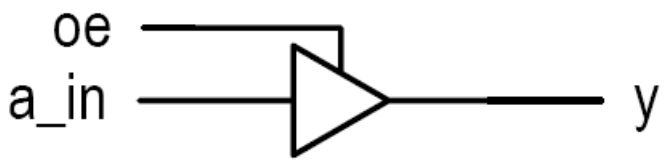- Tri-state buffer:
  - Output with “high-impedance”
  - Not a value in Boolean algebra
  - Need special output circuitry (tri-state buffer)



oe	y
0	Z
1	a_in

- Major application:
  - Bi-directional I/O pins
  - Tri-state bus
- VHDL description:


```
y <= 'Z' when oe='1' else
      a_in;
```

- ‘Z’ cannot be used as input or manipulated

```
f <= 'Z' and a;
y <= data_a when in_bus='Z' else
     data_b;
```


- Separate tri-state buffer from regular code:
  - Less clear:

```
with sel select
   y <= 'Z' when "00",
        '1' when "01"|"11",
        '0' when others;
```

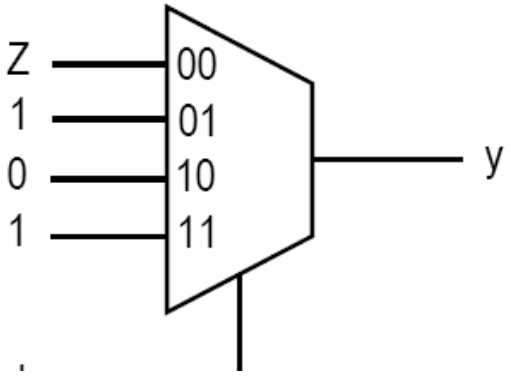


  - better:

```
with sel select
   tmp <= '1' when "01"|"11",
          '0' when others;
  y <= 'Z' when sel="00" else
       tmp;
```

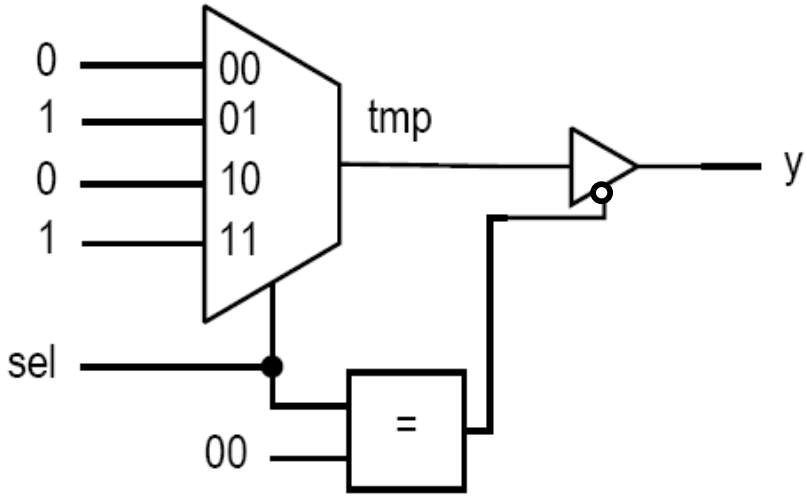


Bi-directional i/o pins

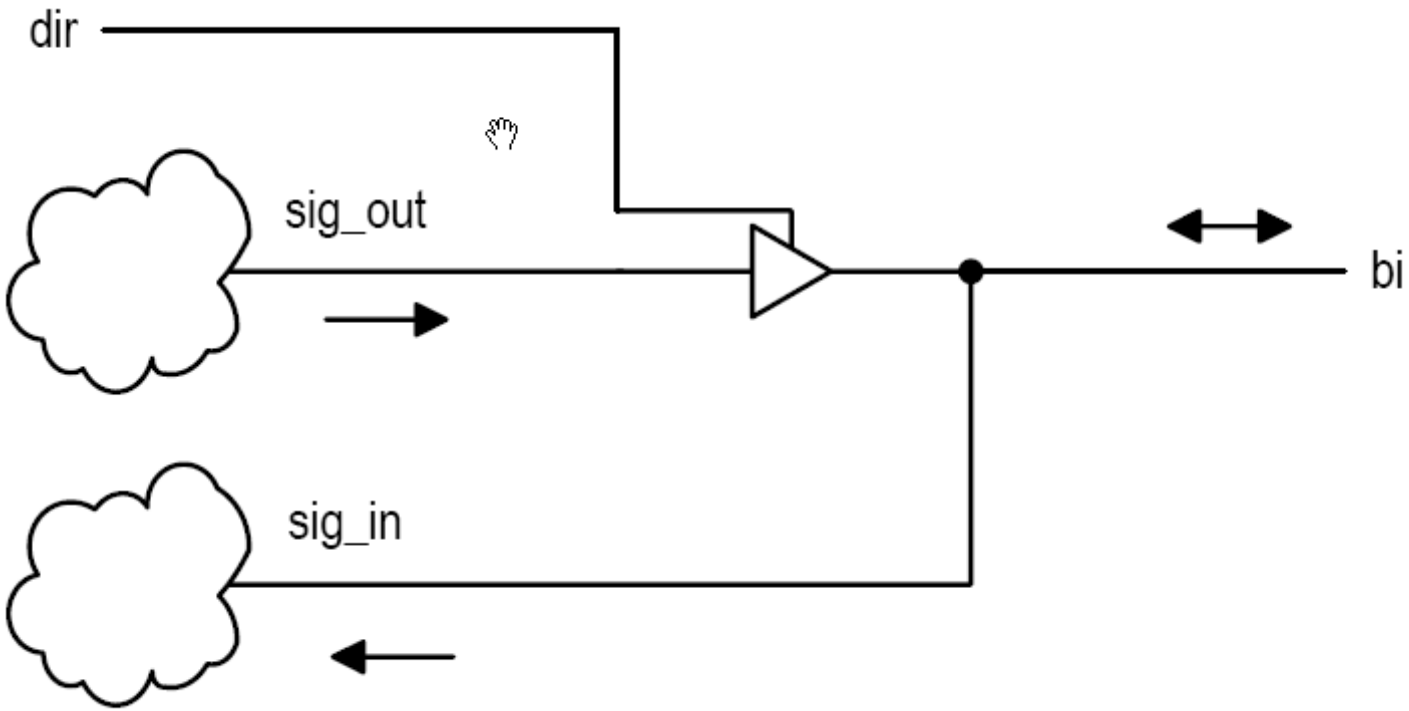


```
entity bi_demo is
   port(bi: inout std_logic;
  . . .

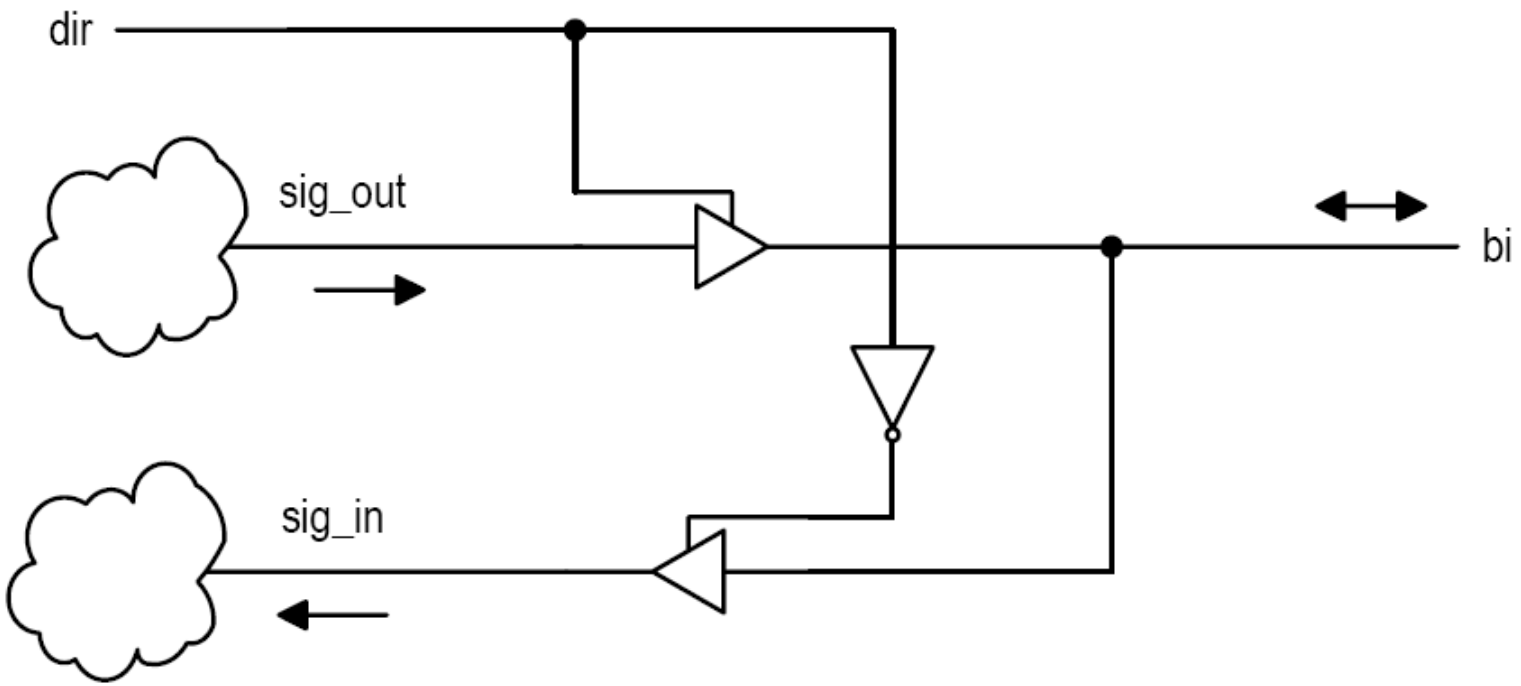begin
   sig_out <= output_expression;
    . . .  <= expression_with_sig_in;
   . . .
   bi <= sig_out when dir='1' else 'Z';
   sig_in <= bi;
   . . .
```




```
sig_in <= bi when dir='0' else 'Z';
```

Tri-state bus

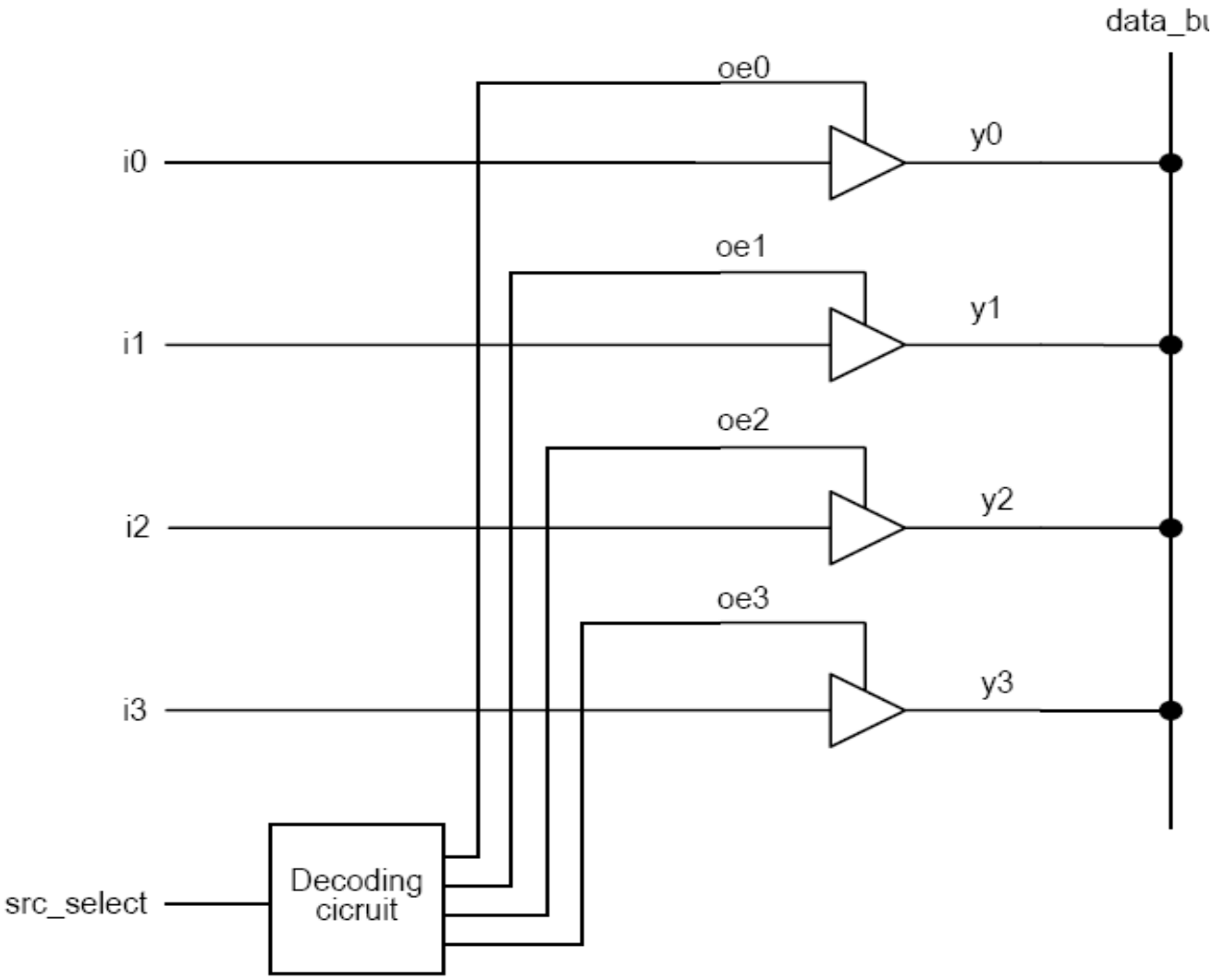

```
-- binary decoder
with src_select select
    oe <= "0001" when "00",
          "0010" when "01",
          "0100" when "10",
          "1000" when others; -- "11"
-- tri-state buffers
y0 <= i0 when oe(0)='1' else 'Z';
y1 <= i1 when oe(1)='1' else 'Z';
y2 <= i2 when oe(2)='1' else 'Z';
y3 <= i3 when oe(3)='1' else 'Z';
data_bus <= y0;
data_bus <= y1;
data_bus <= y2;
data_bus <= y3;
```

- Problem with tri-state bus
  - Difficult to optimize, verify and test
  - Somewhat difficult to design: “parking”, “fighting”
- Alternative to tri-state bus: mux

```
with src_select select
    data_bus <= i0 when "00",
                i1 when "01",
                i2 when "10",
                i3 when others;   -- "11"
```